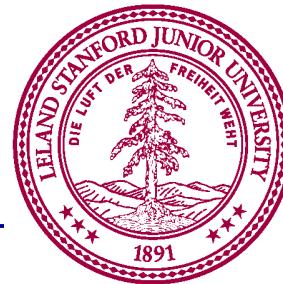


# CMOS RF Integrated Circuit Design

Shanghai Short Course  
Thomas Lee, Stanford University




# Topics

- Impedance transformation.
- Noise in LTI systems (amplifiers).
- Noise in LTV systems (oscillators and mixers).
- Nonlinearity and what to do about it
- Circuit design at extremes of frequency.
  - When good circuits go bad.
  - Exploitation of parasitics, nonlinearity, and time-variance.

# Impedance transformation


- Need to transform impedances arises frequently in RF circuits.
- Some examples:
  - Matching the input of an LNA or PA to 50 ohms (e.g., to avoid reflections on transmission lines).
  - Transforming to a smaller impedance to enable large output power at low supply voltage.
  - Maximizing power gain.
  - Minimizing noise figure.

# Why transform impedances?

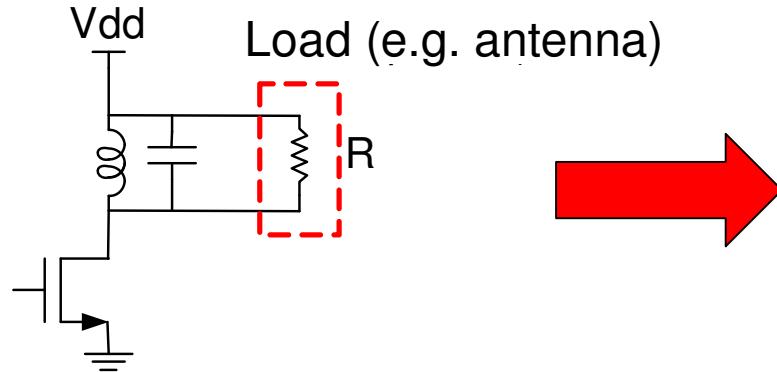

$$P_{o,max} = \frac{V_{dd}^2}{2R}$$
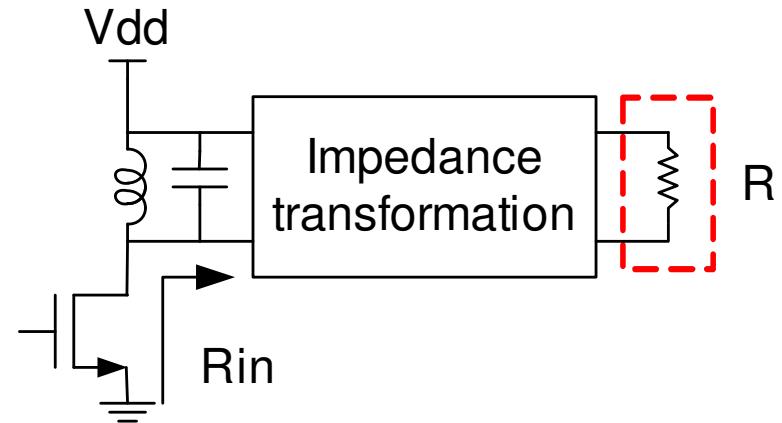
$$\left. \begin{array}{l} V_{dd} = 3V \\ R = 50\Omega \end{array} \right\} \Rightarrow P_{o,max} = 90mW$$




$$P_{o,max} = \frac{V_{dd}^2}{2R_{in}}$$

$$\left. \begin{array}{l} V_{dd} = 3V \\ R_{in} = 5\Omega \end{array} \right\} \Rightarrow P_{o,max} = 900mW$$

- Assuming lossless transformation we can deliver much more power to the load from a given supply voltage.
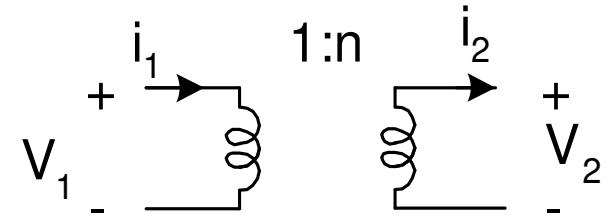
# Textbook ideal transformer

$$\left. \begin{array}{l} v_2 = nv_1 \\ i_2 = \frac{1}{n} i_1 \end{array} \right\} \Rightarrow p_2 = v_2 i_2 = nv_1 \frac{1}{n} i_1 = v_1 i_1 = p_1$$




- An ideal transformer has voltage (or current) gain, but no power gain (of course).

$$i_2 = \frac{v_2}{Z_2}$$

$$i_1 = ni_2 = n \frac{v_2}{Z_2} = n^2 \frac{v_1}{Z_2}$$
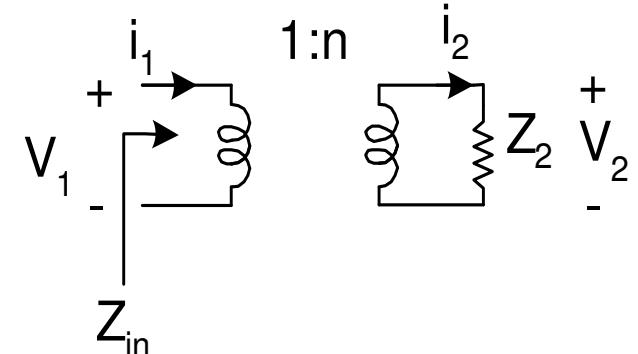
$$Z_{in} = \frac{v_1}{i_1} = \frac{Z_2}{n^2}$$





# Narrowband impedance transformation

---

- Textbook transformer is a broadband impedance transformer.
    - Broadband behavior is not always desirable.
  
  - We can replace any series  $RC$  or  $RL$  with an equivalent parallel counterpart.
    - A series resistance is transformed to a larger parallel resistance and *vice-versa*.
    - Therefore (in narrowband systems) we can use  $LC$  networks as impedance transformers.
-

# Equivalent networks (narrowband)

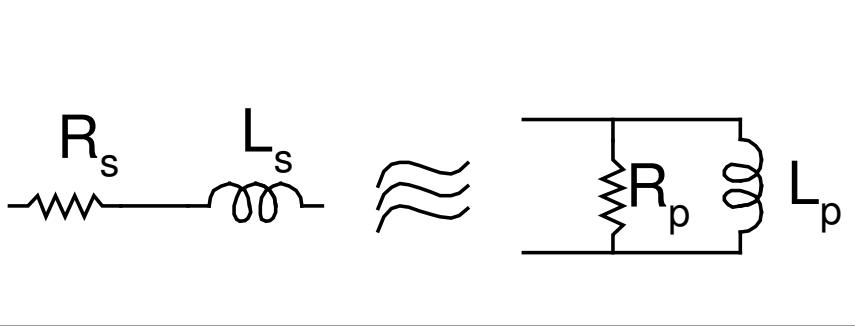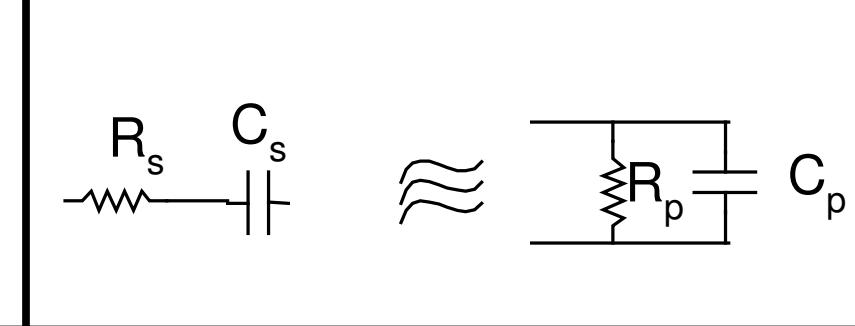			
$R_p = (1+Q^2)R_s$ $L_p = \frac{(1+Q^2)}{Q^2} L_s$	$Q = \frac{\omega L_s}{R_s} = \frac{R_p}{\omega L_p}$	$R_p = (1+Q^2)R_s$ $C_p = \frac{Q^2}{(1+Q^2)} C_s$	$Q = \frac{1}{\omega R_s C_s}$ $Q = \omega R_p C_p$

- $R_p$  is always larger than  $R_s$ .
- $X_p$  is always larger than  $X_s$ :  $X_p = \frac{(Q^2 + 1)}{Q^2} X_s = (1 + \frac{1}{Q^2}) X_s$ 
  - $L_p$  is larger than  $L_s$ .
  - $C_p$  is smaller than  $C_s$ .


# Impedance transformer: The *L*-match

- Suppose we want to transform  $R_p$  to a lower impedance  $R_s$

$$1) \quad Q = \sqrt{\frac{R_p}{R_s} - 1}$$

$$2) \quad X_p = \frac{R_p}{Q}$$
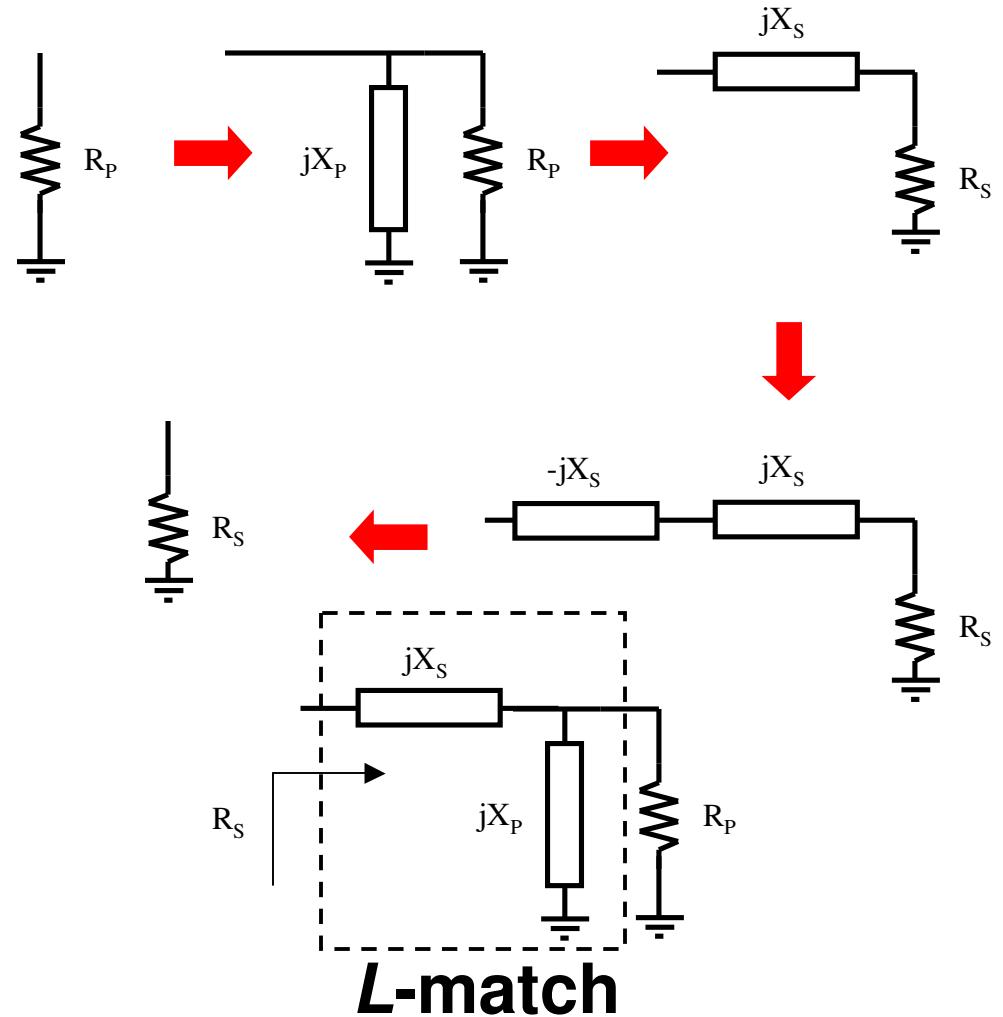
$$3) \quad X_s = X_p \left( \frac{Q^2}{Q^2 + 1} \right)$$




# Impedance transformer: The *L*-match

- Now suppose we want to transform  $R_s$  to a higher impedance  $R_p$

$$1) \quad Q = \sqrt{\frac{R_p}{R_s} - 1}$$


$$2) \quad X_s = QR_s$$
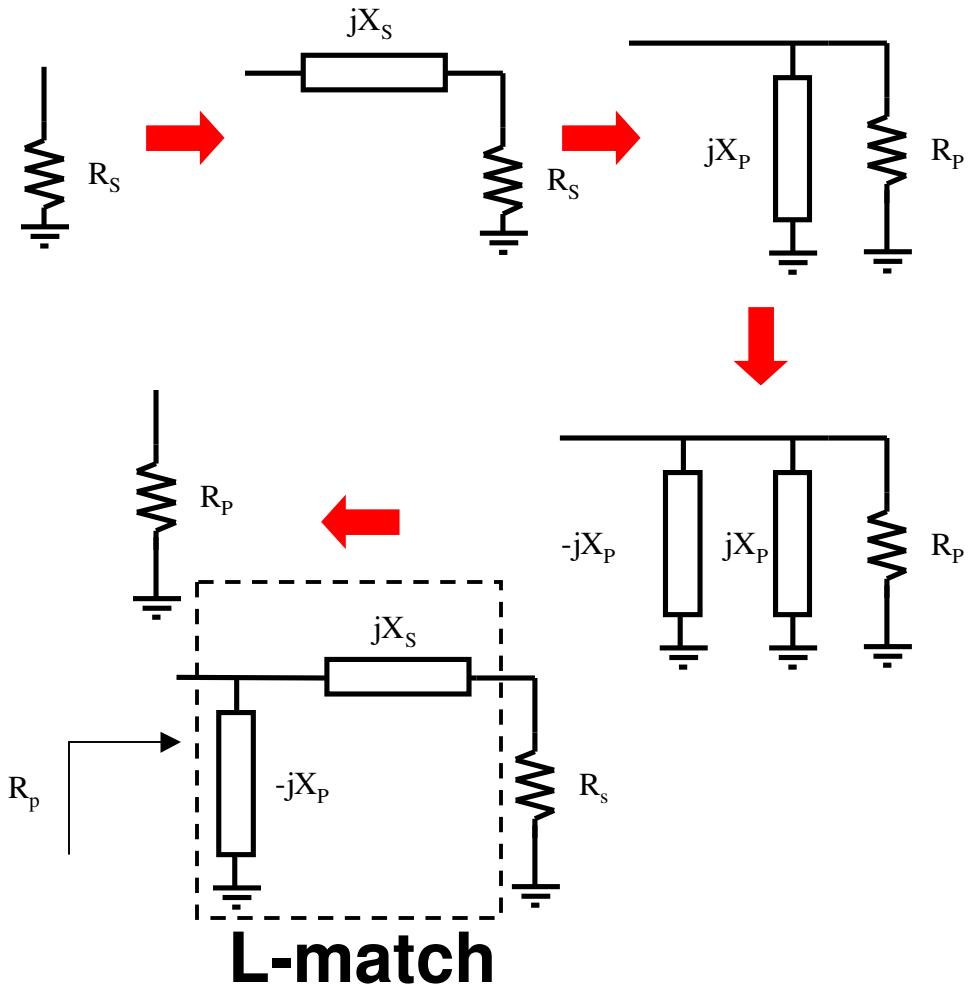
$$3) \quad X_p = X_s \left( \frac{Q^2 + 1}{Q^2} \right)$$


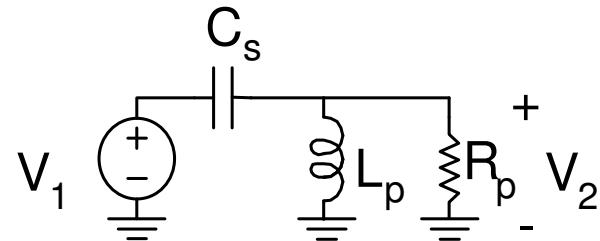
# L-match: Voltage gain

- The  $L$ -match transforms impedance like a broadband ideal transformer, so it also transforms voltages.



- In a lossless  $L$ -match all of the power from  $V_1$  is delivered to  $R_p$ , so:

$$\frac{V_1^2}{2R_s} = \frac{V_2^2}{2R_p} \Rightarrow \frac{V_2}{V_1} = \sqrt{\frac{R_p}{R_s}} = \sqrt{Q^2 + 1}$$


- As with an ideal transformer the voltage gain is the square-root of the impedance transformation ratio.

# L-match example

- Ex: Transform  $50\Omega$  to  $5\Omega$  at 1GHz:


$$\left. \begin{aligned} Q &= \sqrt{\frac{R_p}{R_s} - 1} = 3 \\ L_p &= \frac{R_p}{\omega Q} = \frac{50\Omega}{(2\pi * 10^9)(3)} = 2.6nH \\ C_s &= \frac{1}{\omega R_s Q} = \frac{1}{(2\pi * 10^9)(5\Omega)(3)} = 10.6pF \end{aligned} \right\}$$

**high-pass L-match**

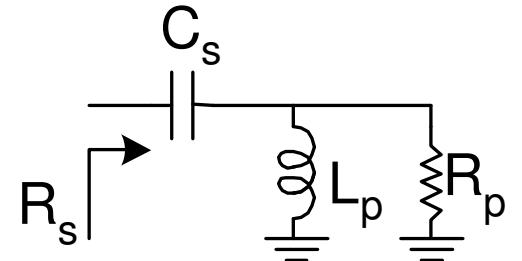



$$\left. \begin{aligned} C_p &= \frac{Q}{\omega R_p} = \frac{3}{(2\pi * 10^9)50\Omega} = 9.5pF \\ L_s &= \frac{R_s Q}{\omega} = \frac{3\Omega * 5}{2\pi * 10^9} = 2.4nH \end{aligned} \right\}$$

**low-pass L-match**


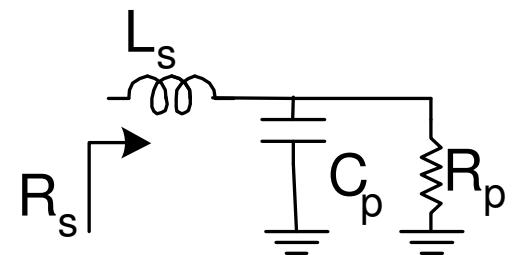


# L-match example (cont.)


## High-pass L-match

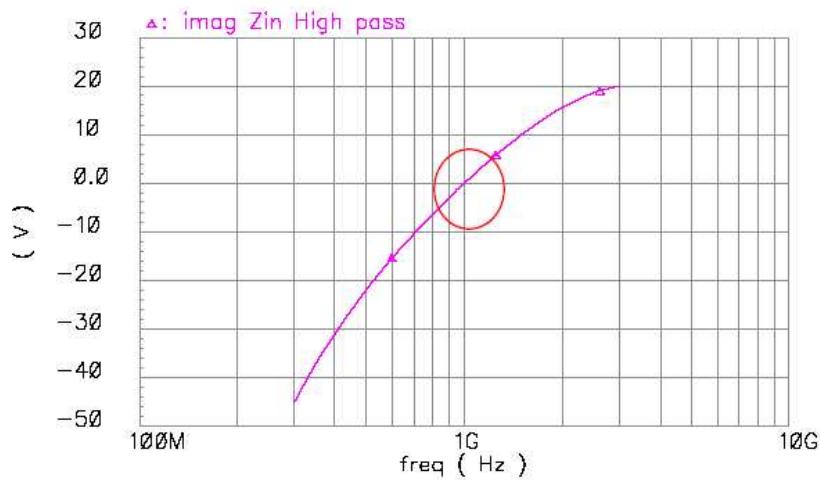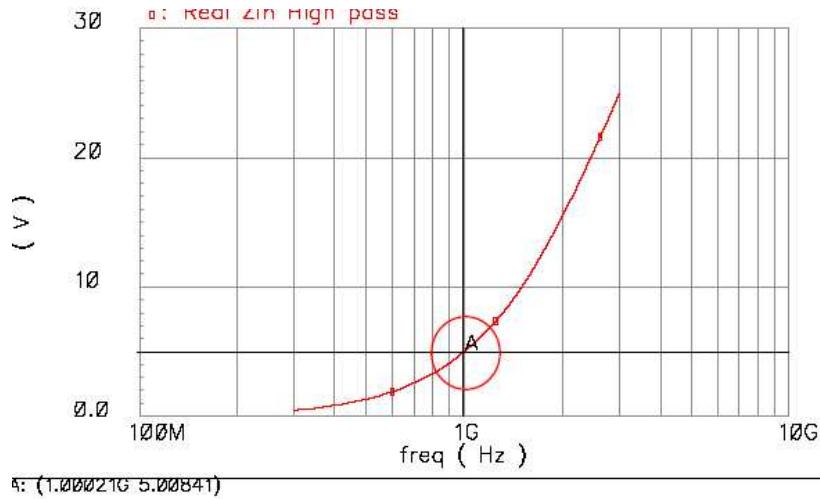

## Low-pass L-match

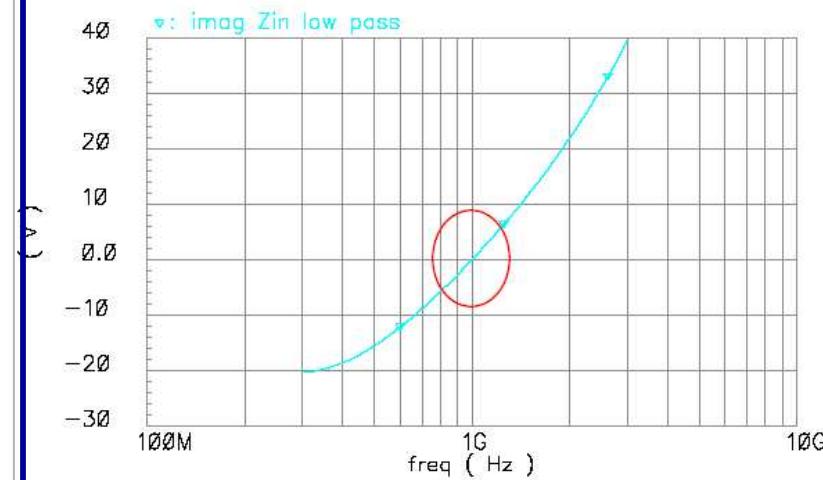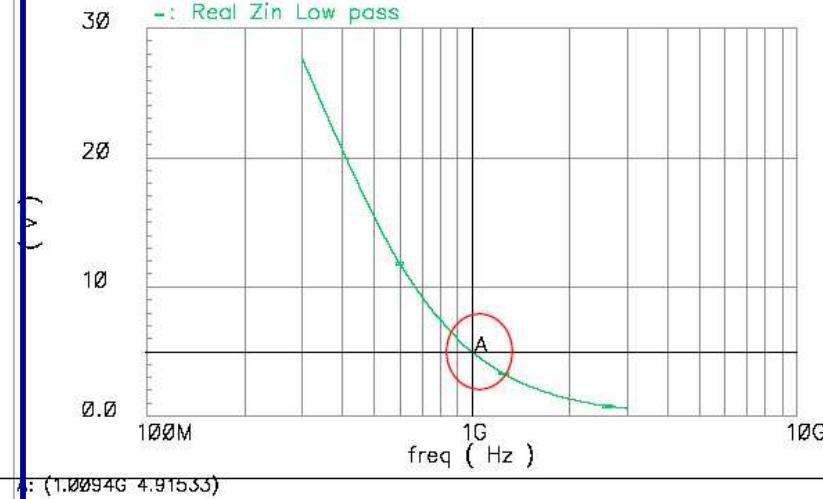

# L-match example (cont.)

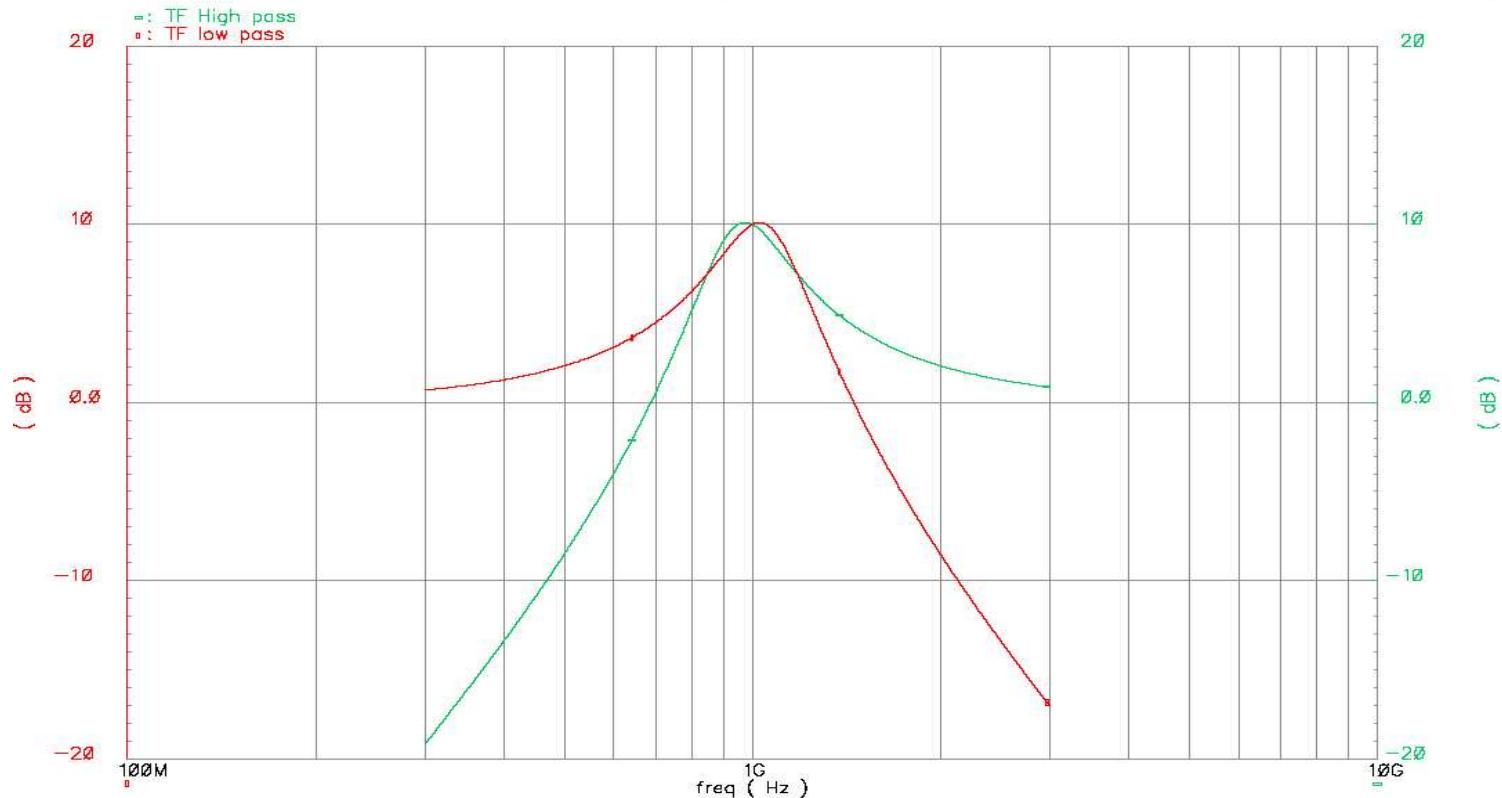

- In the high-pass network voltage gain is unity at high frequencies.
- In the low-pass network voltage gain is unity at DC.

# ***L*-match summary**


---

- In a single *L*-match, the matching network's  $Q$ , and therefore the bandwidth, are set by the transformation ratio.
- Sometimes the bandwidth is unacceptable or the component values are impractical.
- In those cases one would seek additional design degrees of freedom.

# Impedance transformers: $T$ - and $\pi$ -match


- $L$ -match stages can be cascaded for added degrees of freedom.

Cascaded  $L$ -match

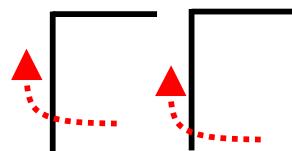

- “Double- $L$ ” transforms impedance in only one direction.
- Widest bandwidth.

$T$ -match

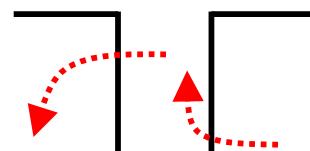


- First stage transforms up, and second stage transforms down.
- Bandwidth is less than single  $L$ -match.

$\pi$ -match




- First stage transforms down, and second stage transforms up.
- Bandwidth is less than single  $L$ -match.

# Cascaded $L$ -match

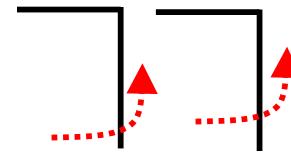

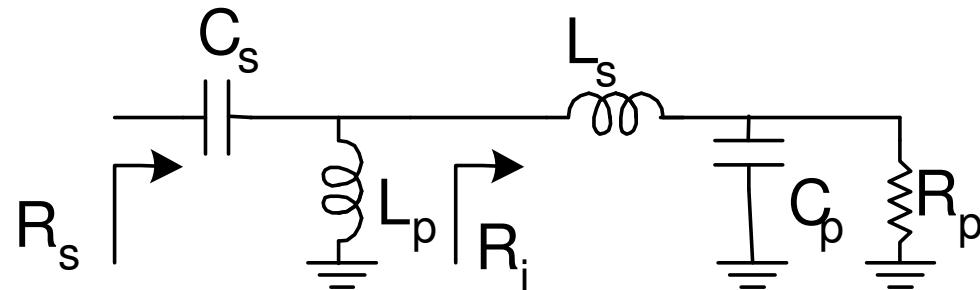
- Specify intermediate impedance  $R_i$  to control Q (BW) and response shape. Design problem is then that of two separate  $L$ -match designs.
- Can combine high-pass and low-pass stages to get both AC coupling and high-frequency (e.g. harmonic) rejection:


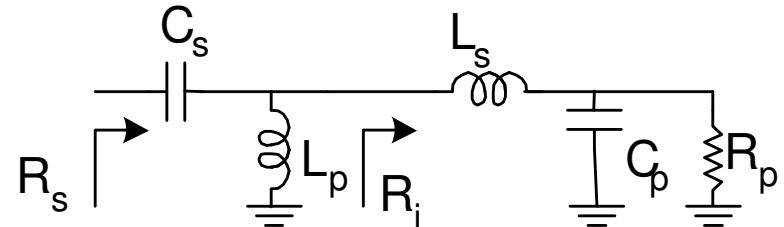
# Cascaded L-match:

(High-pass followed by low-pass)

( $R_s=5$ ,  $R_p=50$ ,  $f=1\text{GHz}$ )



$$R_i = \sqrt{R_p R_s} = 15.8$$

$$Q_l = \sqrt{\frac{R_i}{R_s} - 1} = Q_r = \sqrt{\frac{R_p}{R_i} - 1} = 1.47$$

$$C_p = \frac{Q}{\omega R_p} = \frac{1.47}{(2\pi * 10^9) 50\Omega} = 4.7 \text{ pF}$$

$$L_s = \frac{R_i Q}{\omega} = \frac{15.8\Omega * 1.47}{2\pi * 10^9} = 3.70 \text{ nH}$$



$$L_p = \frac{R_p}{\omega Q} = \frac{15.8\Omega}{(2\pi * 10^9)(1.47)} = 1.7 \text{ nH}$$

$$C_s = \frac{1}{\omega R_s Q} = \frac{1}{(2\pi * 10^9)(5\Omega)(1.47)} = 21.6 \text{ pF}$$

- “Arbitrarily” chose  $R_i$  equal to geometric mean of input-output impedances. Component values will differ if different  $R_i$  is chosen.

# Cascaded L-match



(High-pass followed by low-pass)

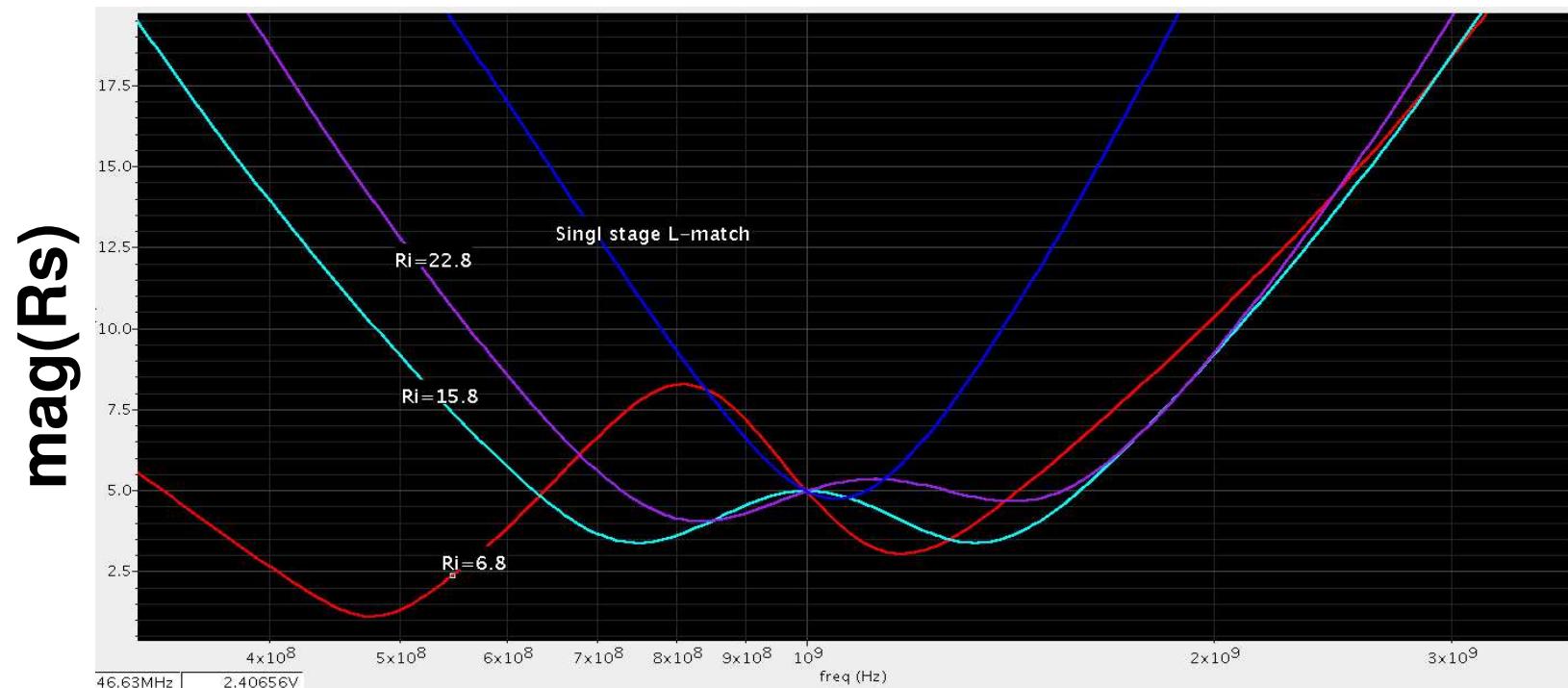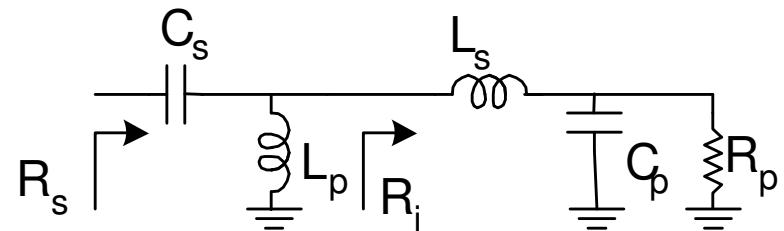

- Symmetric input resistance results when  $R_i = \sqrt{R_p * R_s}$ .
- Symmetric choice also yields widest BW around the design frequency.
- Matching bandwidth is much wider than that of single L-match.

# Cascaded L-match


(High-pass followed by low-pass)

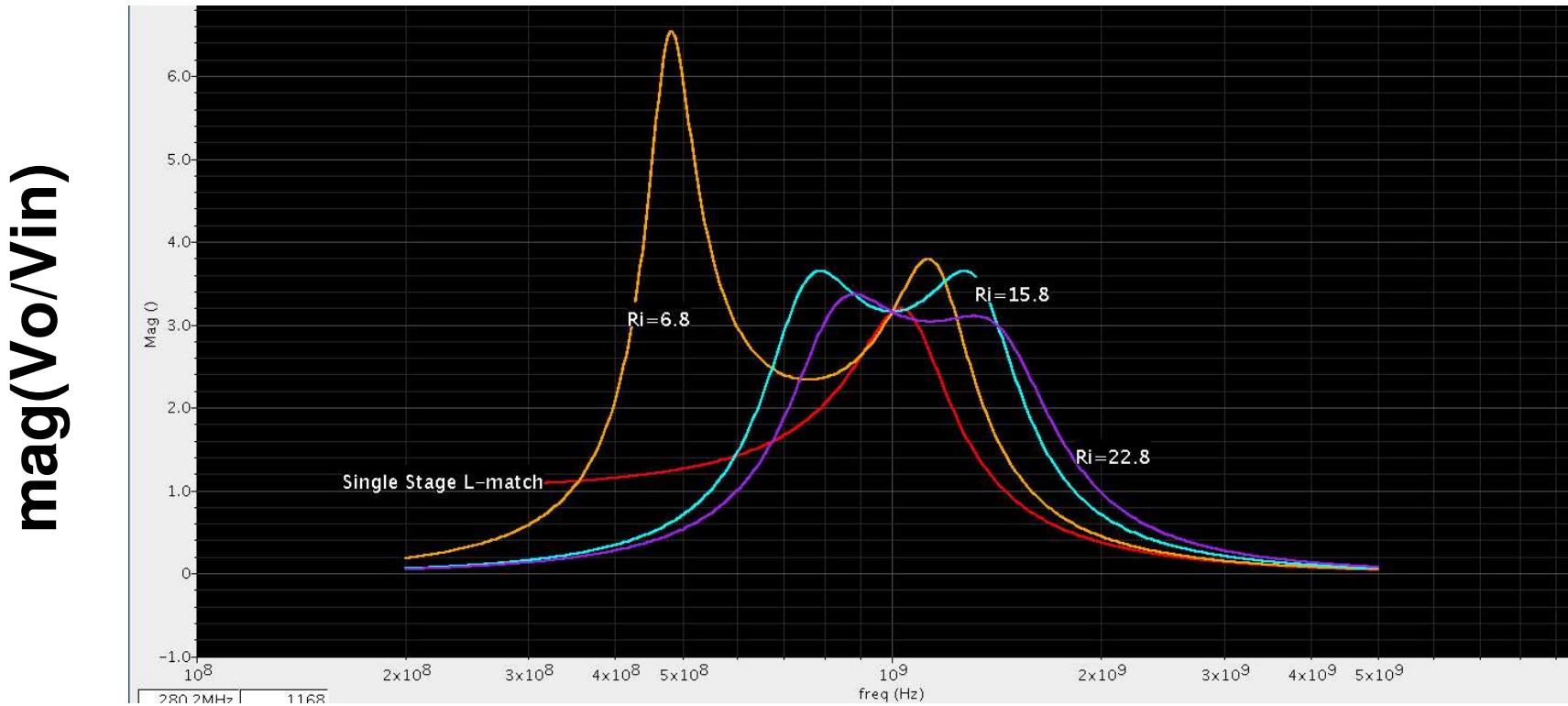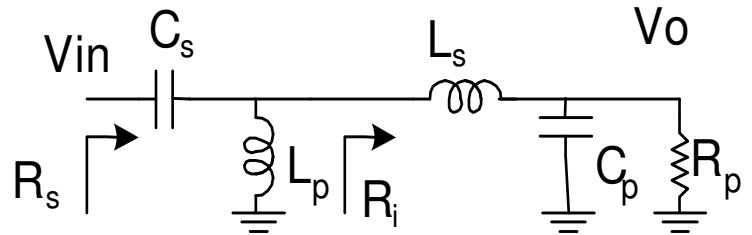

- Symmetric gain results when  $R_i = \sqrt{R_p * R_s}$ .
- $R_i = \sqrt{R_p * R_s}$  results in widest BW around the design frequency.
- Gain at design frequency is  $\sqrt{R_p/R_s} = \sim 3.2$  for all cases.
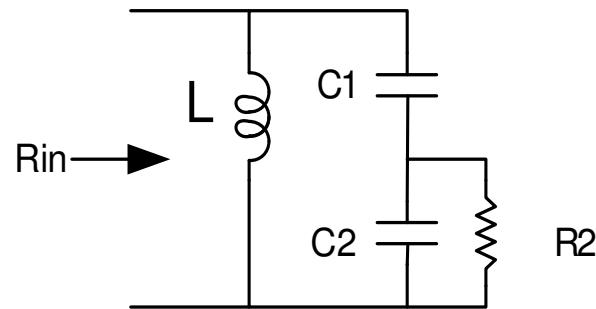
# Tapped capacitor network

- Tapped capacitor is just a voltage divider:




$$\frac{R_2}{R_{in}} \approx \left( \frac{C1}{C1+C2} \right)^2$$

- Impedance transformation ratio is approx. the square of the voltage divide ratio.
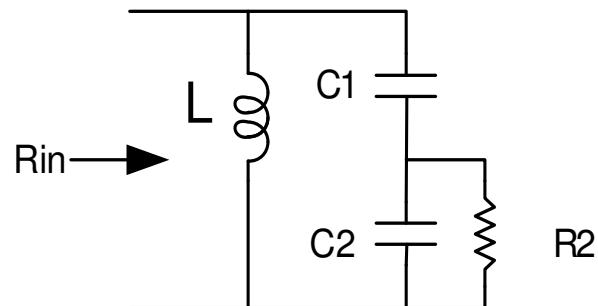
# Tapped capacitor network

- It's left as an exercise to derive the exact formula. (Hint: Convert  $R_2-C_2$  into series equivalent; combine  $C_1$  and  $C_{2s}$  into a single capacitor; convert series  $RC$  into parallel  $RC$ .)



# Why *not* transform impedances?

- Maximizing power transfer isn't always necessary.
  - Impedance transformers consume precious die area, so don't use them unless you have to.
  - Transformers frequently limit bandwidth, too.
- Some amplifiers exhibit improved stability margin with mismatches.
- Later, we will see that most amplifiers exhibit best noise performance with a *mismatch*.

# Introduction to noise

# Noise

---


- All electronic circuits generate noise.
- Random thermal (Brownian) motion of charge carriers is ultimately the origin of noise.
- Both passive and active circuits exhibit noise.
- Due to its random nature, noise must be described with the language of statistics.

# Noise: A little history

- In 1926 Bell Labs' John B. Johnson made careful measurements of thermal noise.
  - Resistors generate noisy voltages/currents!
  - *Q: Why can't we use this phenomenon as a power source?*
- His colleague Harry Nyquist derived the theory with an elegant set of arguments.

# Nyquist and noise: “Available power”

- Consider a doubly-terminated T-line:

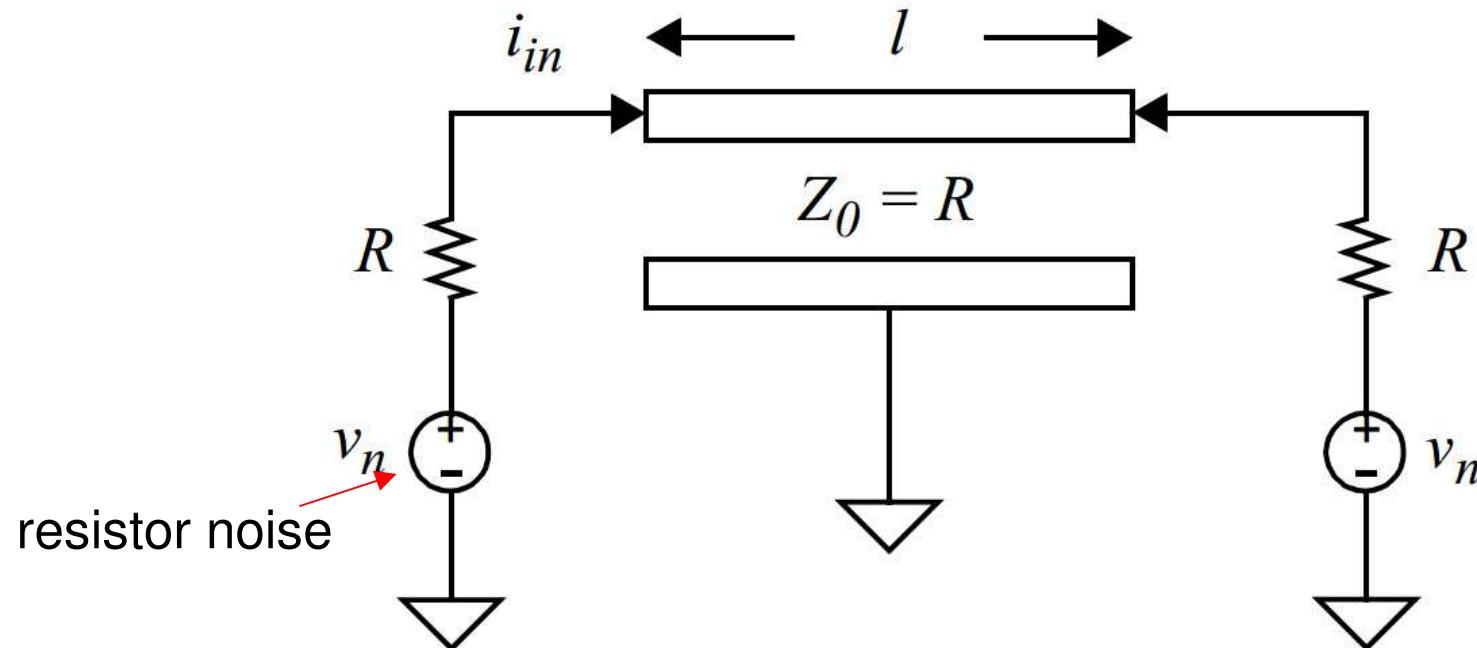

- At equilibrium, as much power flows to the right as flows to the left.
  - Also true within any frequency interval.

# Available power

- Now, the average power supplied by one source to the other is:

$$P_L = \frac{\overline{v_n^2}}{4R} = P_R$$

- Treat noise as random sinusoids propagating back and forth at velocity  $v$ . Then the average energy stored along a line of length  $l$  is

$$U = (P_L + P_R) \frac{l}{v} = \frac{\overline{v_n^2}}{2R} \frac{l}{v}$$

# Available power

- If *equipartition* holds, the spectral density is frequency-independent at a value

$$\frac{U}{\Delta f} = \frac{(P_L + P_R)}{\Delta f} \frac{l}{\nu} = \frac{\overline{\nu_n^2}}{2R\Delta f} \frac{l}{\nu}$$

- Next, compute the spectral density a different way and equate the two expressions.

# Available power

- Suddenly short-circuit both ends of the line. The allowed modes have zero voltage at the ends:

$$\lambda_n = \frac{2l}{n} \Rightarrow f_n = n \frac{\nu}{2l}$$

- If the line is “very long,” the distribution of modes will approach a continuum with density

$$\frac{dn}{df} = 2 \frac{l}{\nu}$$

# Available power

- Again invoke equipartition, with  $kT$  energy per mode ( $kT/2$  each for  $E$  and  $H$ ):

$$\frac{dn}{df} kT = \frac{2l}{\nu} kT$$

- Now equate our first expression for energy spectral density to the second:

$$\frac{\overline{\nu_n^2}}{2R\Delta f} \frac{l}{\nu} = \frac{2l}{\nu} kT$$

# Available power

- We may therefore write, at last, that

$$\frac{\overline{v_n^2}}{4R} = kT\Delta f$$

- This is the power that would be delivered to a matched load; it's the *available* power,  $P_{NA}$ .
- The rhs says that  $P_{NA}$  is proportional to the bandwidth of the measurement.
  - And to  $T$ .

# Thermal noise

- Nyquist showed how thermal agitation of charge results in noisy voltage (and current, via Ohm's law).
  - Amplitude of the thermal noise is Gaussian-distributed with zero mean but non-zero variance (i.e., non-zero power)

$$\overline{v_n(t)} = \frac{1}{T} \int_T v_n(t) dt = 0$$

$P_{NA} = kT\Delta f$  : Available noise power

$k = 1.38 \times 10^{-23} J/K$  : Boltzmann's constant

$T$  : Absolute temperature in kelvins

- Remember: Available power is defined as the maximum power that *could* be delivered to a load.
  - It does not have to be delivered; we only care that it is *available*.

# Refresher on Gaussian distributions


- The Gaussian (normal) distribution is the most widely used continuous PDF for real-valued random variables.

- Here,  $\mu$  is the mean.
- $\sigma^2$  is the variance.
- If  $\mu=0$  then  $\sigma$  is the RMS value.

$$\mu = \int_{-\infty}^{+\infty} xf(x)dx : \text{1st moment (mean)}$$

$$\sigma^2 = \int_{-\infty}^{+\infty} (x - \mu)^2 f(x)dx : \text{2nd moment (variance)}$$
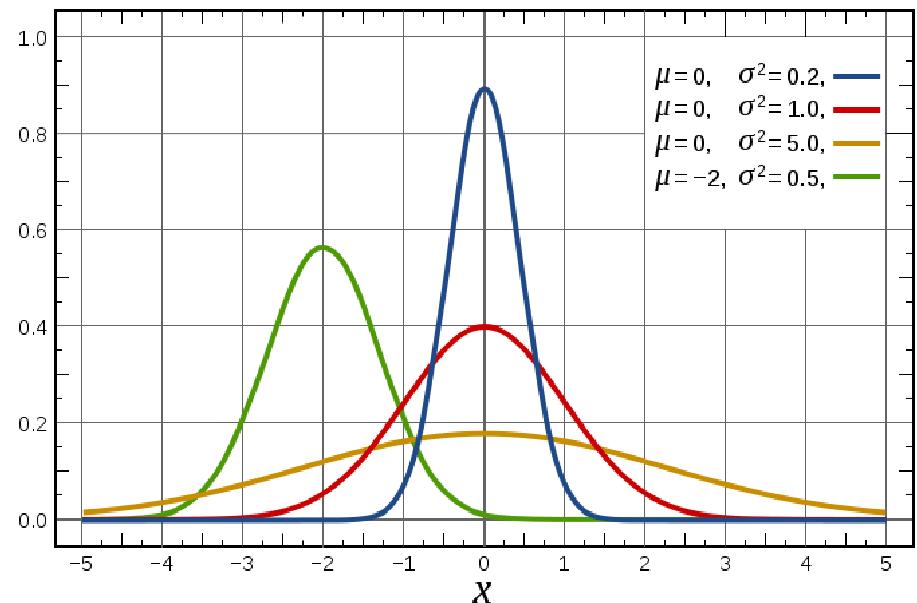
$$f(x) = \frac{1}{\sqrt{2\pi\sigma^2}} e^{-\frac{(x-\mu)^2}{2\sigma^2}}$$



# Thermal noise properties


$$P_{NA} = kT\Delta f$$

- Available noise power is *independent* of the resistance value.
  - $P_{NA}=-174\text{dBm/Hz}$  @ “room” temperature ( $17^\circ\text{C}=290\text{K}$ )
- Thermal noise power is proportional to the absolute temperature.
  - Circuits become noisier when hot!

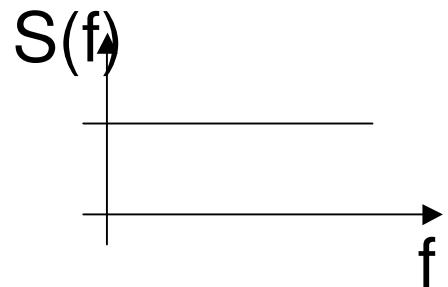
# Thermal noise properties

$$P_{NA} = kT\Delta f$$

- Available noise power has flat spectral density  $S(f)$  and is thus called “white.”
  - Noise power will be infinite if integrated over an infinite bandwidth!
- Q: What happens if white noise drives a system with non-flat spectral response?


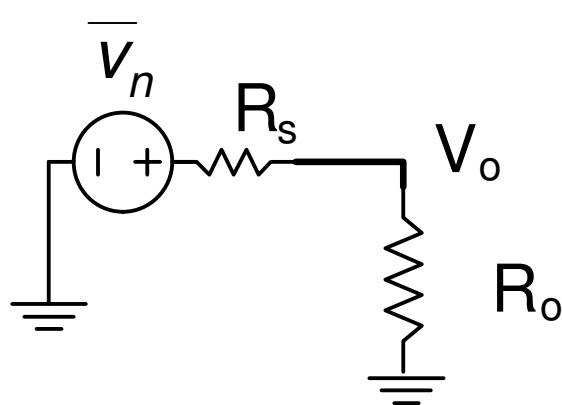
# Resistor noise: $P_{NA}$ vs. rms voltage



$$P_{no} = \frac{V_{no,rms}^2}{R_o}$$


$$V_{no,rms}^2 = \bar{v}_n^2 \left( \frac{R_0}{R_0 + R} \right)^2 \xrightarrow{R_0=R_s} V_{no,rms}^2 = \frac{\bar{v}_n^2}{4}$$

$$P_{NA} = \frac{V_{no,rms}^2}{R} = \frac{\bar{v}_n^2 / 4}{R} \Rightarrow \bar{v}_n^2 = 4kTR\Delta f$$

- $\bar{v}_n$  is the open-circuit rms noise voltage of the resistor.
- Example: If  $R=1\text{k}\Omega$  and  $\Delta f=100\text{MHz}$ , then

$$V_{no,rms} = 4nV\sqrt{100\text{MHz}} = 40\mu\text{V}.$$


# Resistor thermal noise models

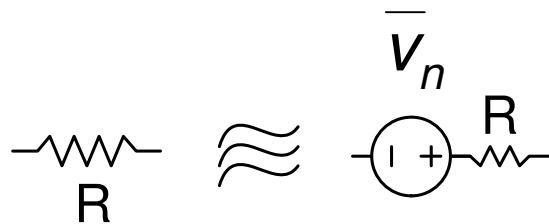

$$P_{NA} = kT\Delta f = \frac{\bar{v}_n^2}{4R}$$

$$\bar{v}_n^2 = 4kTR\Delta f$$

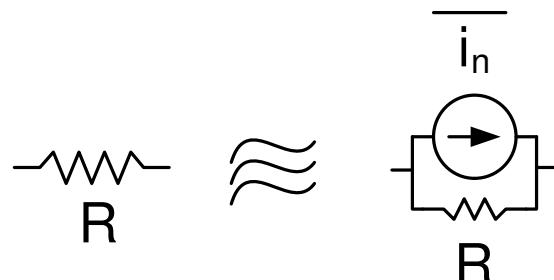$\bar{v}_n$  is the open-circuit rms noise voltage




$$P_{NA} = kT\Delta f = \frac{\bar{i}_n^2}{4} R$$

$$\bar{i}_n^2 = \frac{4kT}{R} \Delta f$$

$\bar{i}_n$  is the short-circuit rms noise current

# Series $R$ thermal noise (example)

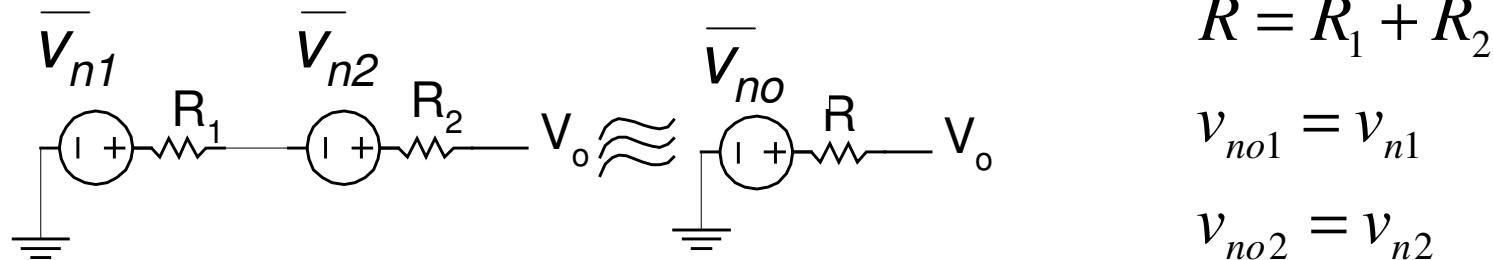

$$v_{no} = v_{no1} + v_{no2}$$

$$\overline{v_{no}^2} = E\{(v_{no1} + v_{no2})^2\} = E\{v_{no1}^2 + v_{no2}^2 + 2v_{no1}v_{no2}\}$$


$$\begin{aligned} \overline{v_{no}^2} &= E\{v_{no1}^2\} + E\{v_{no2}^2\} + E\{2v_{no1}v_{no2}\} = \overline{v_{no1}^2} + \overline{v_{no2}^2} + 2E\{v_{no1}v_{no2}\} \\ \overline{v_{no}^2} &= \overline{v_{n1}^2} + \overline{v_{n2}^2} = 4kT(R_1 + R_2)\Delta f \end{aligned}$$

- The noise of  $R_1$  is uncorrelated with that of  $R_2 \Rightarrow$  the variance of the output noise voltage ( $v_{no}$ ) is just the sum of the variances of  $v_{no1}$  and  $v_{no2}$ .
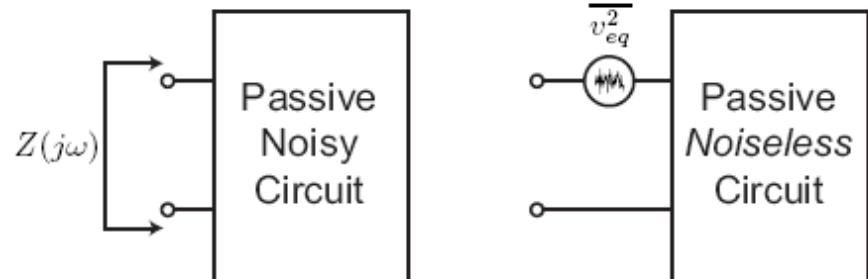
# Thermal noise in *RLC* circuits

- Ideal capacitors and inductors do not *generate* noise, but they may propagate and filter it.
- For a general passive circuit the equivalent mean-squared voltage (or current) noise is:
  - Only a function of the real part of the impedance, not of the imaginary (i.e. reactive) part; noise comes from dissipation.
  - Not white (i.e., NOT flat across frequency). We use ***spot noise*** for voltage (or current) noise at a given frequency.

$$\overline{v^2_{eq}} = 4kT \operatorname{Re}\{Z(j2\pi f)\}df$$




# Thermal noise in *RLC* circuits

- To calculate the total noise we integrate the mean-squared noise over the bandwidth of interest:

$$\overline{v^2_{eq}} = 4kT \operatorname{Re}\{Z(j2\pi f)\}df$$

$$\overline{v^2_{eq,T}} = 4kT \int_B \operatorname{Re}\{Z(j2\pi f)\}df$$


# RLC network noise (example)

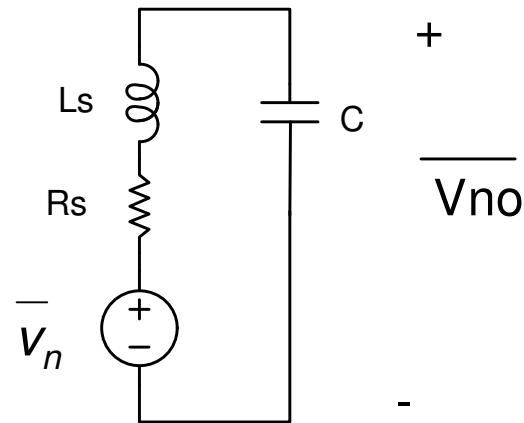

- Let's consider an  $LC$  network with lossy  $L$ .
- What is the rms noise voltage across the  $LC$  network within a small  $\Delta f$  of the resonant frequency?
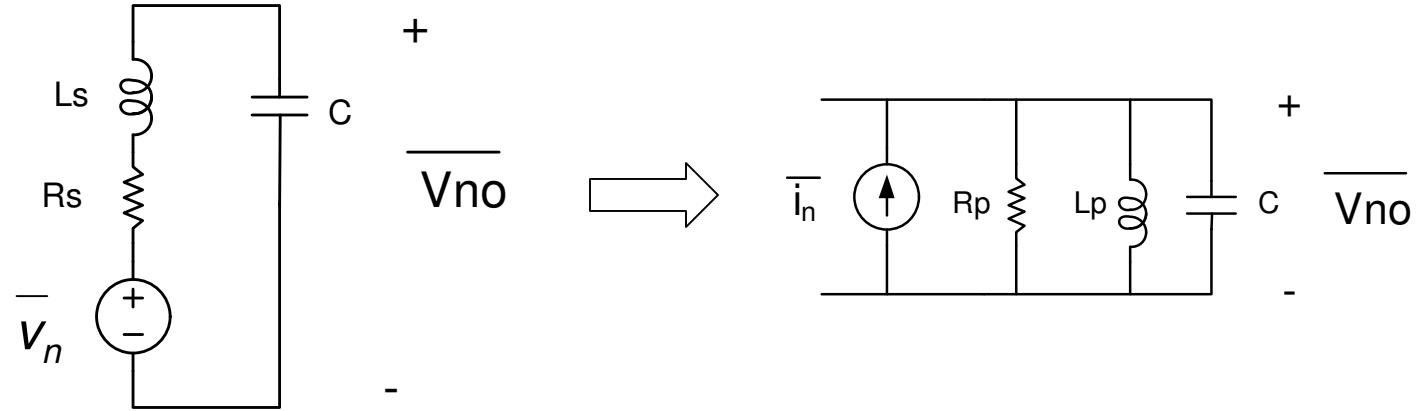
# RLC noise (example, continued)

- Let's do a series-to-parallel transformation:




$$Z(jf) \approx \frac{R_p}{1 + j2Q\frac{f}{f_0}} = \frac{R_p}{1 + \left(2Q\frac{f}{f_0}\right)^2} \left(1 - j2Q\frac{f}{f_0}\right)$$

$$-\frac{\Delta f}{2} < f < \frac{\Delta f}{2} \quad \text{and} \quad Q\Delta f \ll f_0$$

$$\overline{v_{no,rms}^2} = 4kT \int_{-\Delta f/2}^{\Delta f/2} \operatorname{Re}\{Z(jf)\} df = 4kTR_p \int_{-\Delta f/2}^{\Delta f/2} \frac{1}{1 + \left(2Q\frac{f}{f_0}\right)^2} df = 4kTR_p \left. \frac{\tan^{-1}\left(\frac{2Q}{f_0}f\right)}{2Q/f_0} \right|_{f=-\Delta f/2}^{f=\Delta f/2} \approx 4kTR_p \Delta f$$

# Filtering white noise

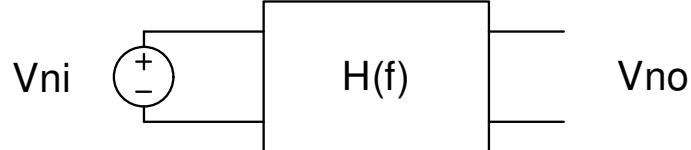

$$S_i(f) = kT$$

$$S_o(f) = S_i(f) \times |H(f)|^2 = kT |H(f)|^2$$

- The noise spectral density is shaped by the filter so that the output noise spectral density is no longer flat across frequency.
- To calculate the available noise power at the output we need to integrate the noise spectral density over the frequency band:

$$P_{NAo} = \int S_o(f) df$$

# Equivalent noise bandwidth

- The idea is to define a term for noise bandwidth similar to the way we define bandwidth for signals.
- *Equivalent noise bandwidth* is the bandwidth of a brick-wall (i.e., rectangular) filter with the same peak and total noise power as that of the system in question.

$$\Delta f_n = \frac{1}{|H_{pk}|^2} \int_0^{\infty} |H(f)|^2 df$$


- *Q: Is the noise bandwidth the same as -3dB bandwidth?*

# Equivalent noise bandwidth (cont.)

- The 3dB bandwidth is simply the half-power frequency.
  - If the rolloff is not abrupt then substantial noise energy will lie beyond the 3dB frequency.
- Let's look at this graphically...
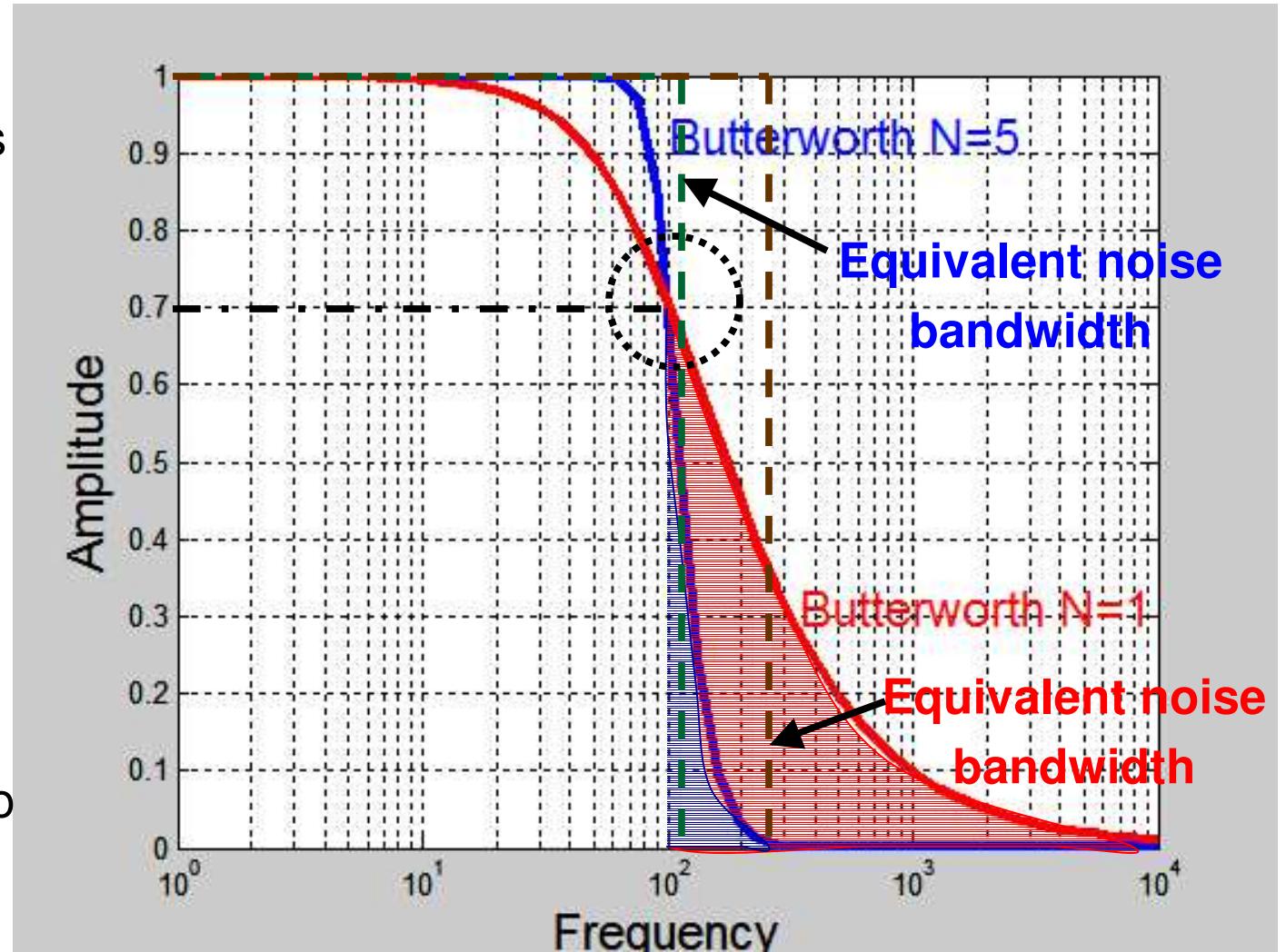
# Equivalent noise bandwidth (cont.)

- Consider two Butterworth filters with equal 3dB BW but unequal orders.
- The 5<sup>th</sup>-order filter's rolloff is steeper than that of the other. Therefore the noise BW of the former is closer to the 3dB BW.



# Noise in active devices

---


- Nyquist's derivation assumes thermal equilibrium.
- Non-equilibrium is accommodated by adding fudge factors to equilibrium equations.

# MOSFET drain current noise

$\overline{i_n^2} = 4kT\gamma g_{d0}\Delta f$ ; this is a modified resistor current noise eqn.

$g_{d0}$ : Drain - source conductance @  $V_{DS} = 0$
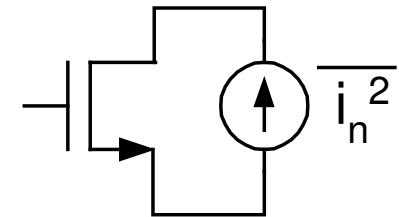
$$\gamma = \begin{cases} 1 & V_{DS} = 0 \\ 2/3 & \text{Saturation (long channel)} \\ \frac{4}{3} \text{ to } 2 & \text{Saturation (short channel)} \end{cases}$$



- At low  $V_{DS}$  the MOS device behaves like a resistor and  $\gamma$  is unity.
- Excess noise factor ( $\gamma$ ) is ~2 times larger in short-channel devices, compared to long-channel devices.

# MOSFET drain current noise

---

- High electric field is partly to blame for the excess noise in short channel devices ⇒
  - Using minimum practical  $V_{DS}$  will reduce the excess noise in short-channel devices.
- PMOS devices show less excess noise than NMOS in the short-channel regime.

# Flicker noise

- Power spectral density of flicker ( $1/f$ ) noise increases as frequency decreases.
- Sensitivity to surface phenomena (such as charge trapping) worsens  $1/f$  noise.  
MOSFETs exhibit *much* worse  $1/f$  noise than bipolar devices.
- Resistors exhibit flicker noise which increases with DC drop across the resistor.

$$\overline{v_n^2} = \frac{K}{f} \frac{R^2}{A} V_{DC}^2 \Delta f$$

# MOSFET flicker noise


$$\overline{i_n^2} = \frac{K}{f} \frac{g_m^2}{WLC_{ox}^2} \Delta f$$

- The flicker and drain thermal noise are equal at the “ $1/f$  corner” frequency.
- Increasing the device area (for a given  $g_m$ ) reduces the  $1/f$  corner.
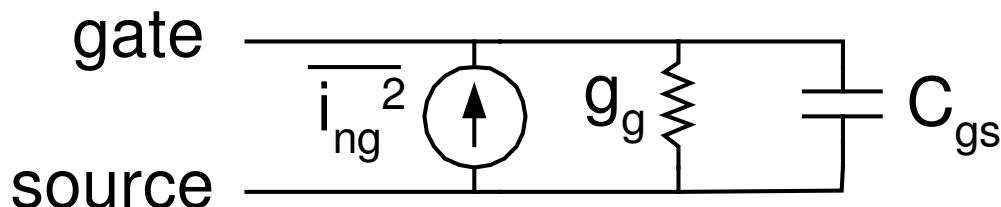
# MOSFET gate noise

- Noisy channel charge couples capacitively to the gate and induces a noisy **gate current**.

$$\overline{i_{ng}^2} = 4kT\delta g_g \Delta f$$



$$g_g = \frac{\omega^2 C_{gs}}{5g_{d0}}$$

$$\delta = \frac{4}{3} \approx 2\gamma$$


- Gate noise factor ( $\delta$ ) is twice the drain noise factor ( $\gamma$ ) in long-channel devices.
  - We often use the same ratio for short-channel devices as well, in the absence of actual data.
  - $\delta = 8/3-4$  for short-channel devices, conservatively.

# MOSFET gate noise (cont.)

- Gate noise has the same origin as the drain noise so the two will be *correlated*.
  - ***Cannot simply add their powers to calculate total noise!***
- Gate noise current increases with frequency (it's “blue,” not white).
- Gate noise is usually negligible at low frequencies.
  - It can dominate in high frequency/high impedance circuits.
- For those who are bothered by “blue noise,” there is an alternative model with white noise:
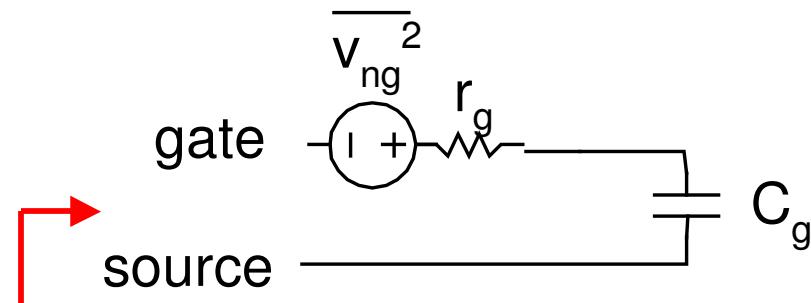
# MOSFET gate noise

- A parallel-to-series transformation works miracles:



ACHTUNG!  $V_{gs}$  is defined across the series combination of  $C_g$  and  $r_g$ .

$$\overline{v_{ng}}^2 = 4kT\delta r_g \Delta f$$

$$Q = \frac{\omega C_{gs}}{g_g} = \frac{5g_{d0}}{\omega C_{gs}} = \frac{5}{\alpha} \frac{\omega_T}{\omega} \gg 1$$


$$C_g = C_{gs} \frac{Q^2 + 1}{Q^2} \approx C_{gs}$$

$$r_g = \frac{1}{g_g} \frac{1}{Q^2 + 1} \approx \frac{1}{g_g Q^2} = \frac{1}{5g_{d0}}$$

- Magically,  $v_{ng}$  has a *flat* spectral density!
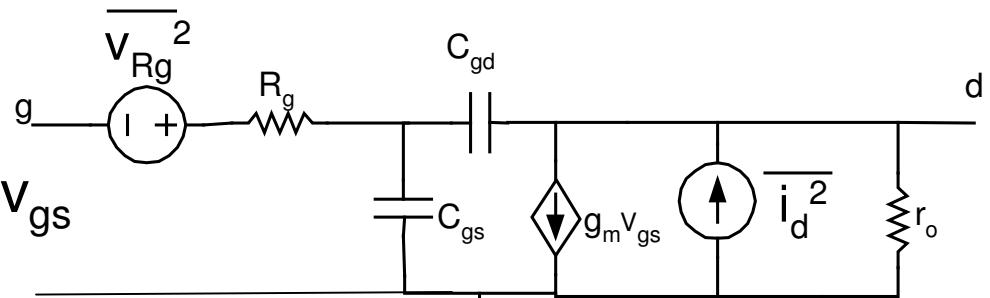
# MOS noise model

Again:  $V_{gs}$  is defined across the series combination of  $C_{gs}$  and  $R_g$ .



- Gate resistance has two terms:
  - Induced gate noise resistance.
  - Gate poly resistance.
- $n$  is number of gate fingers.
- Factor of 1/3 in  $r_p$  comes from the distributed nature of the gate (assuming single-sided contact).


$$\overline{v_{Rg}^2} = \underbrace{4kT r_p \Delta f}_{\text{gate resistance thermal noise}} + \underbrace{4kT \delta r_g \Delta f}_{\text{induced gate noise}}$$

$$r_p = \frac{R_s}{3n^2} \frac{W}{L}$$

$$r_g = \frac{1}{5g_{do}}$$

$$\overline{i_d^2} = \underbrace{4kT \gamma g_{d0} \Delta f}_{\text{thermal noise}} + \underbrace{\frac{K}{f} \frac{g_m^2}{WLC_{ox}^2} \Delta f}_{\text{flicker noise}}$$
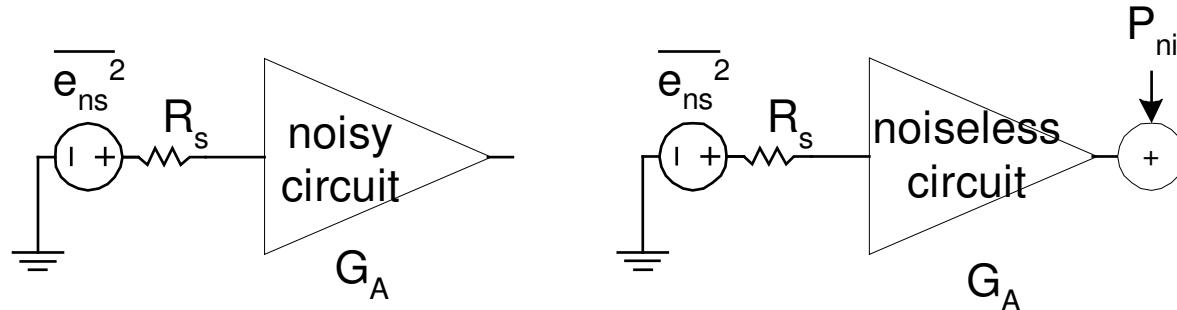
# Metrics for noise in electronic circuits



Noise factor (F);  
evaluated at 290K  
by convention

$$F = \frac{\text{Total output noise}}{\text{Total output noise due to the source}}$$

$$F = \frac{kTBG_A + P_{ni}}{kTBG_A} = 1 + \frac{P_{ni}}{kTBG_A} \geq 1$$

Noise figure (NF)

$$NF = 10 \log(F)$$

Noise temperature  
( $T_N$ )


$$F = 1 + \frac{T_N}{T_{ref}}$$

# Noise figure

---


- Noise figures of 2-3dB are generally considered very good.
  - Noise figure less than 1dB is outstanding.
  - Noise *temperature* is preferred over noise figure when:
    - Noise figure is close to 0dB (noise temperature provides higher resolution).
    - Describing the performance of cascaded amplifiers (the math is simpler, as we'll see).
-

# NF and cascaded amplifiers

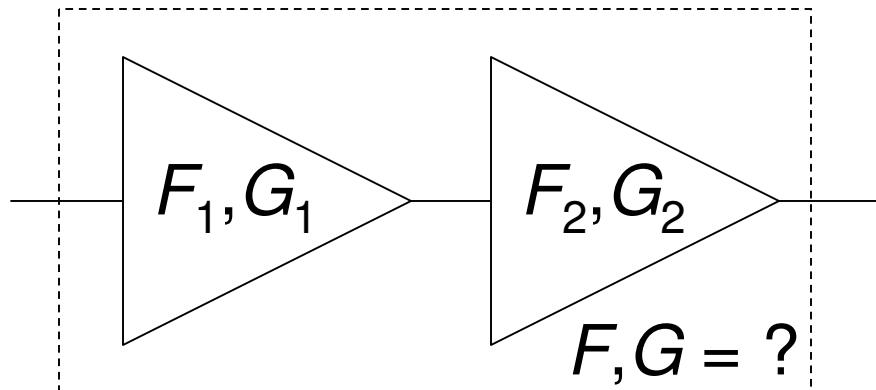

- Assume that each input matches the output impedance of the preceding stage.
- What are the gain and noise figure of the overall system?
  - $G = G_1 G_2$  (that's the easy one)

# NF calculation in cascaded amplifiers

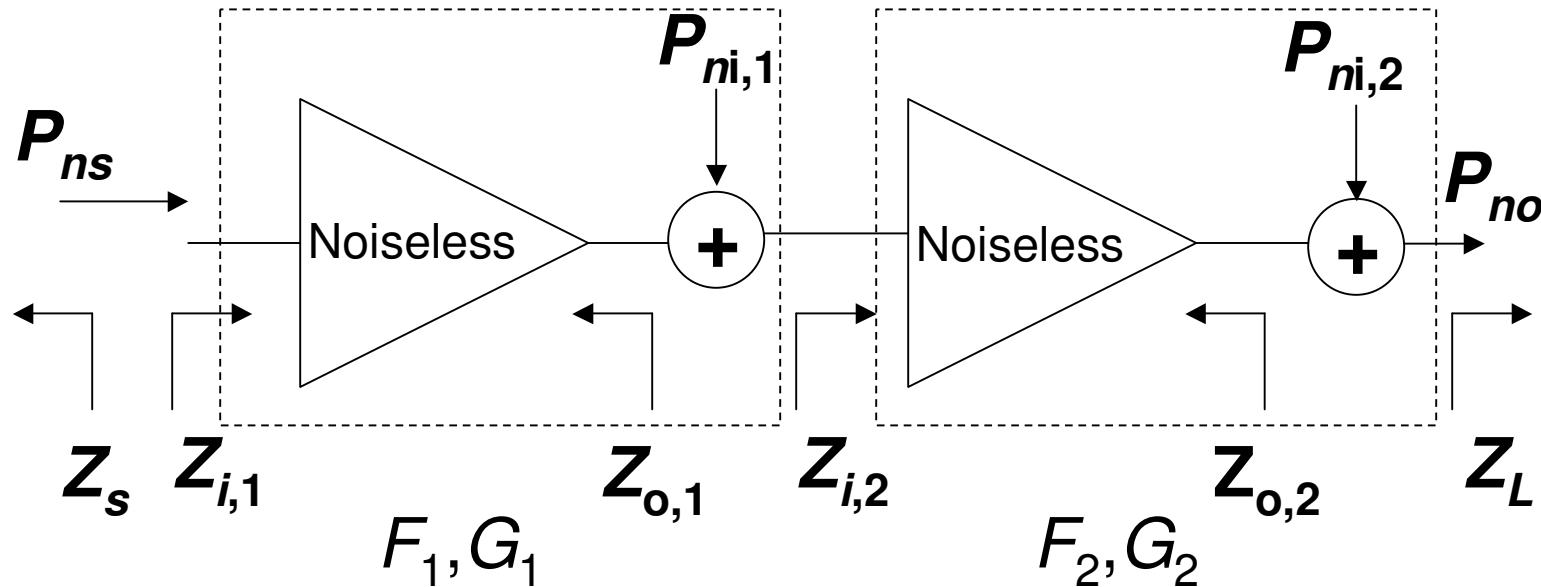

- Assumption is that all stages are power matched:

$$Z_s = Z_{i,1}^*$$

$$Z_{o,1} = Z_{i,2}^*$$

$$Z_{o,2} = Z_L^*$$

# NF and cascaded amplifiers (general case)


- It can be shown that (Friis' equation):

$$F = 1 + (F_1 - 1) + \frac{(F_2 - 1)}{G_1} + \frac{(F_3 - 1)}{G_1 G_2} + \dots$$

- If we use noise temperature then the expression is simpler:

$$T_N = T_{N1} + \frac{T_{N2}}{G_1} + \frac{T_{N3}}{G_1 G_2} + \dots$$

# NF (cascade example)

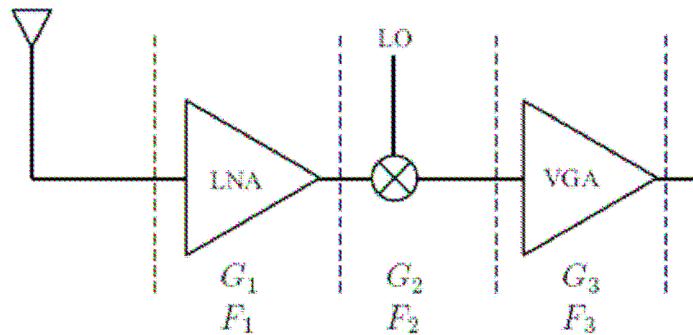


- The LNA has  $G_1=20\text{dB}$  with  $\text{NF}=2\text{dB}$ . The mixer has a conversion gain of  $G_2=10\text{dB}$  and  $\text{NF}=12\text{dB}$ . The VGA has max gain of  $60\text{dB}$  and  $\text{NF}=20\text{dB}$ .
- As long as the stages are impedance-matched we can apply the cascade formula, even though the circuits operate at different frequencies. Thus,

$$NF = 10 \log(1.58 + \frac{15.85 - 1}{100} + \frac{100 - 1}{100 * 10}) = 2.63\text{dB}$$
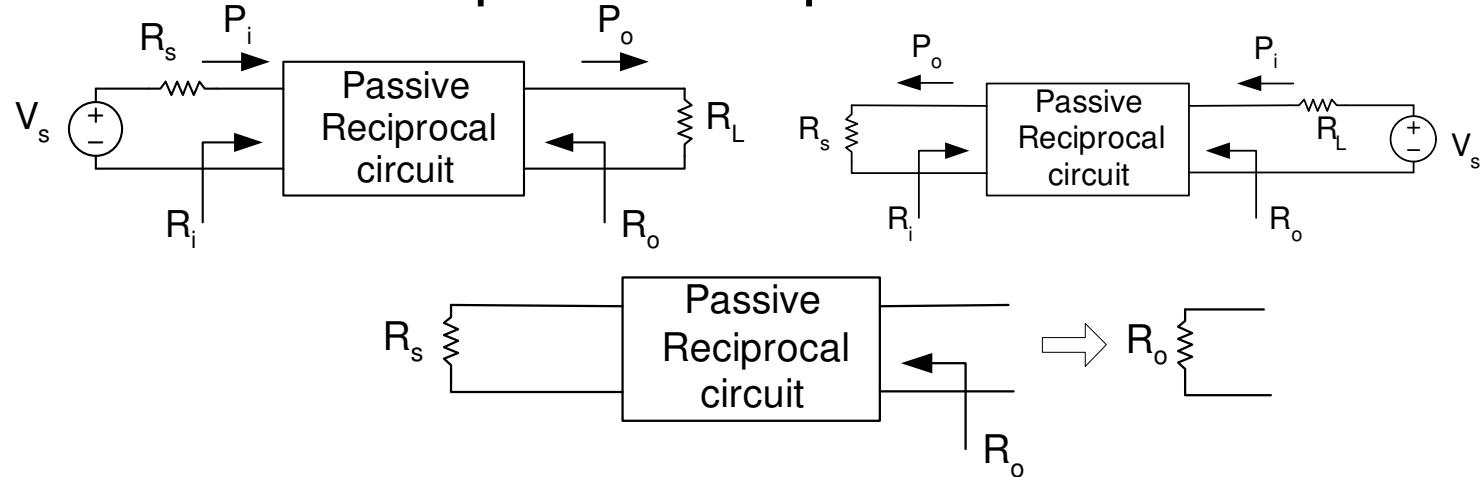
# Lossy reciprocal passive circuits

- Consider a reciprocal LTI passive circuit




- Under an impedance-matched condition we have:

$$R_i = R_s \quad L = \frac{P_o}{P_i} < 1 \quad ; \text{ independent of direction}$$
$$R_o = R_L$$

- It can be shown that  $F=1/L$ . “Loss (dissipation) => noise.”

# Receiver NF example

- Consider the front-end of a receiver:

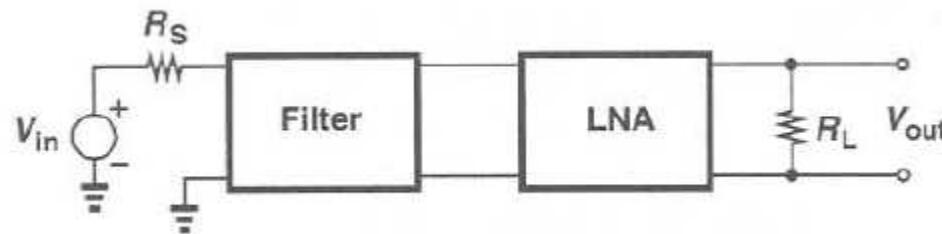

- From the Friis equation we have

$$F = 1 + (1/L - 1) + (F_{LNA} - 1)/L = F_{LNA}/L$$

$$NF = 10 \log(1/L) + NF_{LNA}$$

- Therefore the loss of the front-end elements degrades the receiver noise figure by precisely that loss, dB for dB.
- Example: If the filter has a 2dB loss the front-end NF will be  $2\text{dB} + NF_{LNA}$

# Receiver sensitivity

- Sensitivity is the minimum signal that can be detected with a certain error probability.
- The signal-to-noise-ratio (SNR) is used to calculate the bit-error-rate (BER).
- If the total noise power is  $N_i$ , we have:

$$S_{\min} (\text{dB}) = N_i (\text{dB}) + SNR_{\min} (\text{dB})$$

# Receiver sensitivity example

- Assume that the receiver requires SNR=10dB to guarantee a BER of 0.1%.
- If NF=10dB and  $B=10\text{MHz}$ , then

$$N_i = P_{ns} + P_{ni} = P_{ns} + P_{ns}(F - 1) = P_{ns}F = FkTB$$

$$N_i(\text{dBm}) = \underbrace{-174}_{\substack{\text{thermal noise} \\ \text{from source}}} + \underbrace{10\log(10^7)}_B + \underbrace{10}_{NF} = -94\text{dBm}$$

$$S_{\min} = N_i(\text{dBm}) + \underbrace{10}_{SNR} = -84\text{dBm}$$

- What should we do if we need -90dBm sensitivity?

# Receiver sensitivity example (cont.)

- There is only one solution: Reduce noise!
  - Reducing the bandwidth by 6dB ( $B_{\text{new}}=2.5\text{MHz}$ ) would reduce noise, but the bandwidth is often dictated by other constraints.
  - Reducing the noise figure by 6dB is the only practical option.
- Notice that a 6dB increase in sensitivity corresponds to needing a factor of four lower signal power.
- If the received signal strength is proportional to  $1/d^2$  (where  $d=\text{distance}$ ), the range doubles.
- Looking at it differently: To have the same range without improving NF the transmitter would have to provide 4x as much power. So, NF is important.

# Receiver sensitivity example (cont.)

- To increase the sensitivity by 6dB we should reduce the NF by the same amount, from 10dB to 4dB.
- We are given the option of adding an amplifier in front of the receiver.
- Obviously the amplifier NF must be less than 4dB (why?). If the amp's NF=3dB, then what should be the minimum available gain of the amplifier?

$$F = \underbrace{10^{(4/10)}}_{2.51} = \underbrace{10^{(3/10)}}_2 + \frac{10-1}{G_{\min}} \Rightarrow G_{\min} = \frac{9}{2.51 - 2} = 17.65 = 12.5 \text{dB}$$

---

# Linearity, Time-Variation, Phase Modulation and Oscillator Phase Noise

---

# Preliminaries (to refresh dormant neurons)


---

- A system is linear if superposition holds.
    - Scaling of a single input is included.
    - Impulse response yields sufficient information to deduce the response to an arbitrary input.
    - All real systems can be driven into nonlinearity.
      - Linearity only holds over limited range.
  - A system is time-invariant if time-shifting an input *only* time-shifts the output.
  - If a system is LTI, then excitation at  $f$  produces response only at  $f$ .
-


# Preliminaries

- If a system is LTV, excitation at  $f$  can produce response at other than  $f$ .
  - Superposition holds, so impulse response still tells us about response to any other input.
- If a system is nonlinear, excitation at  $f$  can also produce response at other than  $f$ .
  - Superposition doesn't hold; impulse response cannot be used to infer response to arbitrary excitations.

# Oscillator as input-output system


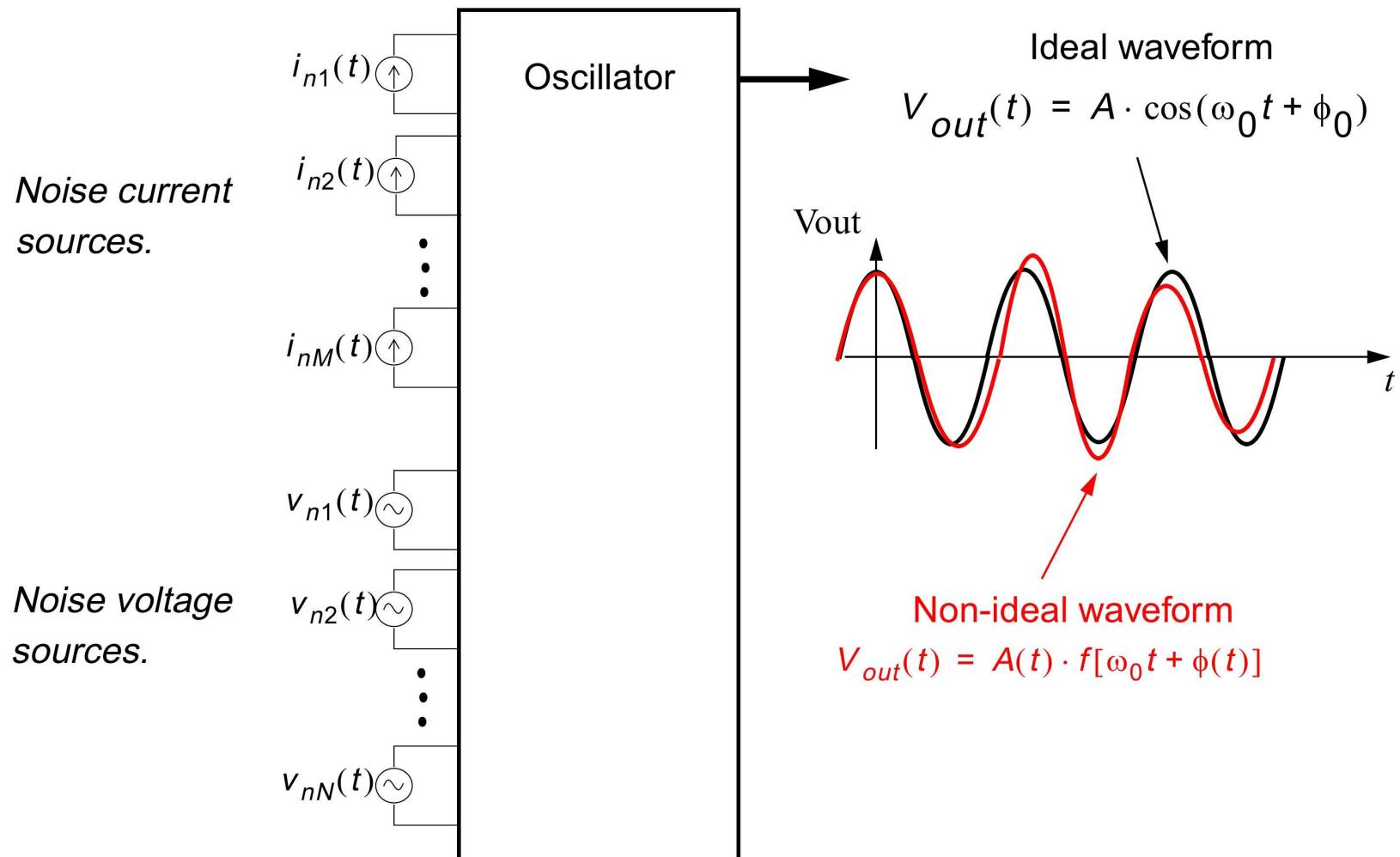


# Phase noise effects in RF systems

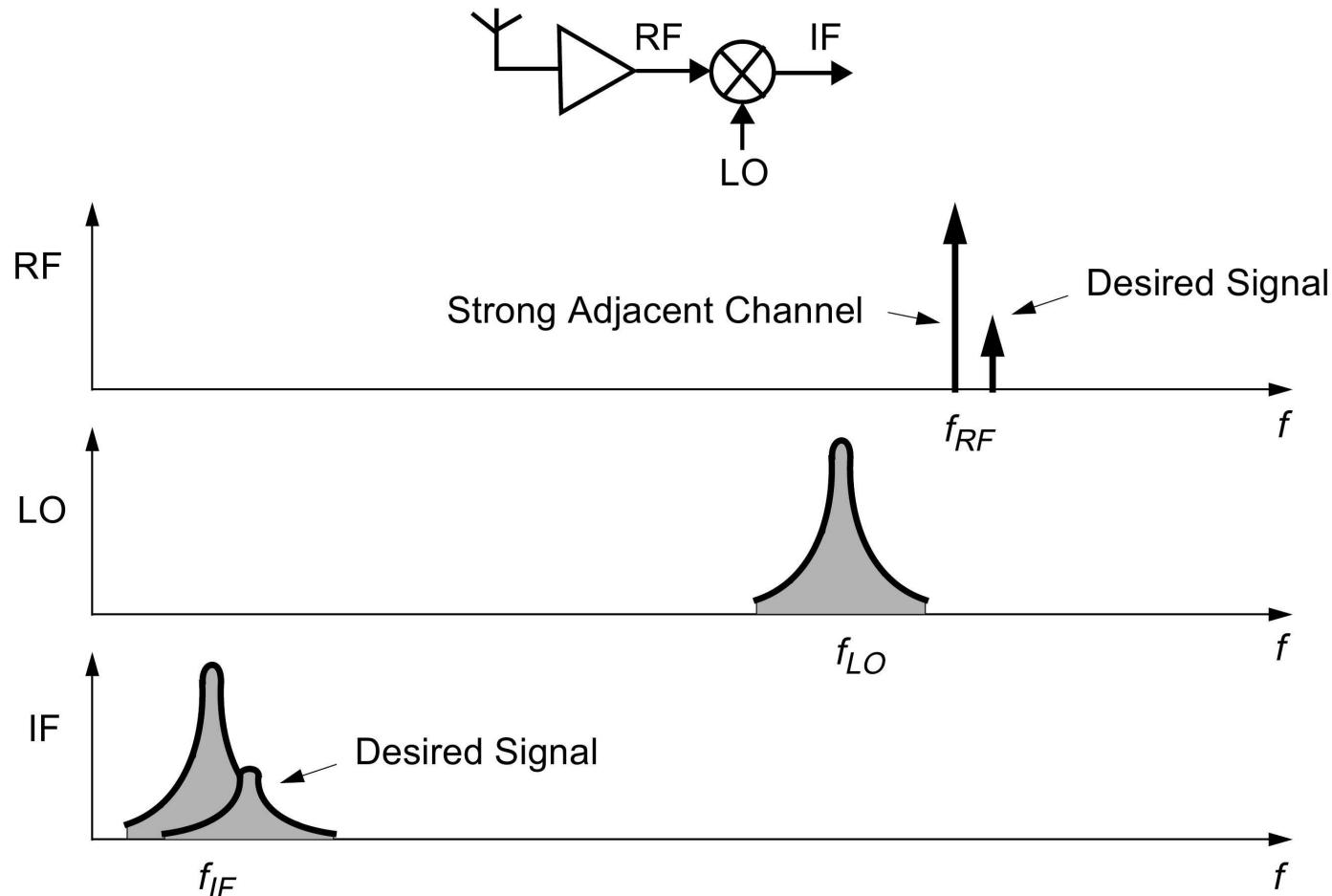


*Phase noise buries desired signal in skirts of interferer*

# Units of phase noise

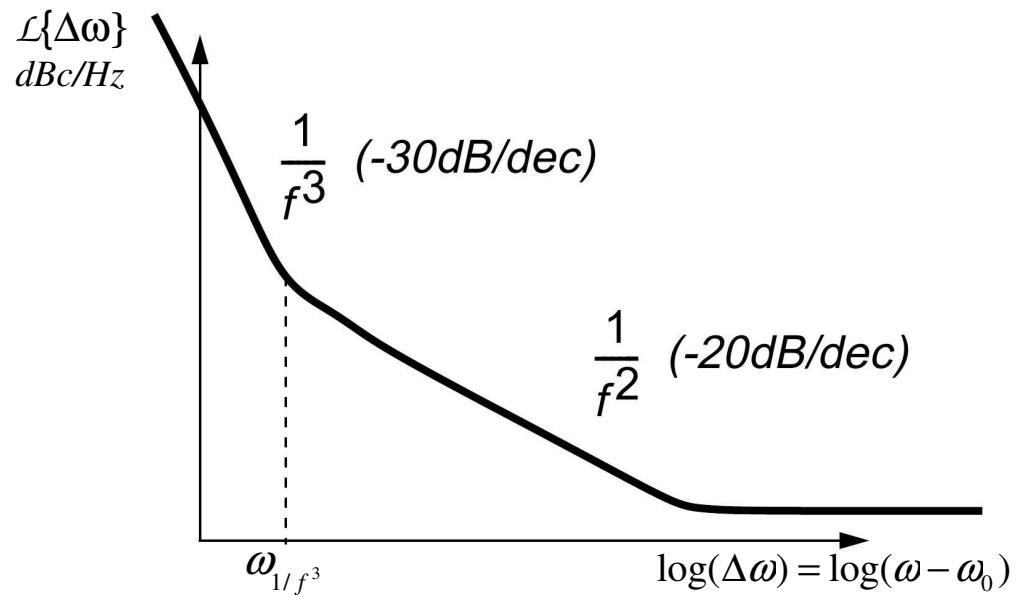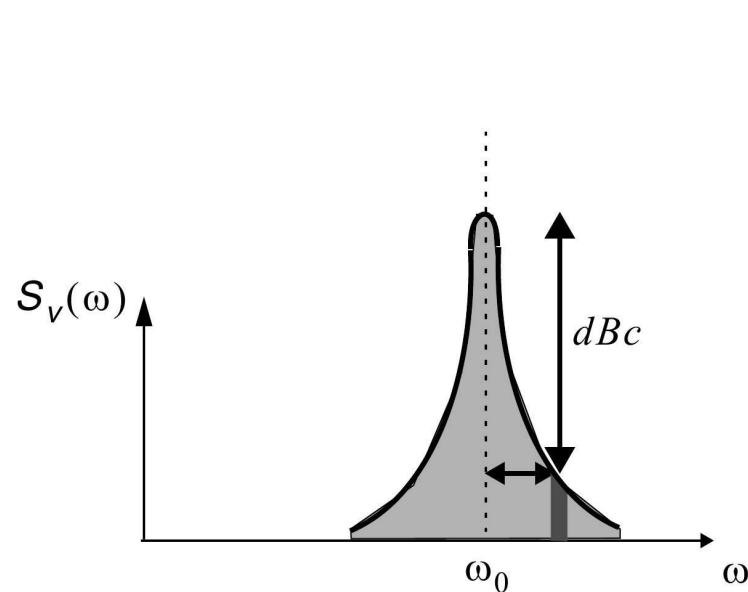


**Phase noise units: dB below carrier, in a 1Hz bandwidth.**

# Substrate and supply noise

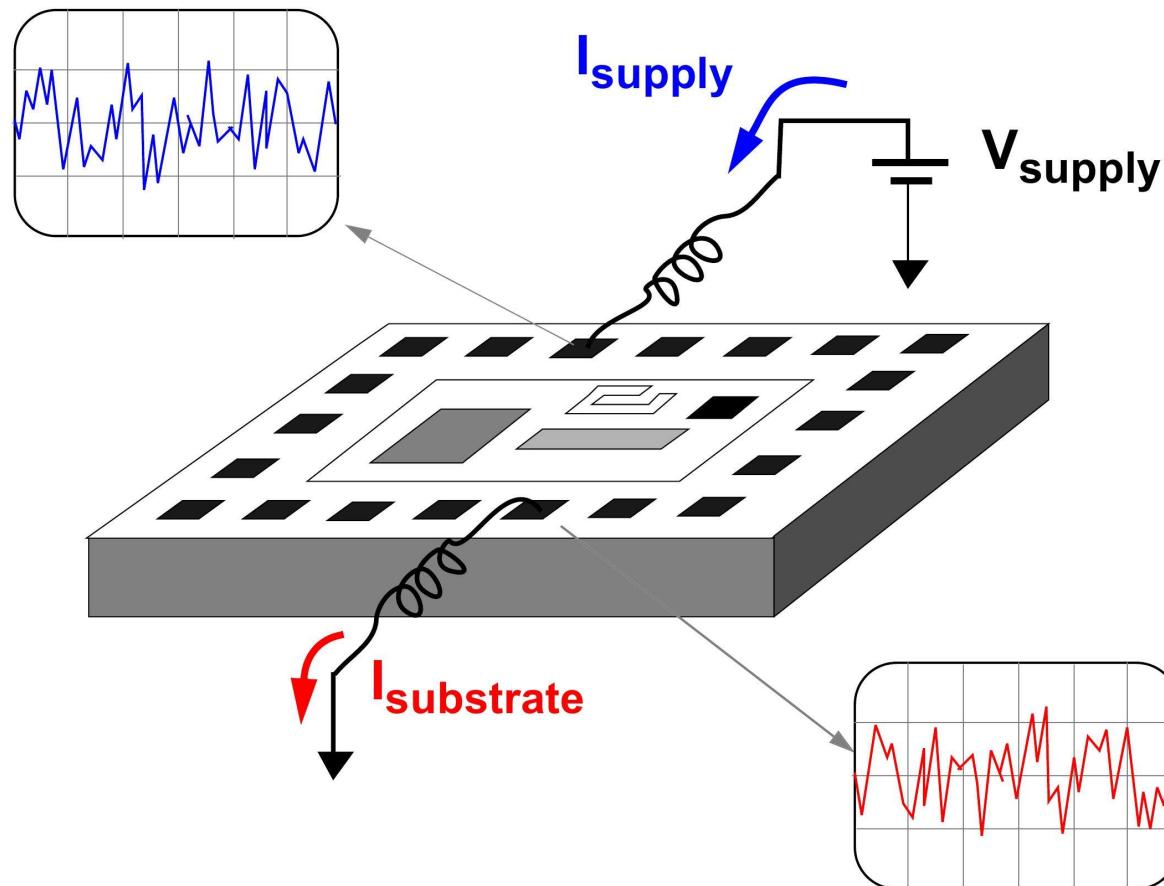
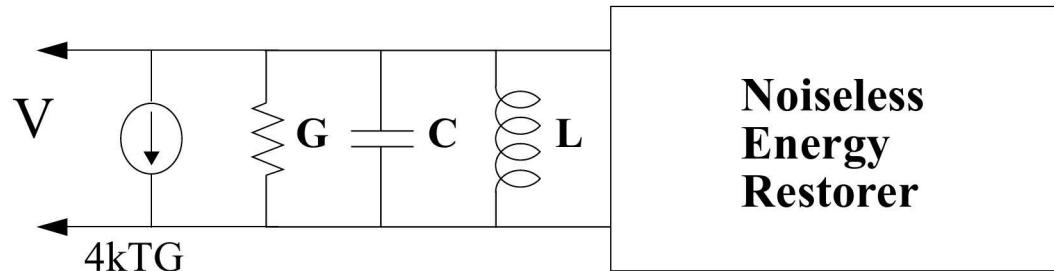
# Phase noise: General considerations

- Idealize oscillator as  $RLC$  + negative resistance:




- Can show that the noise-to-signal ratio is

$$\frac{N}{S} = \frac{\overline{V_n^2}}{V_{sig}^2} = \frac{kT}{E_{stored}} = \frac{\omega kT}{QP_{diss}}.$$

- Negative- $R$  must cancel tank loss in steady state.
- Noise current then sees pure  $LC$  impedance.
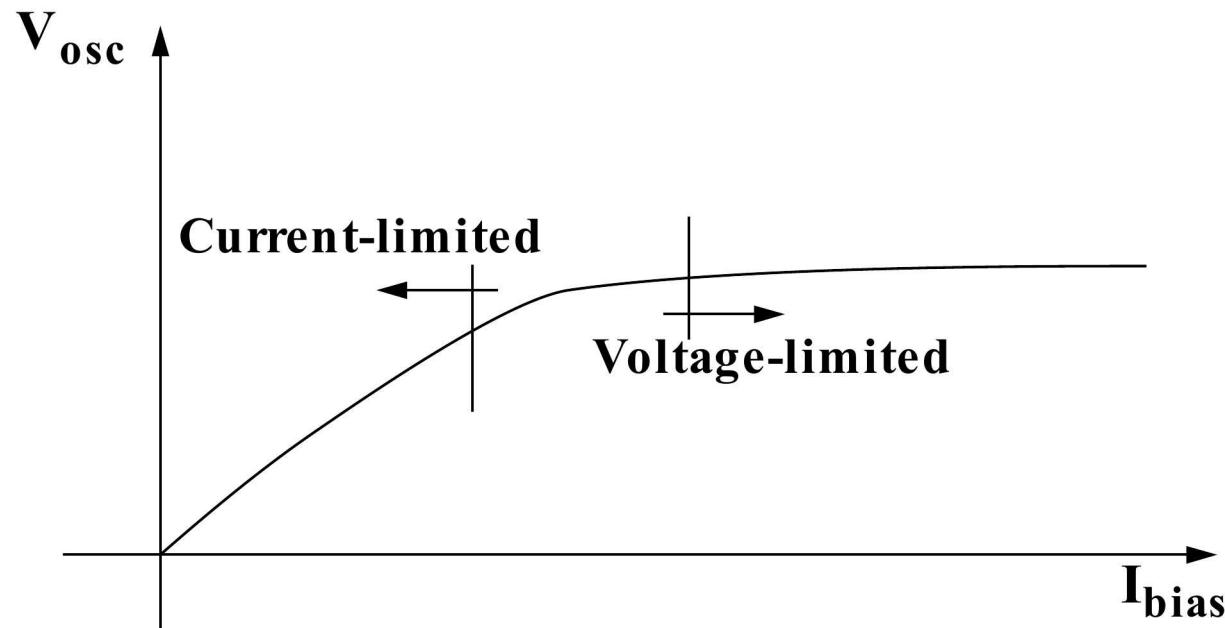
# Phase noise: General considerations

- Practical oscillators operate in one of two regimes:
  - *Current-limited*, where oscillation amplitude is proportional to  $I_{bias} R_{tank}$ .
  - *Voltage-limited*, where oscillation amplitude is independent of  $I_{bias}$ .



# General considerations

---

- In the voltage-limited regime, increases in  $I_{bias}$  do not increase carrier power.
  - Additional bias current only increases noise and dissipation, so CNR degrades.
- In the current-limited regime, increases in  $I_{bias}$  increase signal power faster than noise power.
  - CNR increases until incipient voltage-limiting occurs.
  - Best CNR occurs near boundary between limiting regimes.

# Oscillator phase noise

- The expression for CNR reveals important optimization objectives:
  - $V_{carrier} \propto I_{bias} R_{tank} \Rightarrow P_{carrier} \propto (I_{bias})^2 R_{tank}$  in the current-limited regime.
  - $P_{noise} = kT/C = kT\omega^2 L$ , if dominated by tank loss.
  - So  $N/C \propto kT\omega^2 L/(I_{bias})^2 R_{tank}$  to an approximation.
- Generally want to *minimize*  $L/R$  to optimize for a given frequency and power consumption.
  - This contradicts much published advice to *maximize*  $L$ .
  - $N/C$  is important, but so is detailed spectrum.

# Naive LTI model

- Assuming all noise comes from tank loss, PSD of tank voltage is approximately

$$\frac{\overline{v_n^2}}{\Delta f} = \frac{\overline{i_n^2}}{\Delta f} |Z|^2 = 4kTG \left( \frac{1}{G} \frac{\omega_0}{2Q\Delta\omega} \right)^2 = 4kTR \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2$$


- Noise power splits evenly between phase and amplitude domains. Then

$$\mathcal{L}(\Delta\omega) = 10 \log \left[ \frac{\overline{v_n^2} / \Delta f}{v_{sig}^2} \right] = 10 \log \left[ \frac{2kT}{P_{sig}} \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2 \right]$$

- Funny units: dBc/Hz at a certain offset freq., e.g., “-110dBc/Hz@600kHz offset from 1.8GHz.”
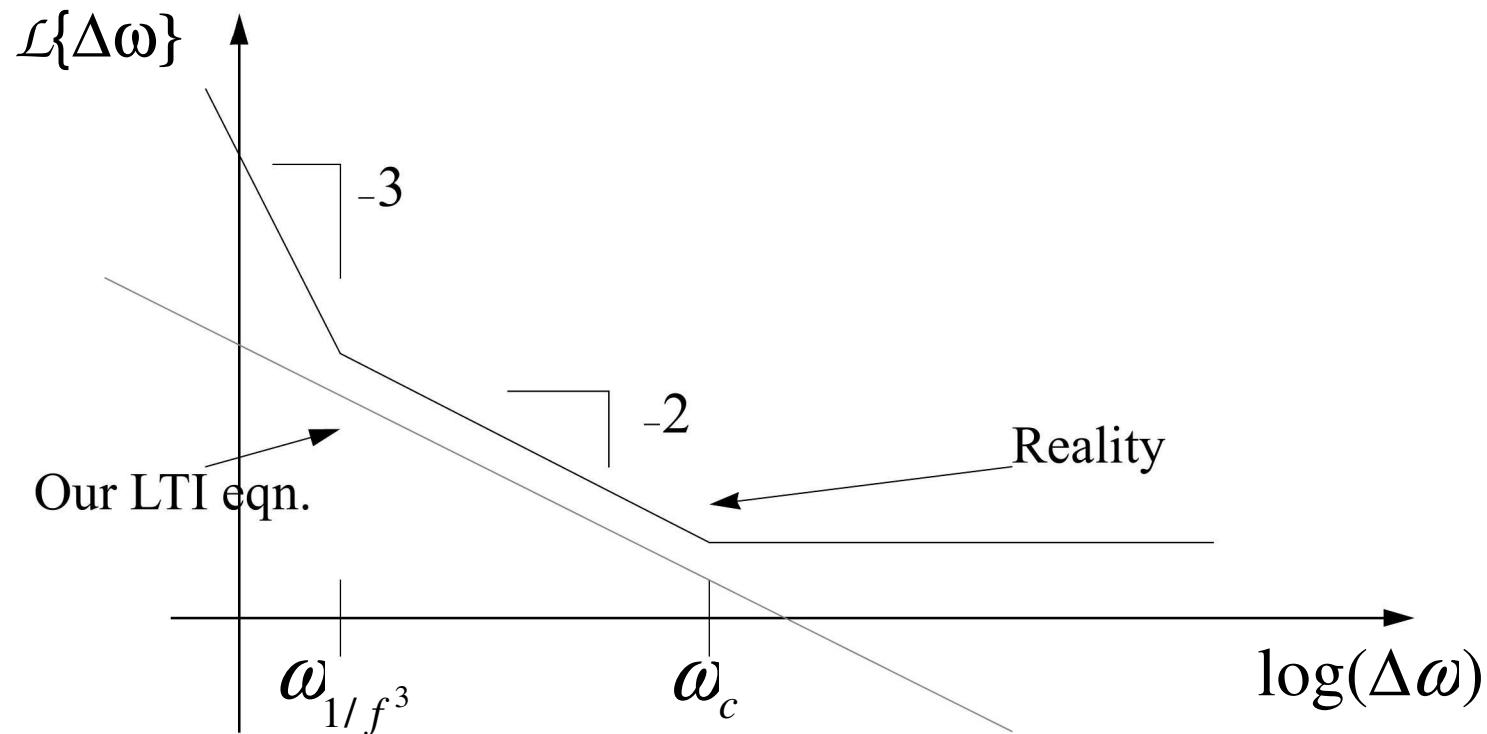
# Naive LTI model vs. reality

- Previous expression doesn't describe real PN well:






# Leeson model

- Leeson provided quasi-empirical fix to remove discrepancies:


$$\mathcal{L}(\Delta\omega) = 10 \log \left[ \frac{2FkT}{P_{sig}} \left\{ 1 + \left( \frac{\omega_0}{2Q\Delta\omega} \right)^2 \right\} \left( 1 + \frac{\Delta\omega_{1/f^3}}{|\Delta\omega|} \right) \right]$$

- $F$  accounts for excess noise at all offsets.
- $\Delta\omega_{1/f^3}$  accounts for  $1/f^3$  region near carrier.
- First additive factor of 1 accounts for noise floor.
- These factors cannot be determined *a priori*; they are *a posteriori* fitting parameters.
- Need to revisit assumption that oscillators are LTI.

# Are oscillators LTI?

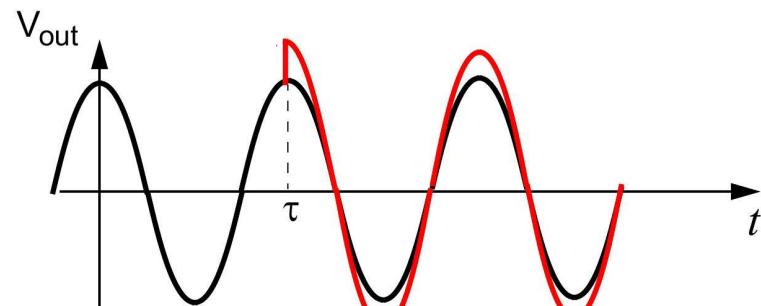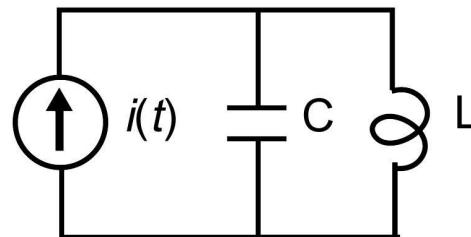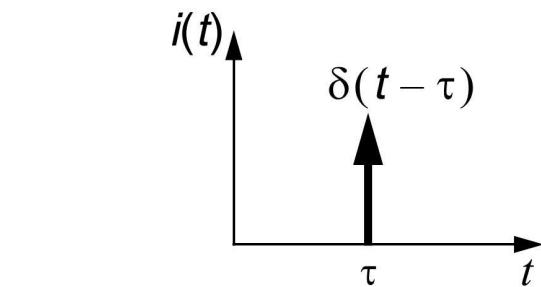



**Impulse injected at peak**

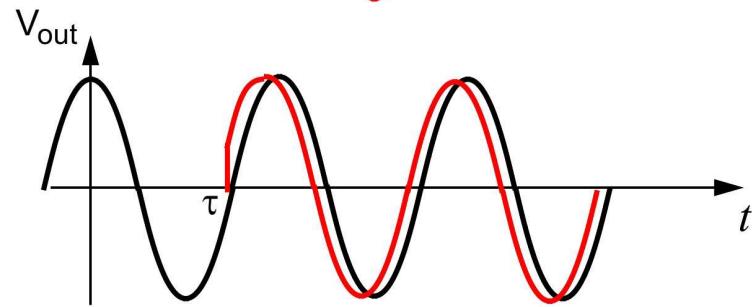

**Impulse injected at zero crossing**


***Even for an ideal LC, the phase response is time-variant.***
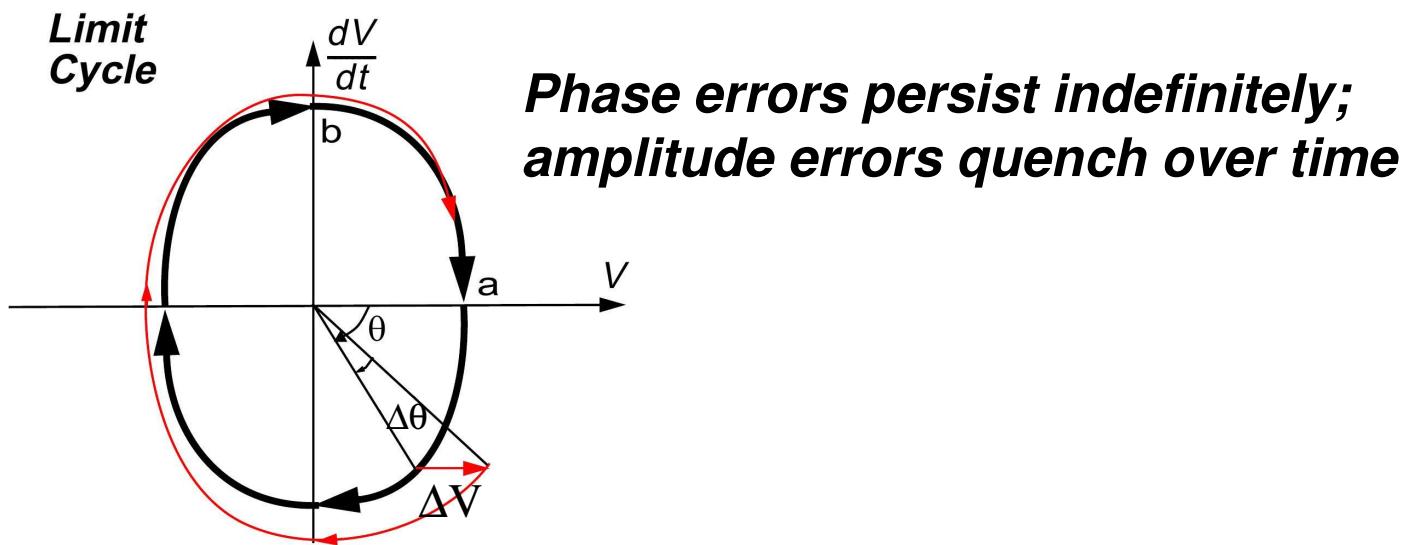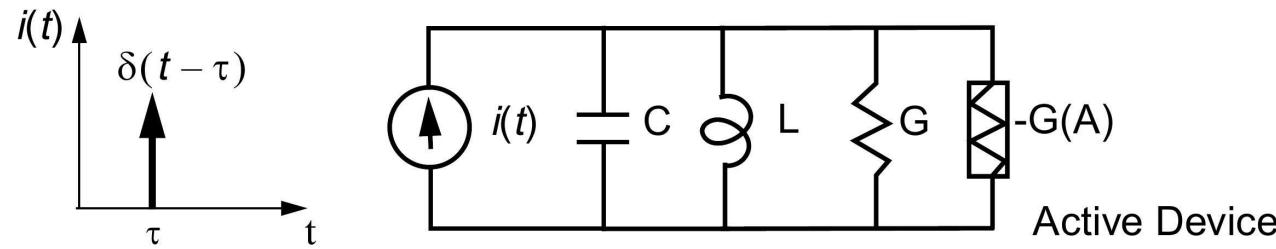
# Amplitude restoration in real oscillators


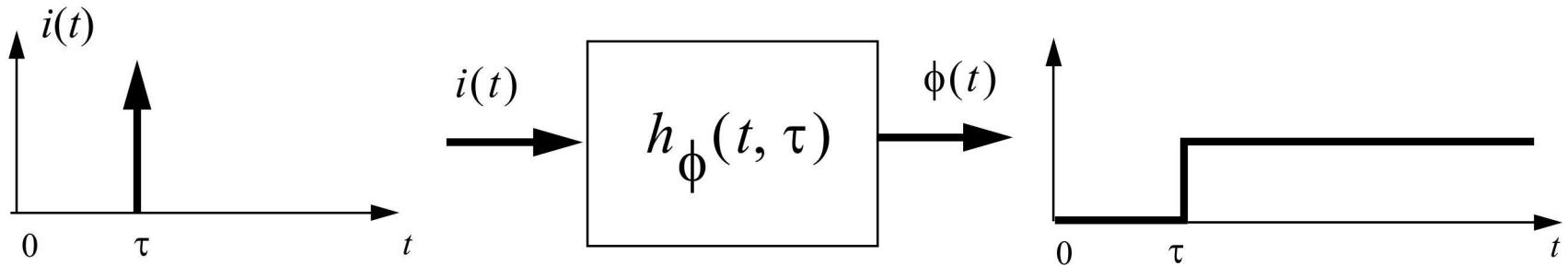
# Phase impulse response

*The phase impulse response of an oscillator is a step:*





*The unit impulse response is:*

$$h_\phi(t, \tau) = \frac{\Gamma(\omega_0 t)}{q_{\max}} u(t - \tau)$$

*$\Gamma(x)$  is a dimensionless function, periodic in  $2\pi$ , describing how much phase change results from impulse at*


$$t = T \frac{x}{2\pi}$$

# Impulse sensitivity function (ISF)

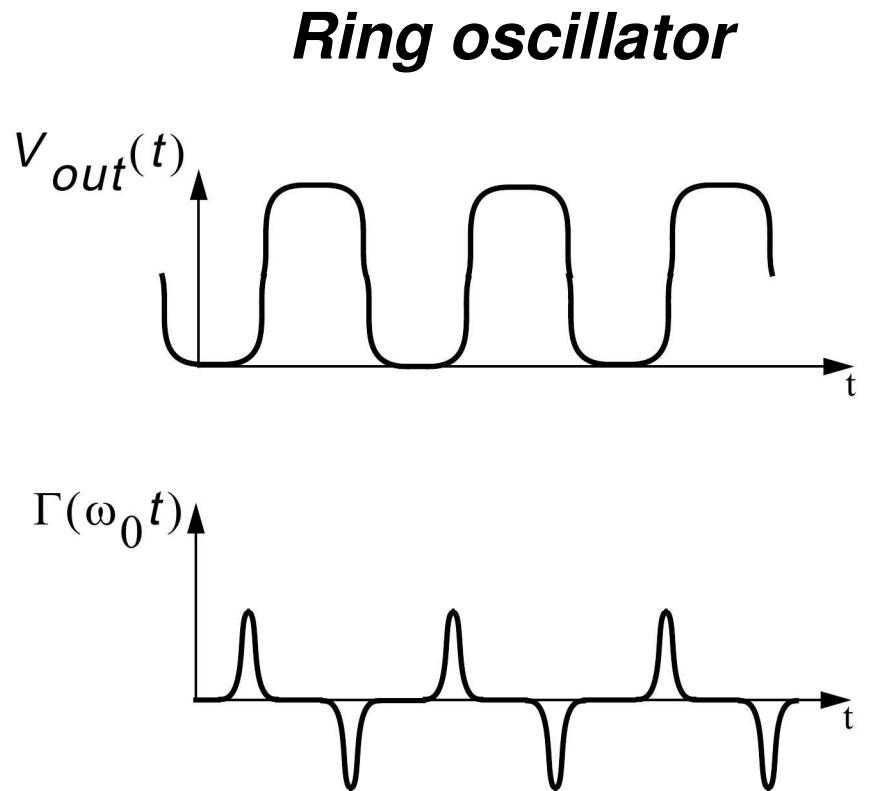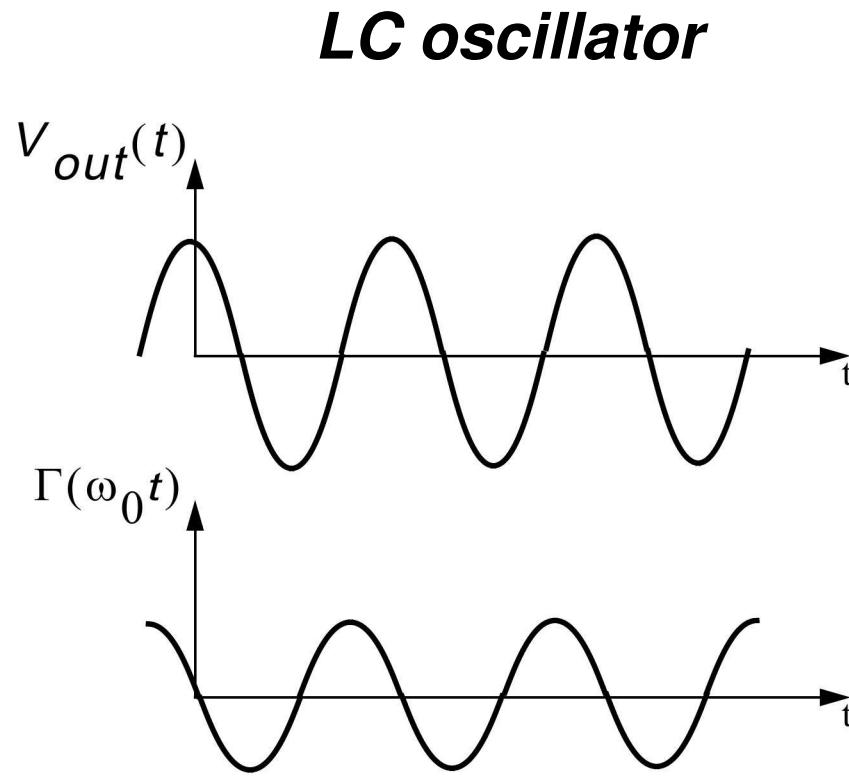

***The ISF quantifies the sensitivity to perturbations at all instants.***


# Phase response to arbitrary inputs

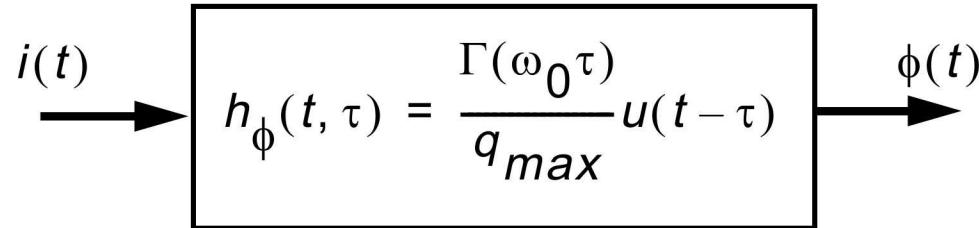


*Use the superposition integral to compute phase response:*

$$\phi(t) = \int_{-\infty}^{\infty} h_\phi(t, \tau) i(\tau) d\tau = \frac{1}{q_{max}} \int_{-\infty}^t \Gamma(\omega_0 t) i(\tau) d\tau$$

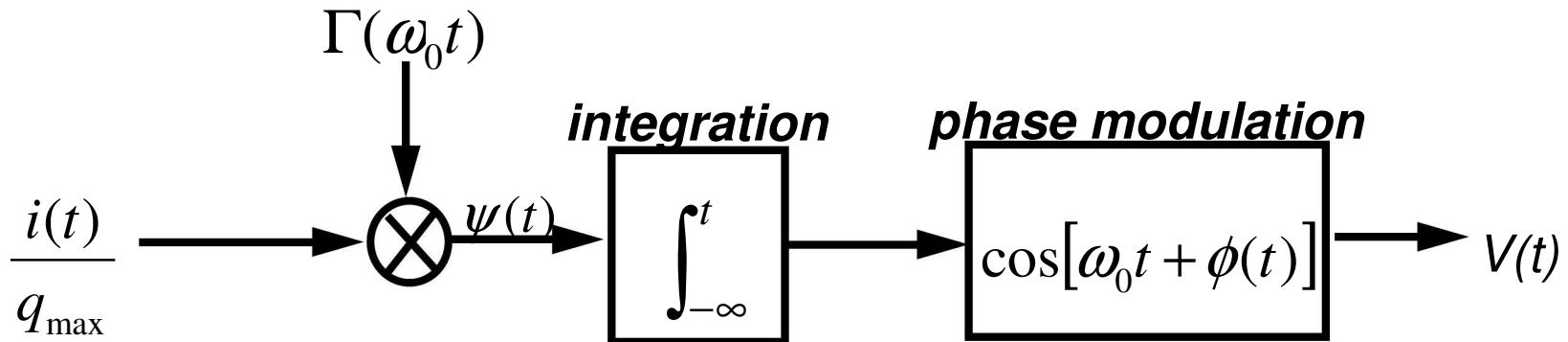*Block diagram representation of superposition integral is:*



# Phase noise due to white noise

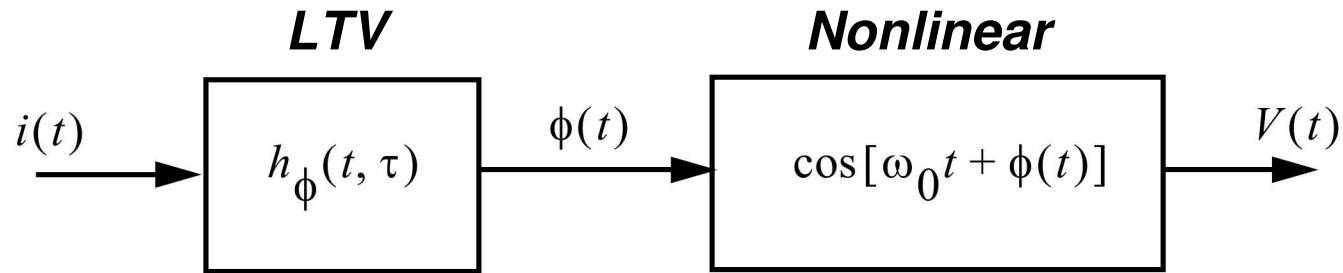

**For a white noise input current of spectral density**  $\frac{\overline{i_n^2}}{\Delta f}$ ,  
**the phase noise is given by**

$$\mathcal{L}(\Delta\omega) = 10 \log \left[ \frac{\Gamma_{rms}^2}{q_{max}^2} \frac{\overline{i_n^2} / \Delta f}{2(\Delta\omega)^2} \right],$$

**where  $\Gamma_{rms}$  is the rms value of the ISF.**


# ISF in greater detail

**ISF is periodic, expressible as a Fourier series:**


$$\Gamma(\omega_0 t) = c_0 + \sum_{n=1}^{\infty} c_n \cos(n\omega_0 t + \theta_n)$$

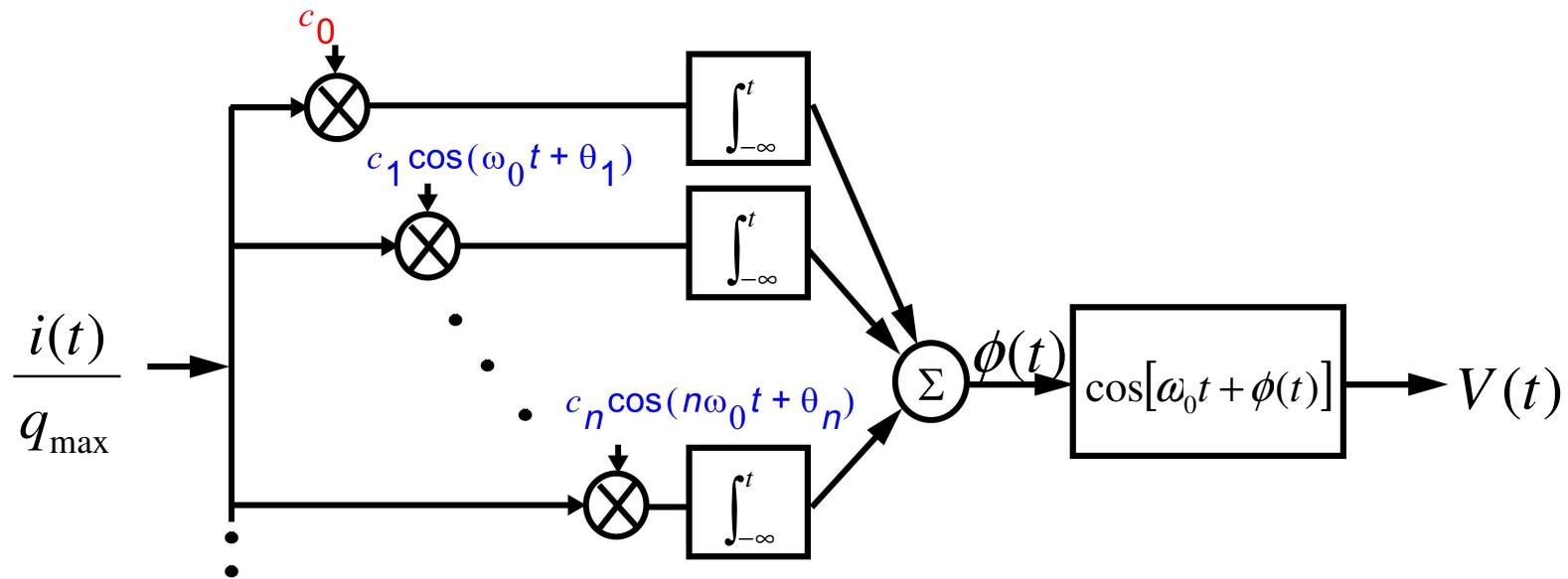**The phase is then as follows:**

$$\phi(t) = \frac{1}{q_{\max}} \left[ c_0 \int_{-\infty}^t i(\tau) d\tau + \sum_{n=1}^{\infty} c_n \int_{-\infty}^t i(\tau) \cos(n\omega_0 \tau) d\tau \right]$$







# Contributions by noise at $n\omega_0$

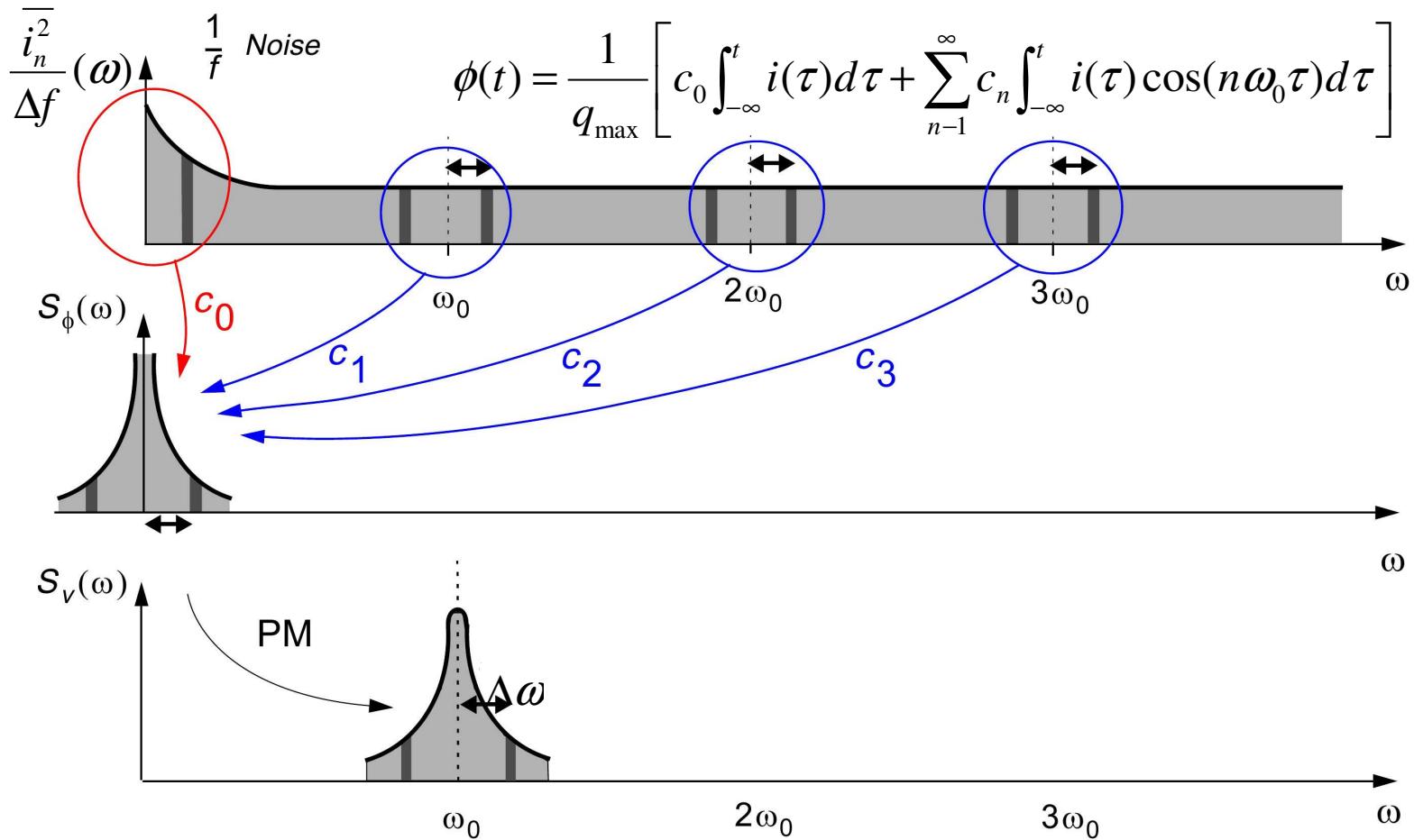
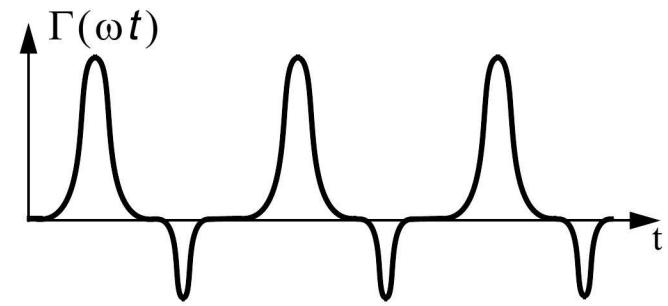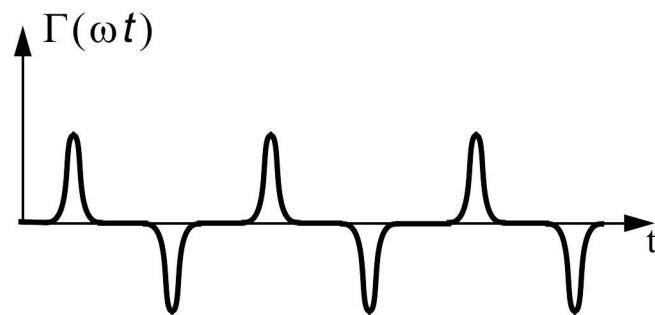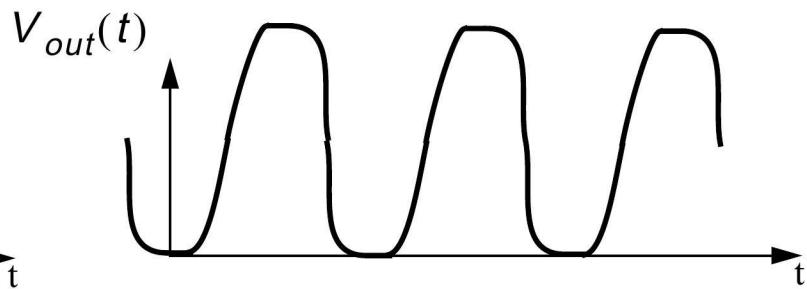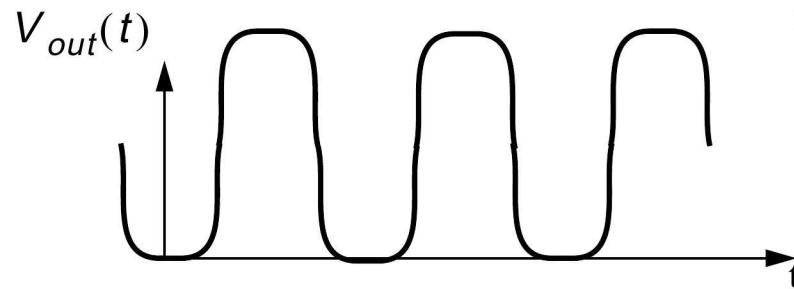
# Symmetry matters


$$c_0 = \frac{1}{2\pi} \int_0^{2\pi} \Gamma(x) dx$$



***The dc value of the ISF is affected by waveform symmetry***

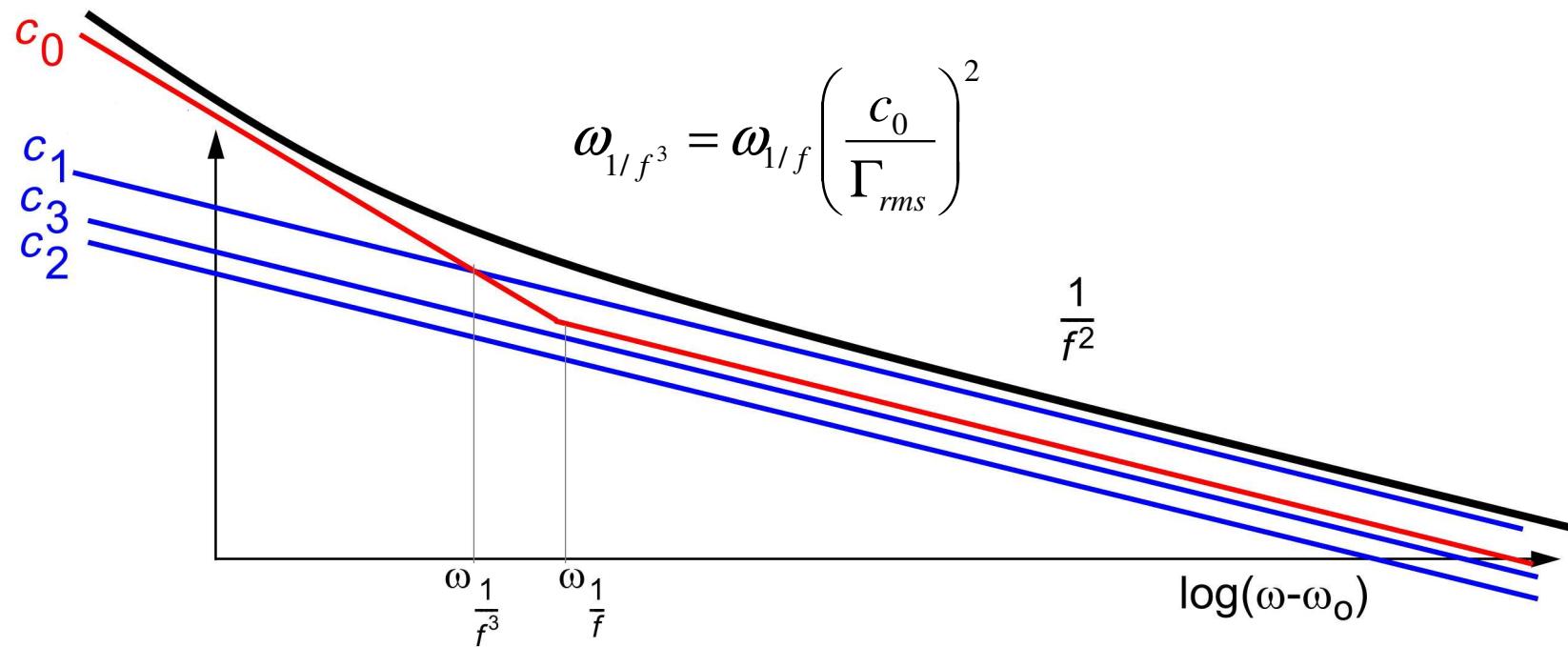
# $1/f^3$ corner of phase noise spectrum

*The  $1/f^3$  phase noise corner is not the same as the  $1/f$  device noise corner.*






*Adjustment of waveform symmetry can control  $1/f$  noise upconversion.*
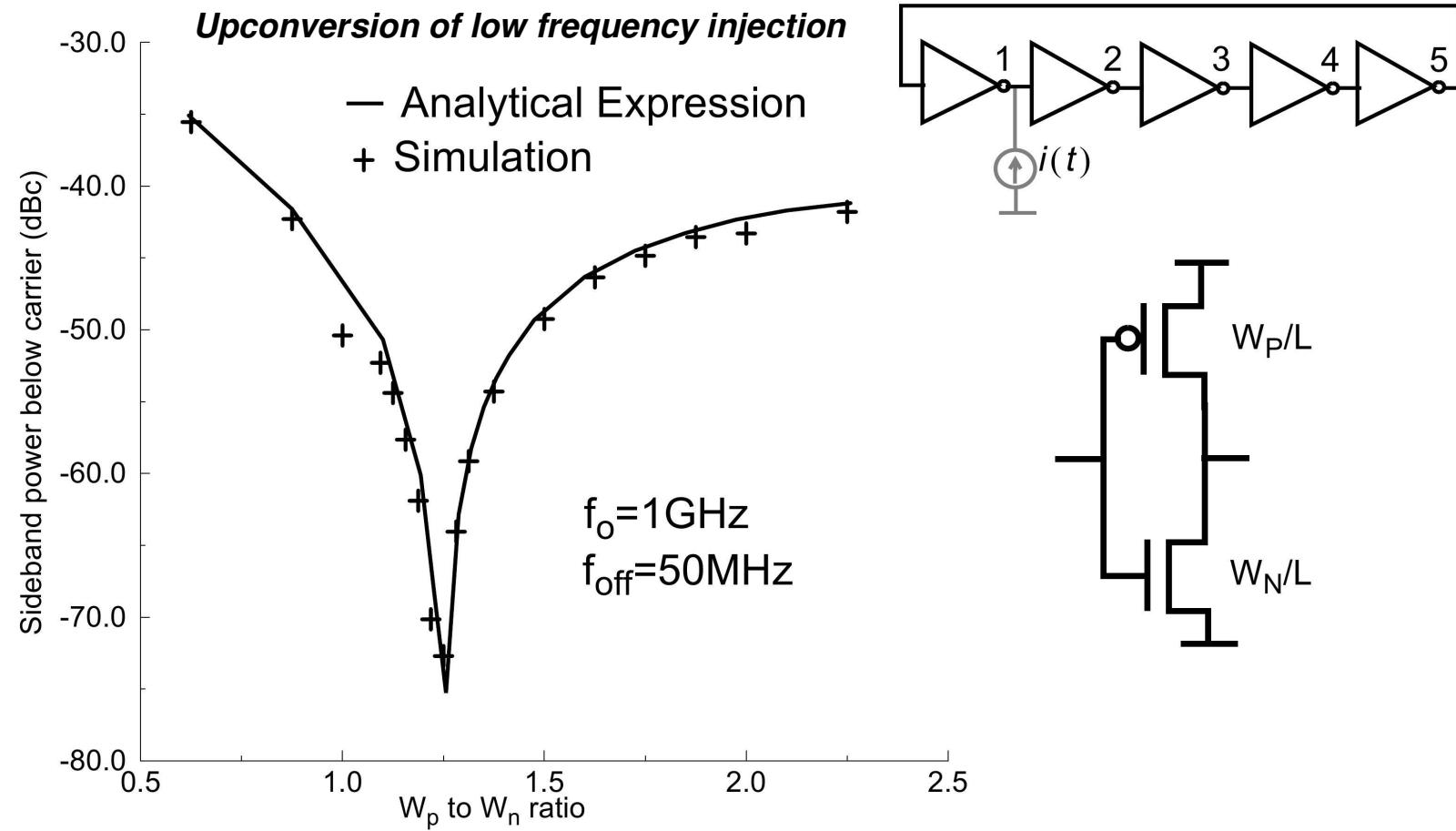
# Exploring the effect of waveform symmetry




# Effect of waveform symmetry

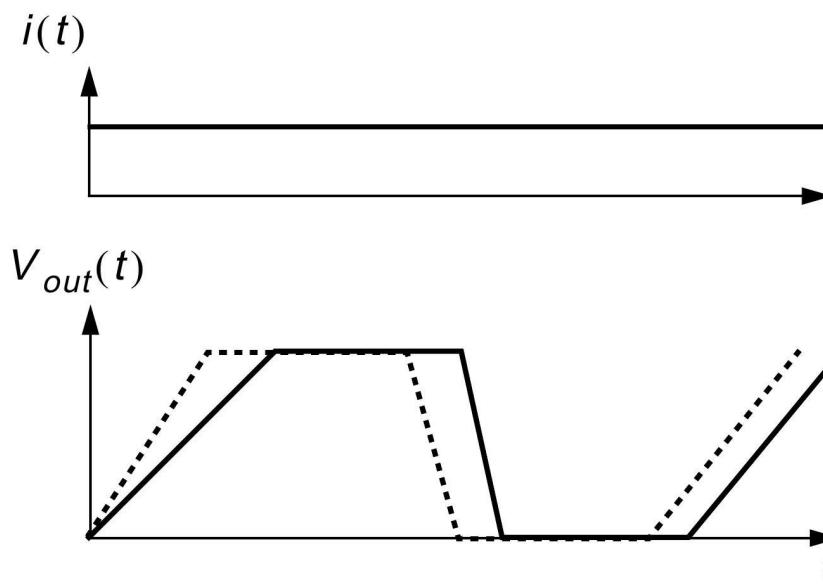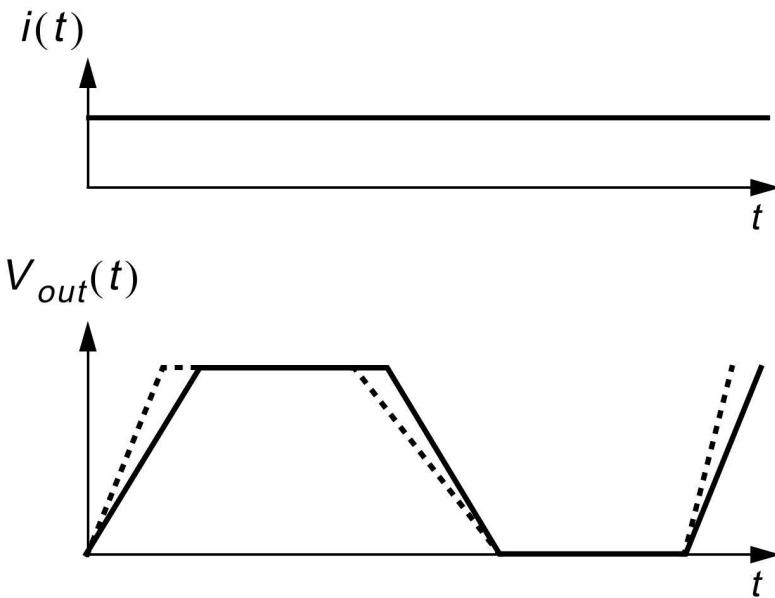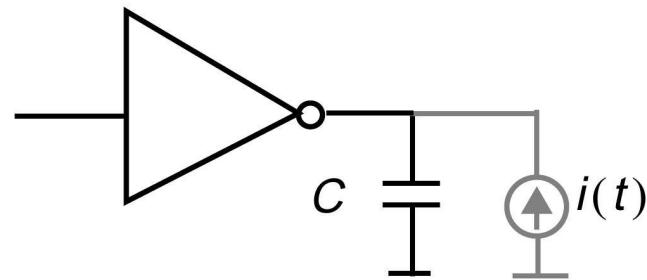


***Low frequency injection shifts the frequency of the asymmetric waveform.***


# Effect of injection at $nf_0$

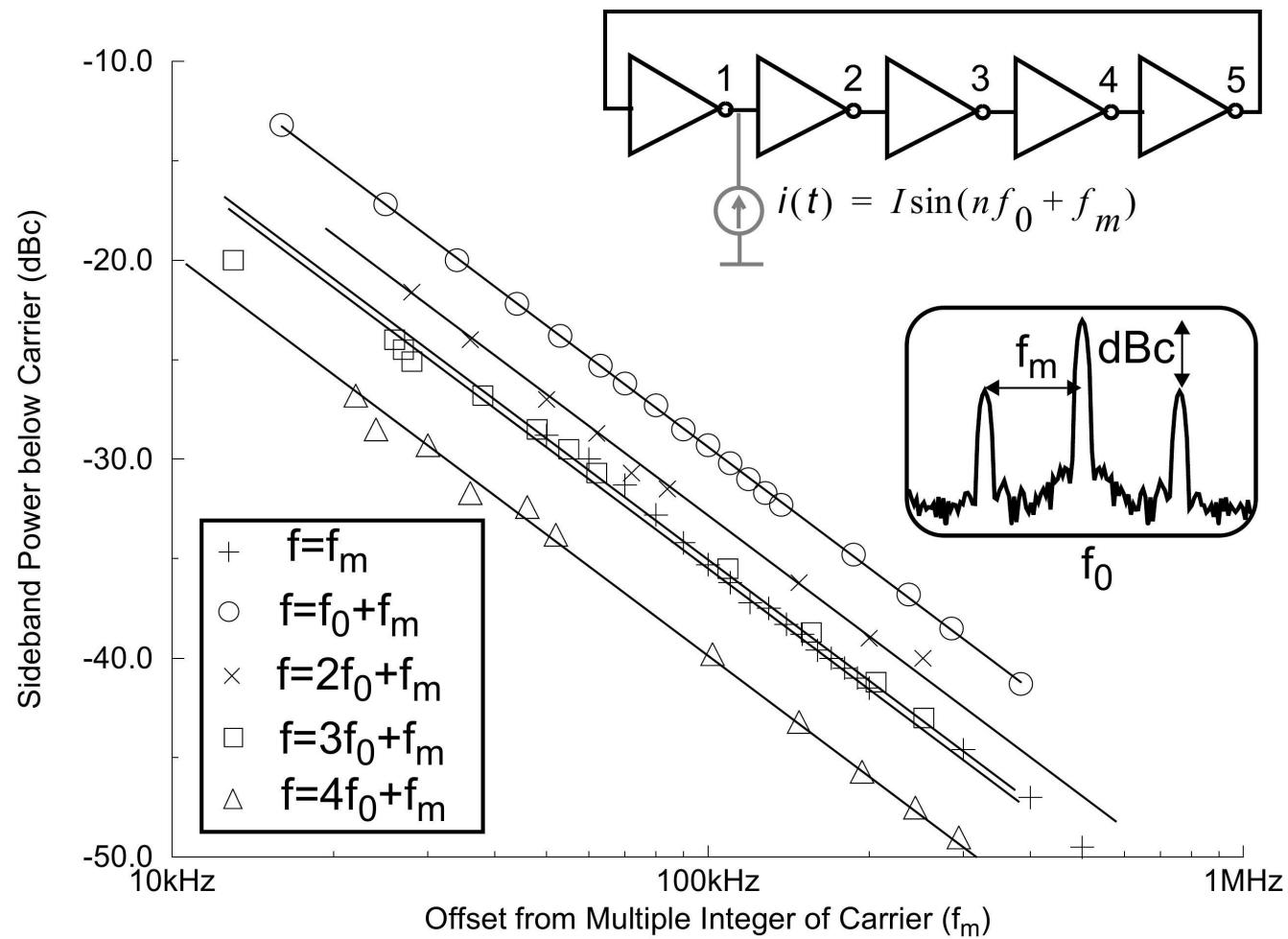



# Sideband power vs. injected current

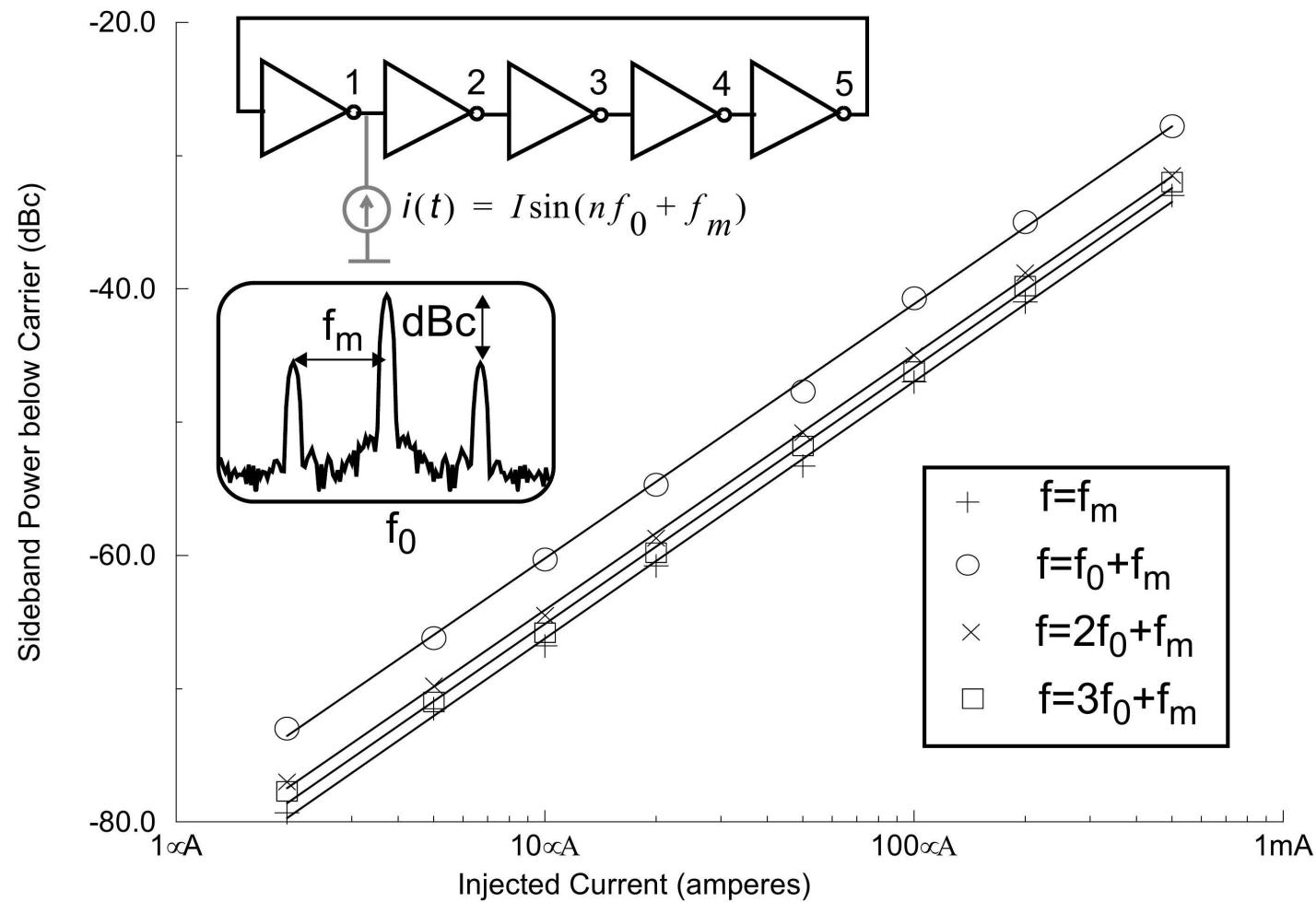

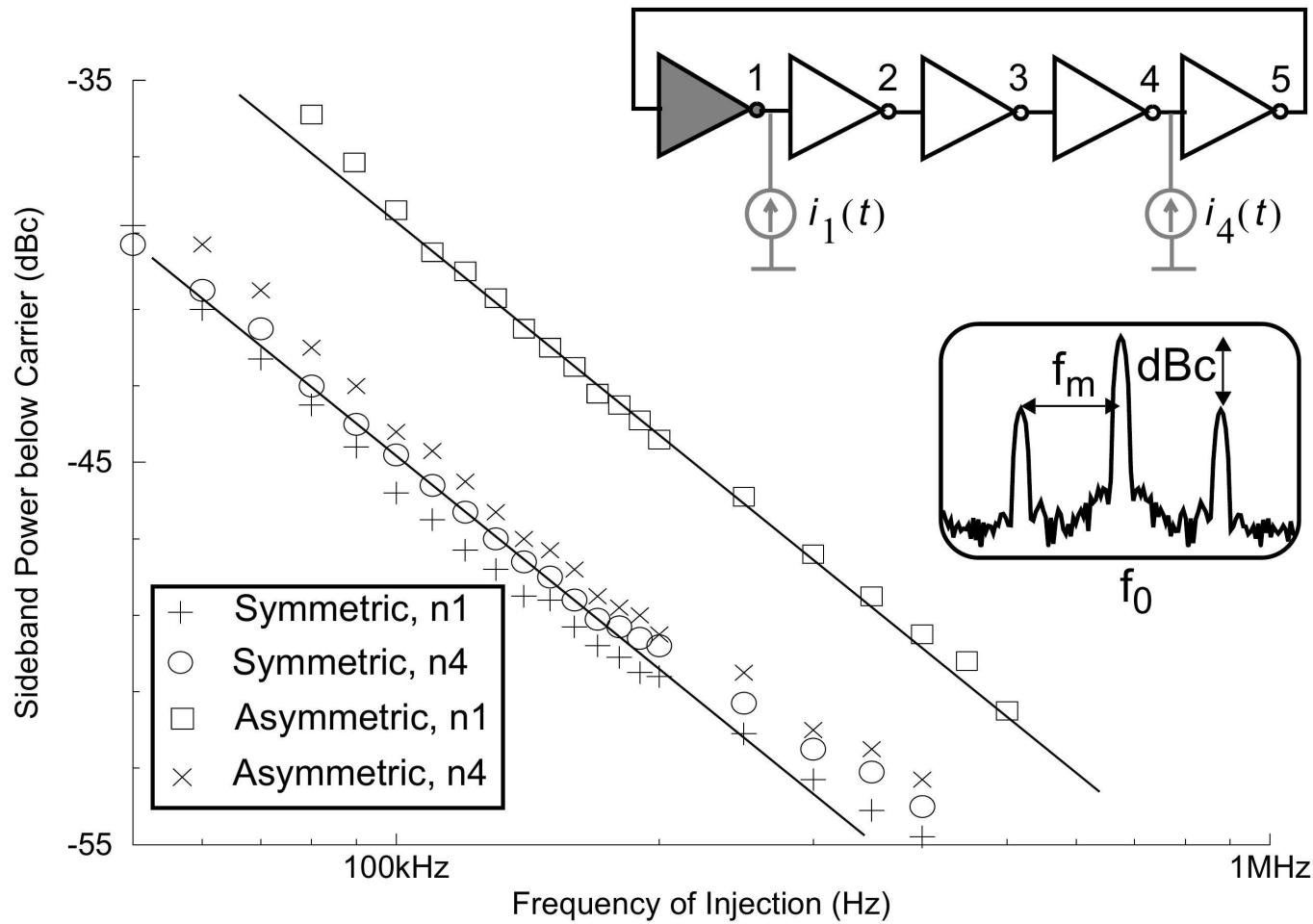
# Symmetric vs. asymmetric ring oscillator



# Oscillator currents are time-varying

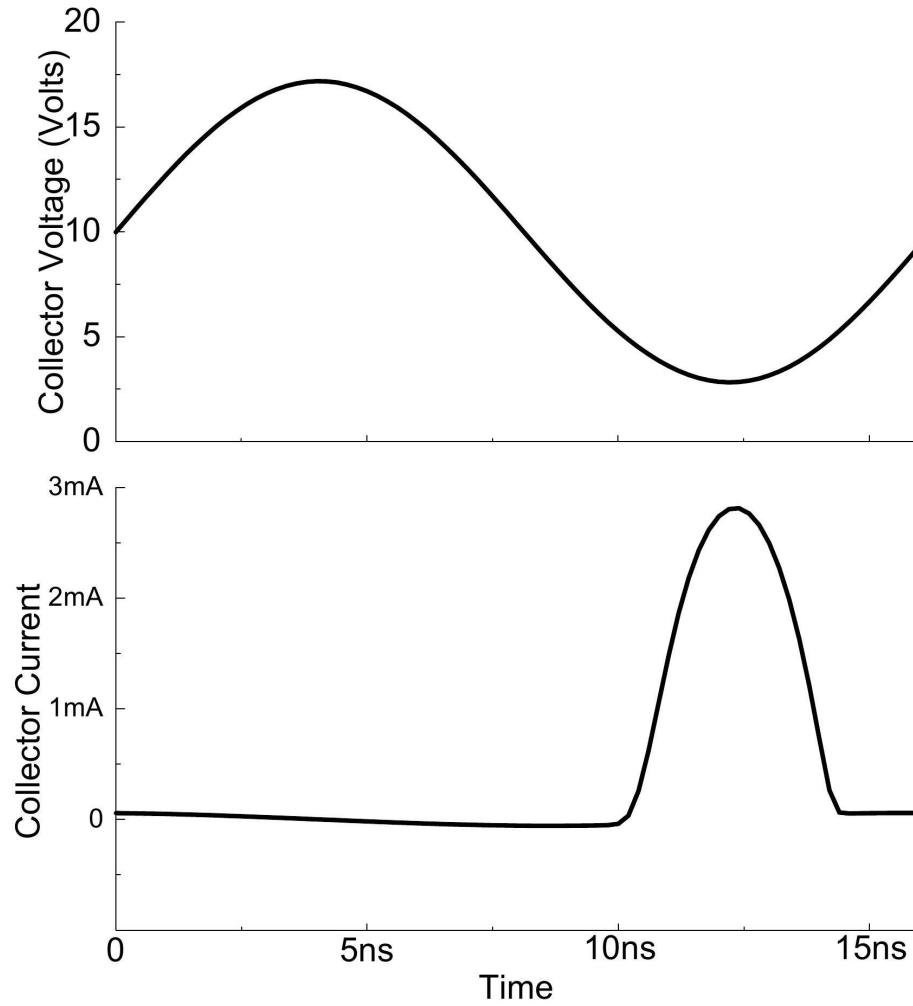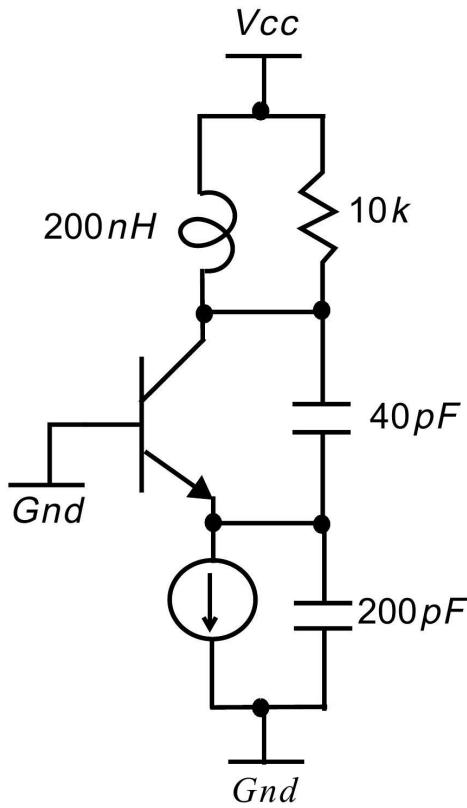

# Effects of time-varying currents

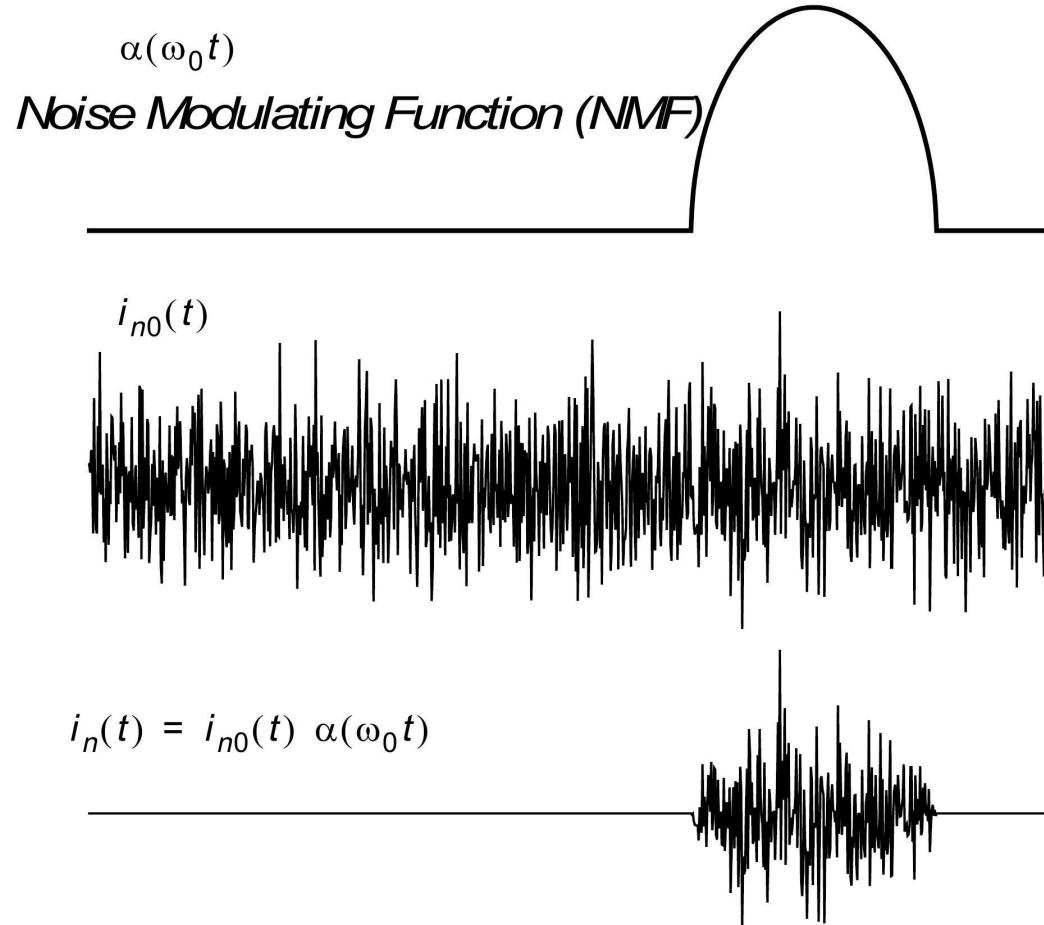


$$\begin{aligned}\phi(t) &= \int_{-\infty}^t i_n(t) \frac{\Gamma(\omega_0 \tau)}{q_{\max}} d\tau \\ &= \int_{-\infty}^t i_{n0}(t) \frac{\alpha(\omega_0 \tau) \Gamma(\omega_0 \tau)}{q_{\max}} d\tau\end{aligned}$$

Effective ISF:

$$\Gamma_{eff}(x) = \Gamma(x) \cdot \alpha(x)$$


**Cyclostationary noise can be modeled as stationary with modified ISF.**

# Colpitts

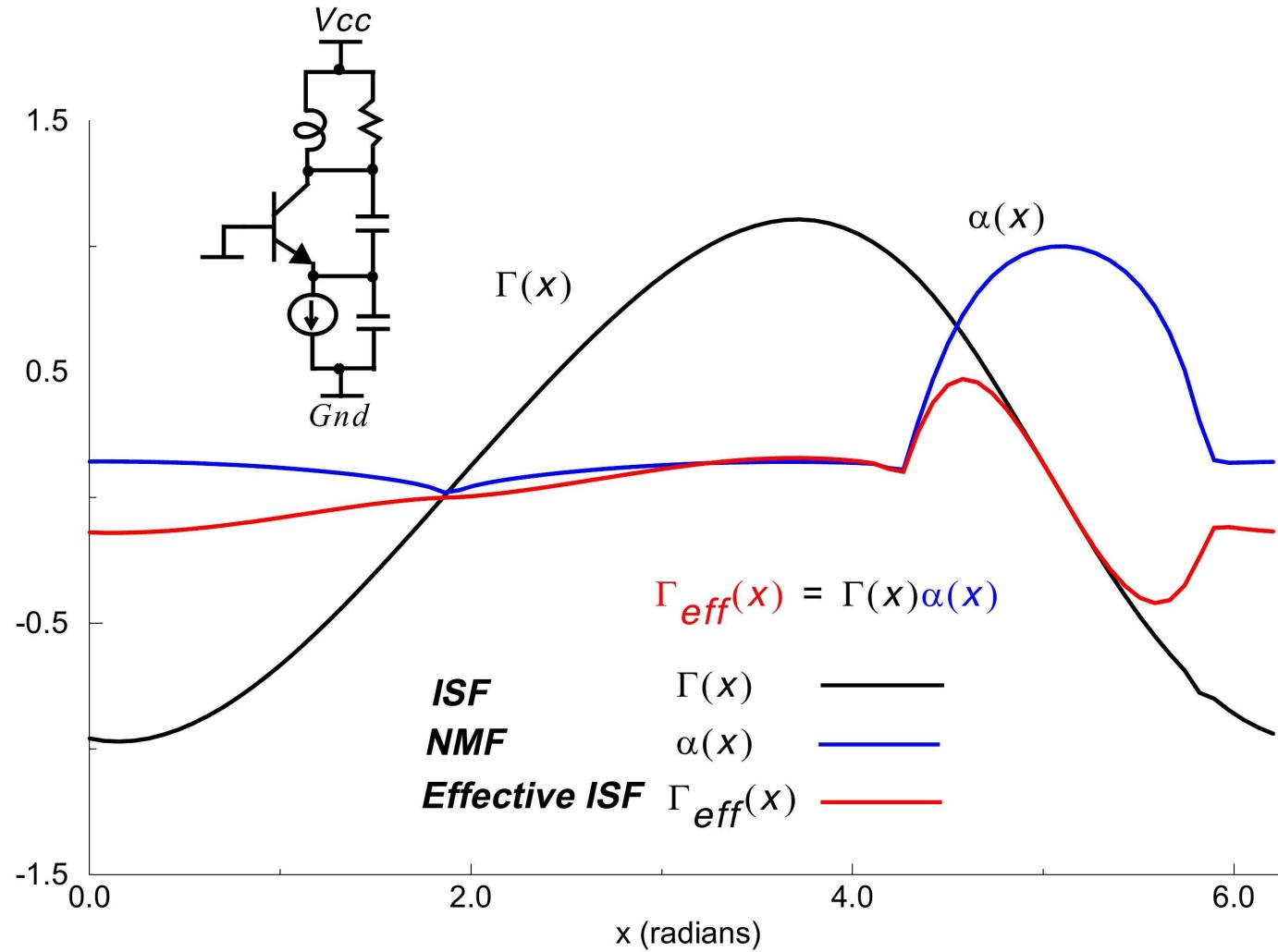
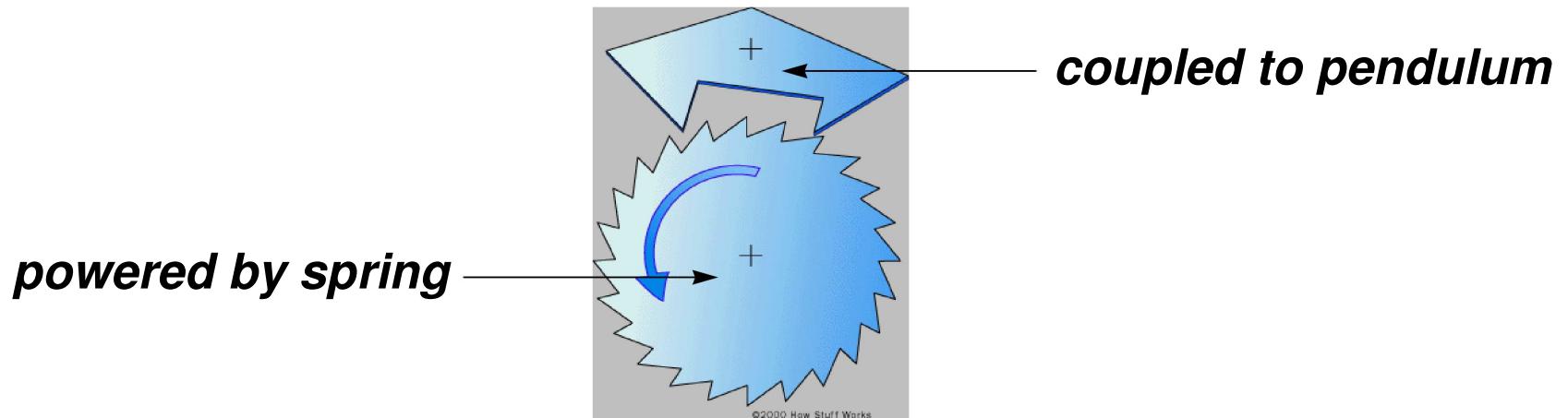
## *Plus ça change...*

- To exploit cyclostationarity, deliver energy to the tank impulsively, where the ISF is a minimum.
- This idea is old; an *escapement* in mechanical clocks delivers energy to pendulum impulsively.




# Conditions for optimal phase noise


---

- Impulses are delivered at or near pendulum's velocity maxima.
  - The escapement returns energy with minimal perturbation of oscillation period.[Airy, 1826]
- Similarly, the optimal moments in an *LC* oscillator are near the tank voltage maxima.


# A symmetric *LC* oscillator

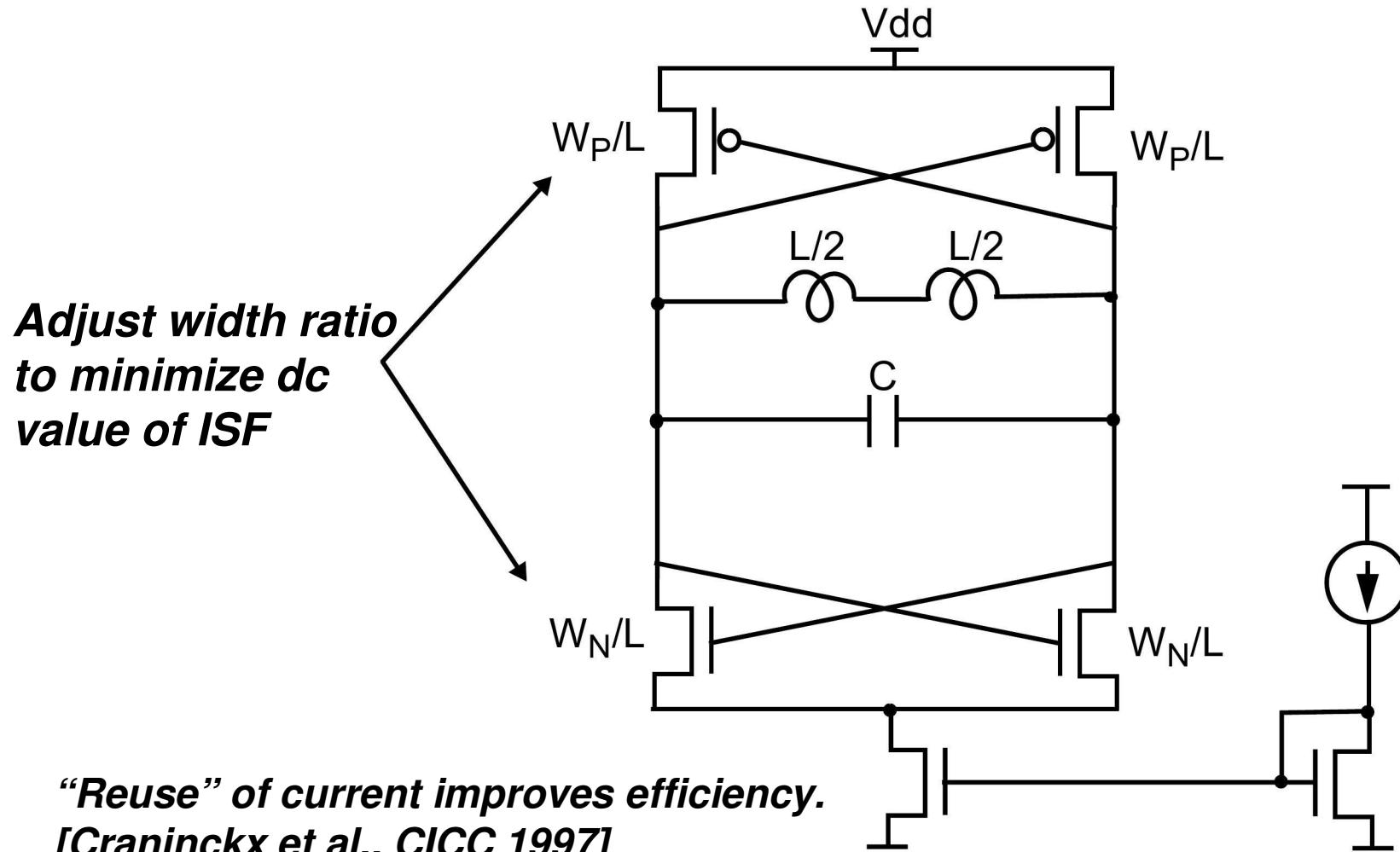


# Tank voltage amplitude

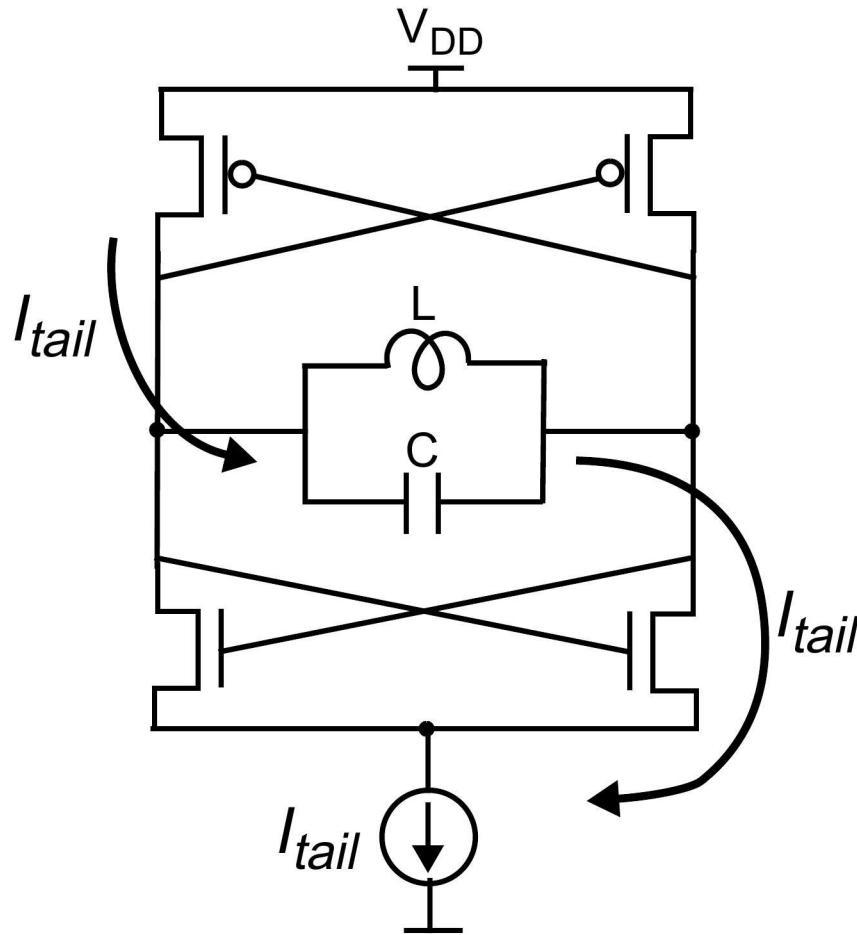

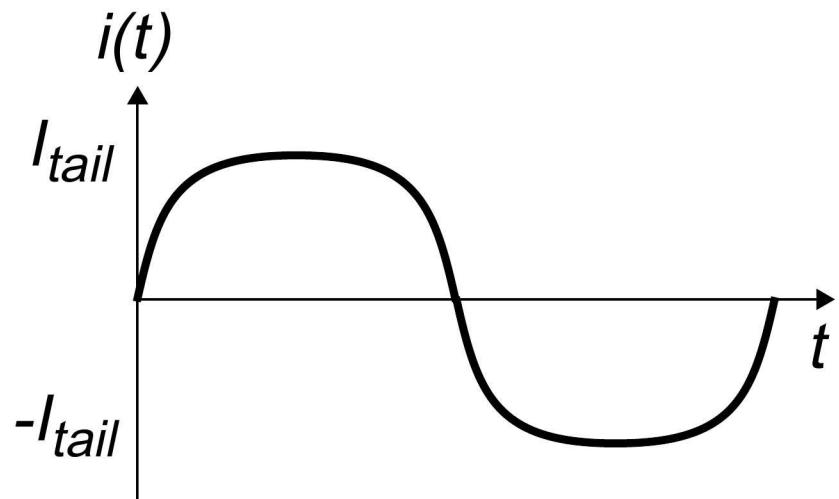*Assuming fast current steering,  
current can be approximated as  
nearly square:*



# Tank voltage amplitude

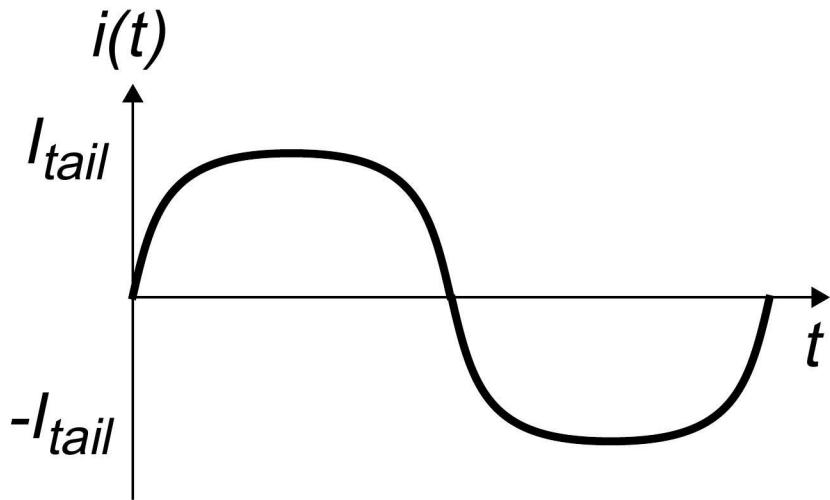


*For an ideal square waveform:*

$$V_{\max} = \frac{4}{\pi} I_{tail} R_{eq}$$


*For a sinusoidal waveform:*

$$V_{\max} = I_{tail} R_{eq}$$

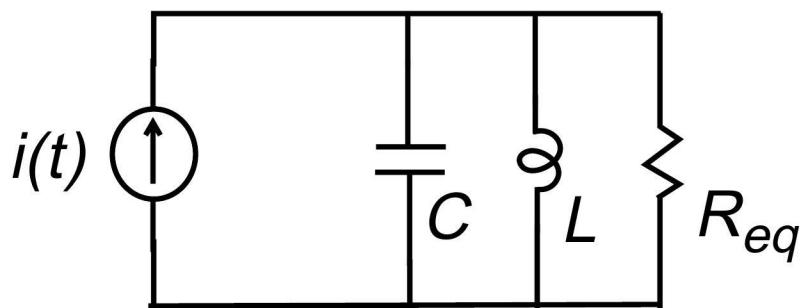


*(assuming operation in current-limited mode)*

# Modes of amplitude limiting

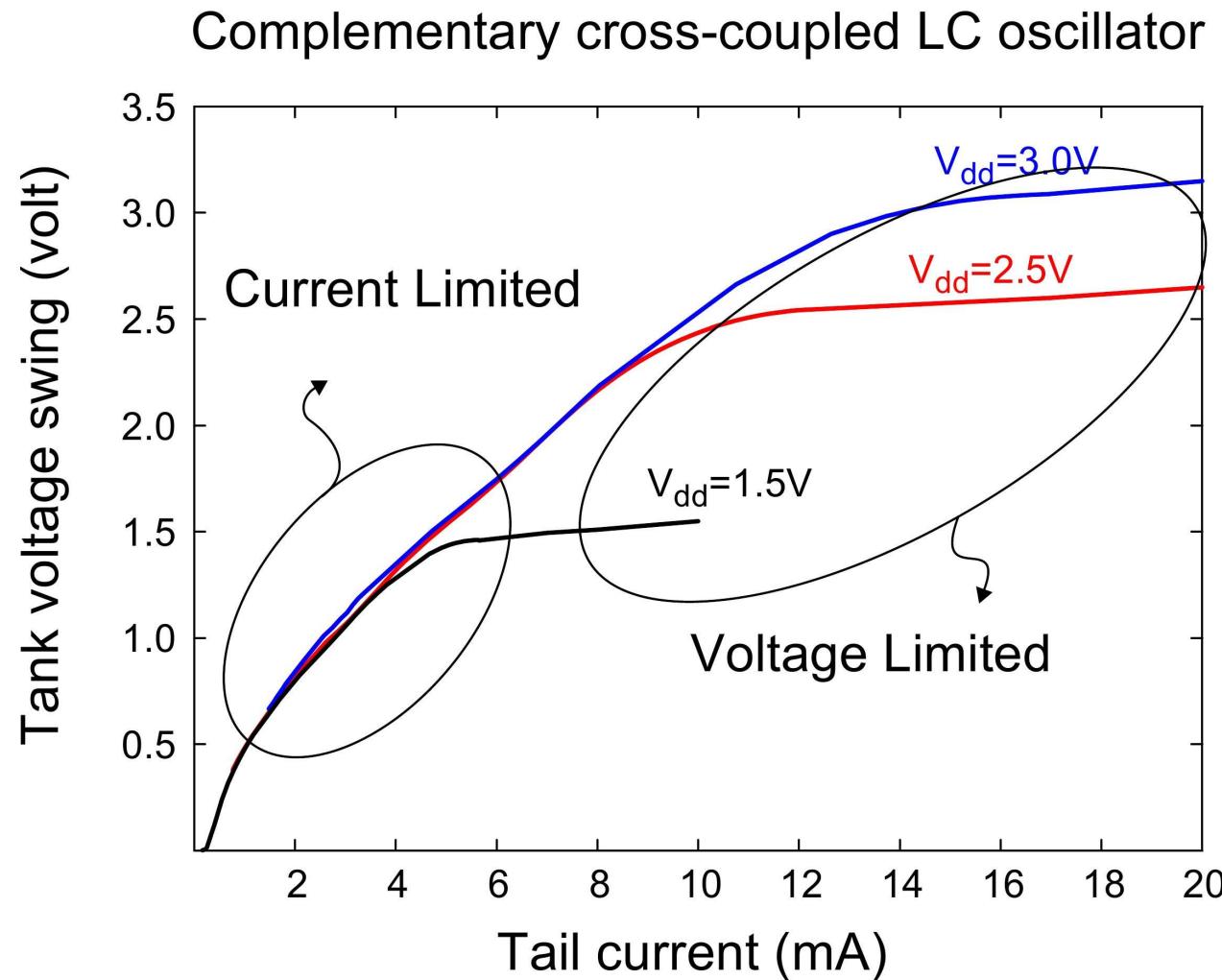

# Major noise sources

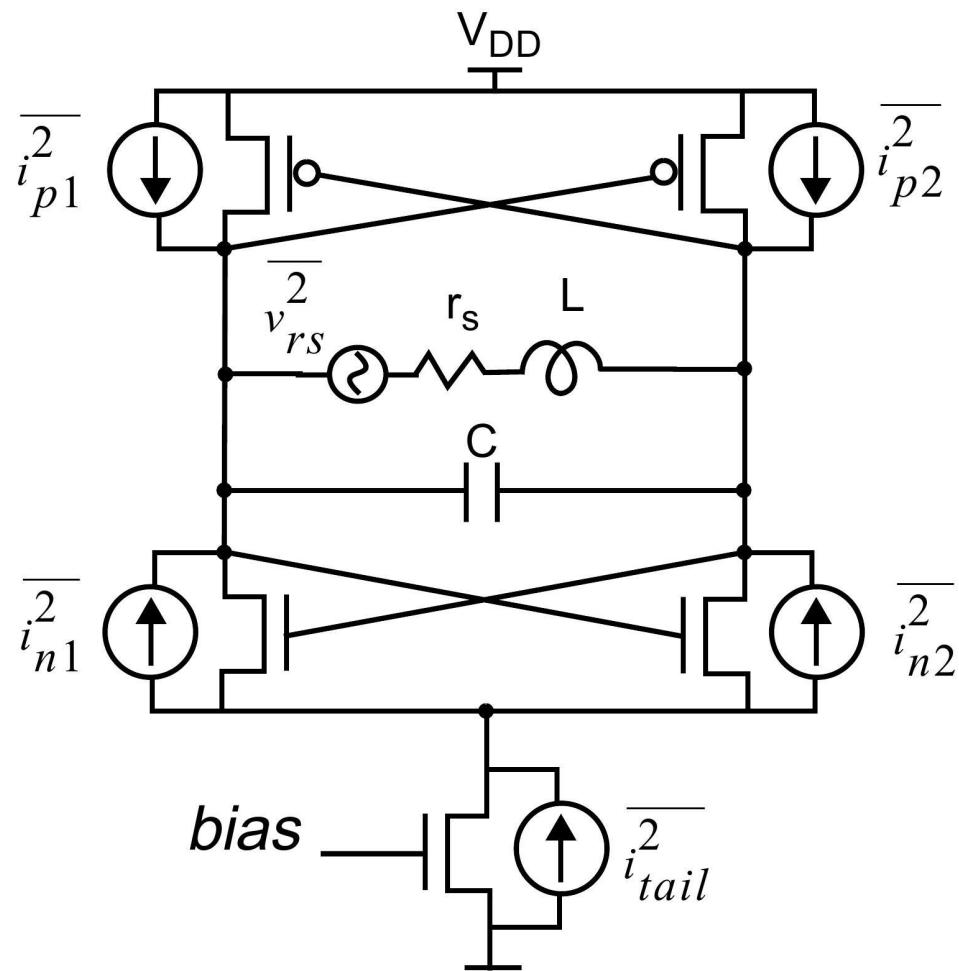

***Not all noise sources affect phase noise equally.***

***MOS noise:***


$$\frac{\overline{i_n^2}}{\Delta f} = 4kT\gamma\mu C_{ox} \frac{W}{L} (V_{GS} - V_T),$$

***(valid for long- and short-channel devices).***

***Inductor noise:***


$$\frac{\overline{v_n^2}}{\Delta f} = 4kTr_s.$$

# Equivalent circuit for noise sources

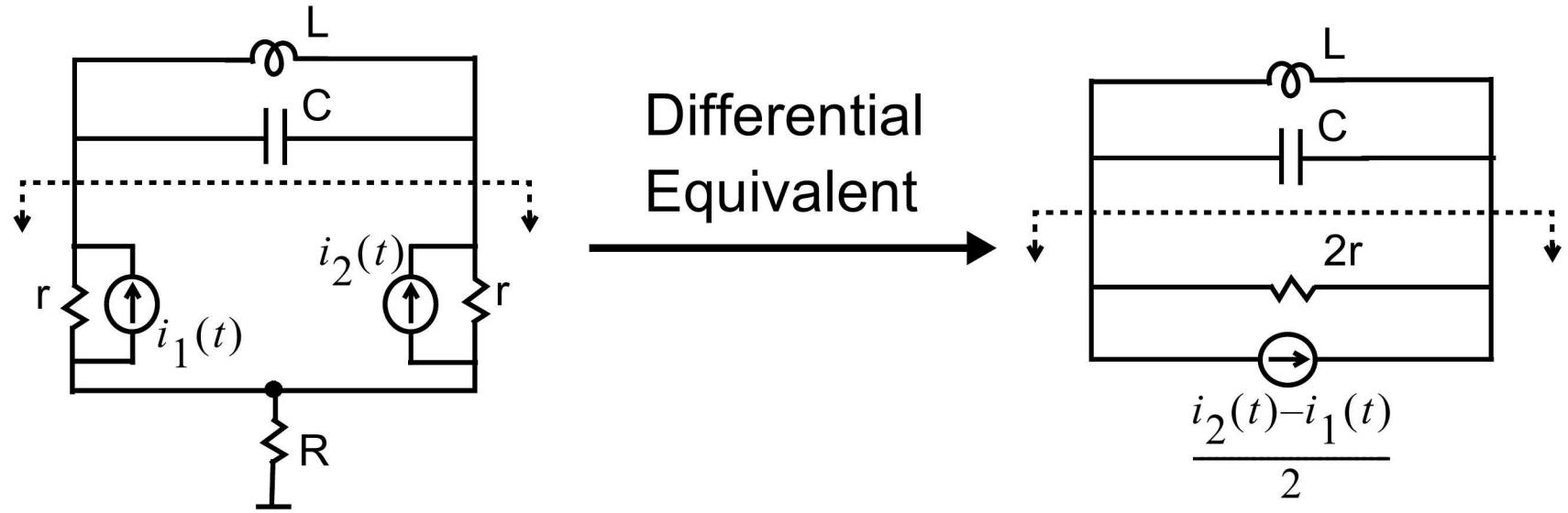


$$\left. \frac{\overline{i_n^2}}{\Delta f} \right|_{diff-pair} = \frac{1}{4} \left( \frac{\overline{i_{n1}^2}}{\Delta f} + \frac{\overline{i_{n2}^2}}{\Delta f} + \frac{\overline{i_{p1}^2}}{\Delta f} + \frac{\overline{i_{p2}^2}}{\Delta f} \right) = \frac{1}{2} \left( \frac{\overline{i_n^2}}{\Delta f} + \frac{\overline{i_p^2}}{\Delta f} \right)$$


# Waveform and ISF

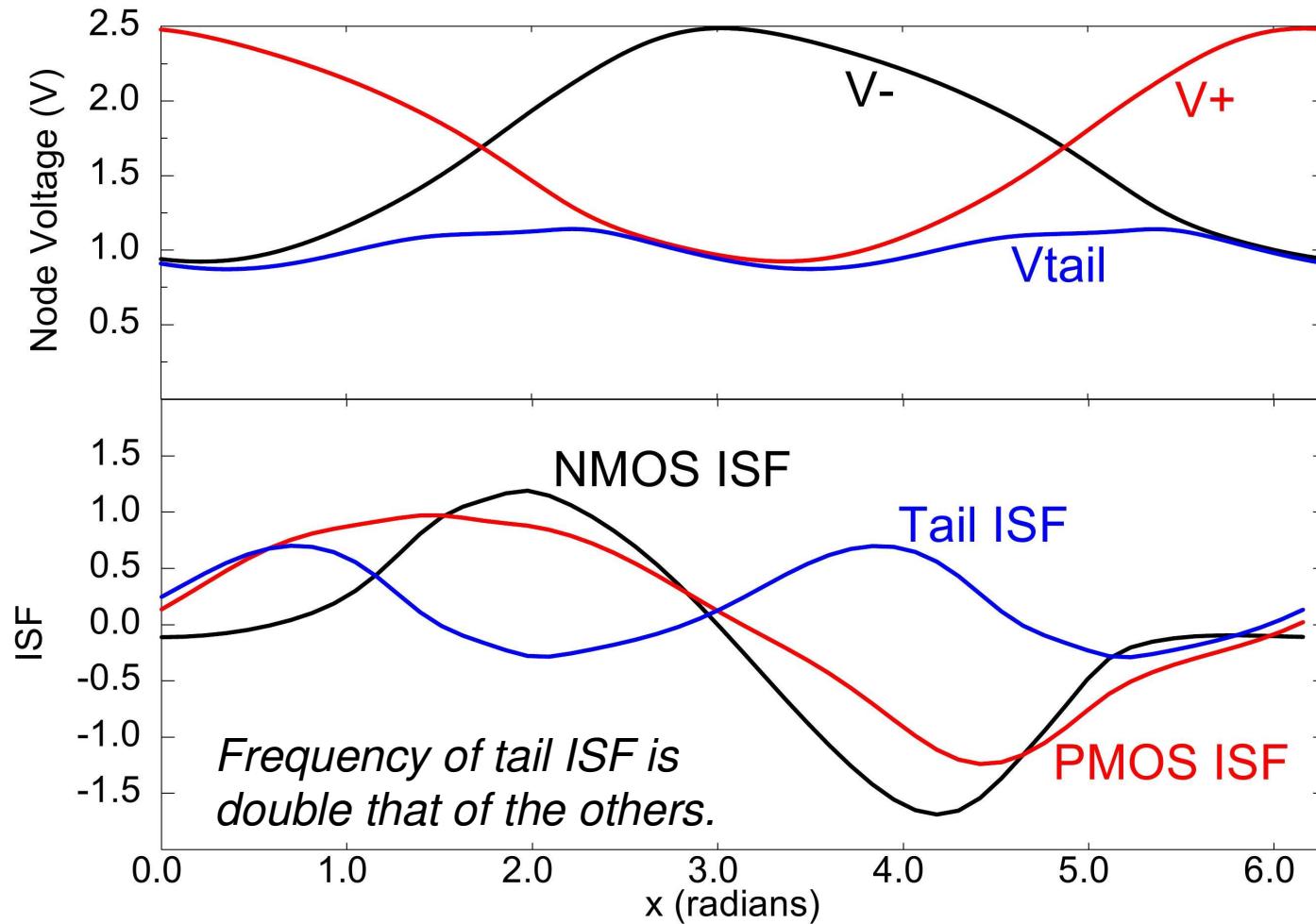


# Effect of tail current noise

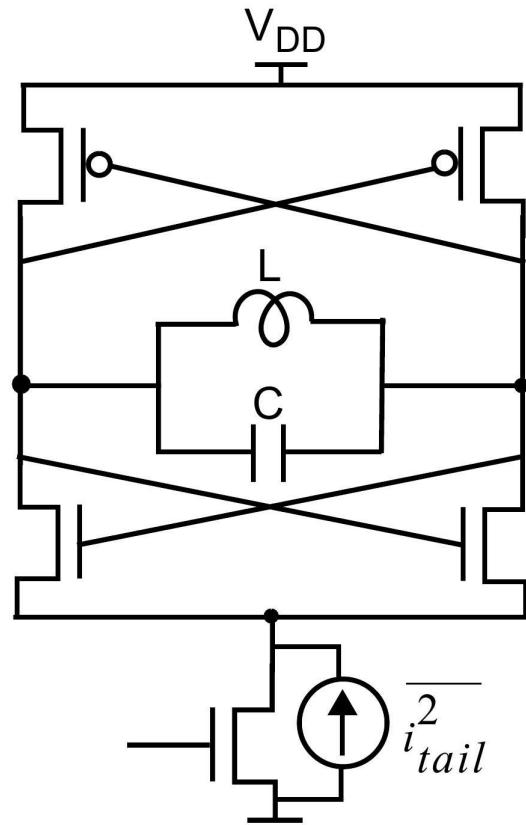

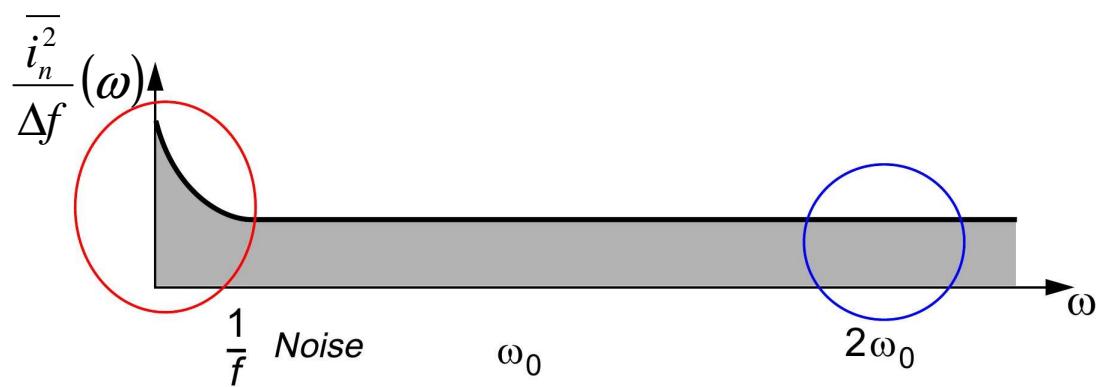*For the tail current source, only noise centered about even harmonics of the carrier contribute to phase noise, as consequence of double-frequency tail ISF.*




# Die photo of complementary oscillator


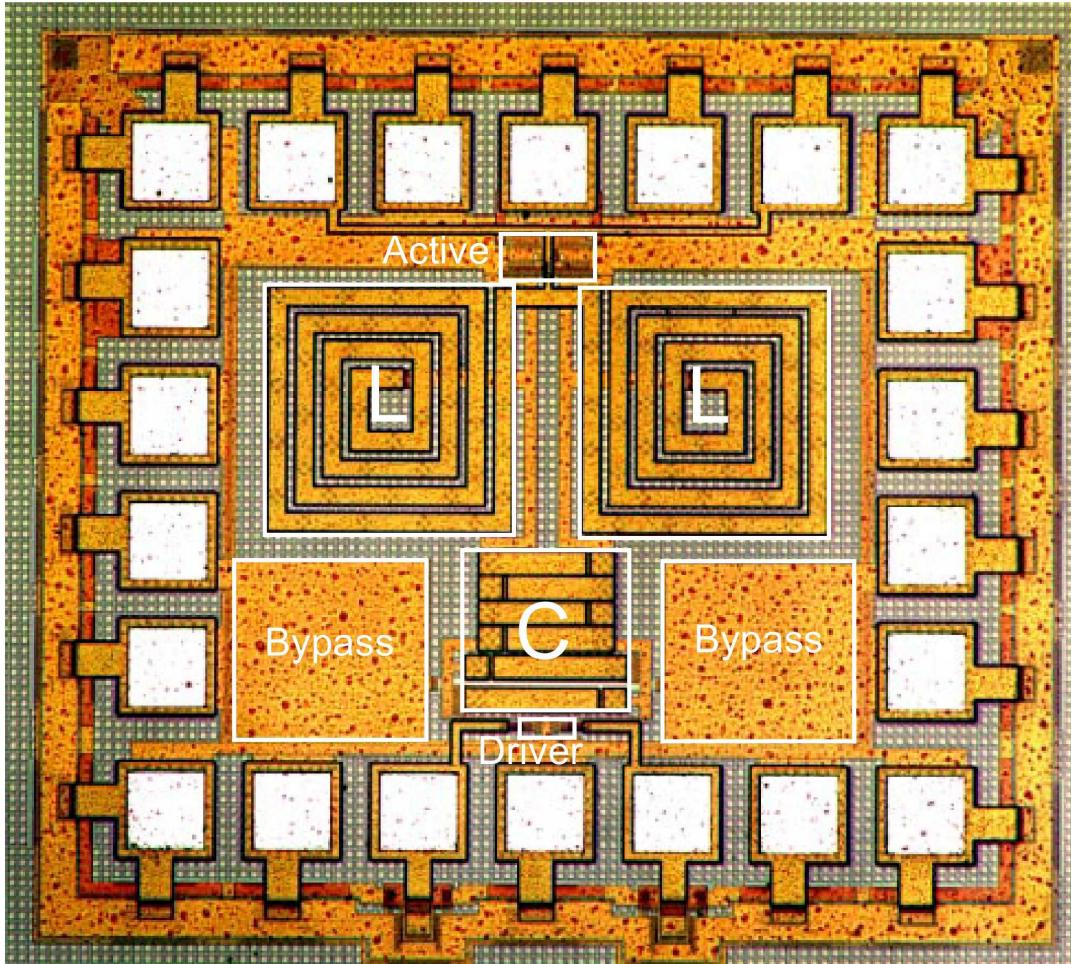


***0.25μm CMOS  
700μm x 600μm  
Pad-limited***



# Measured phase noise

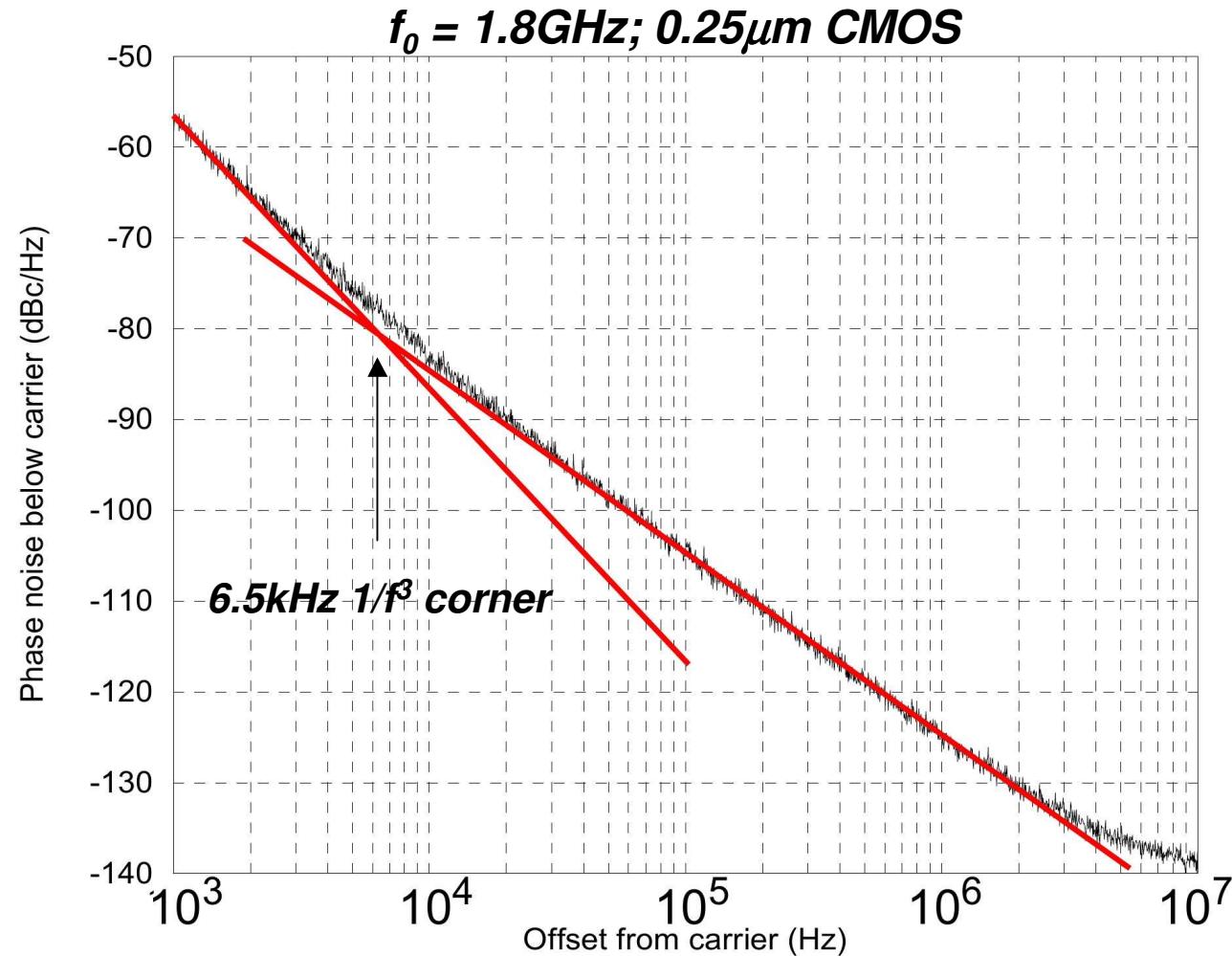

# Complementary cross-coupled oscillator

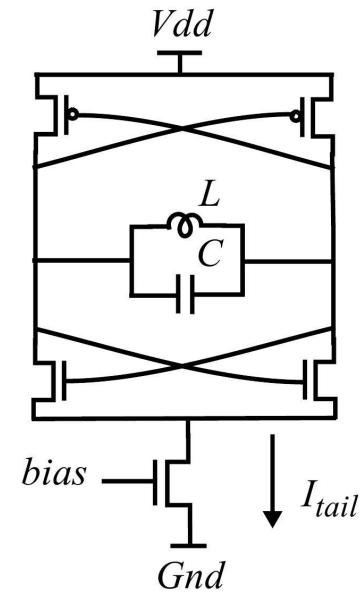
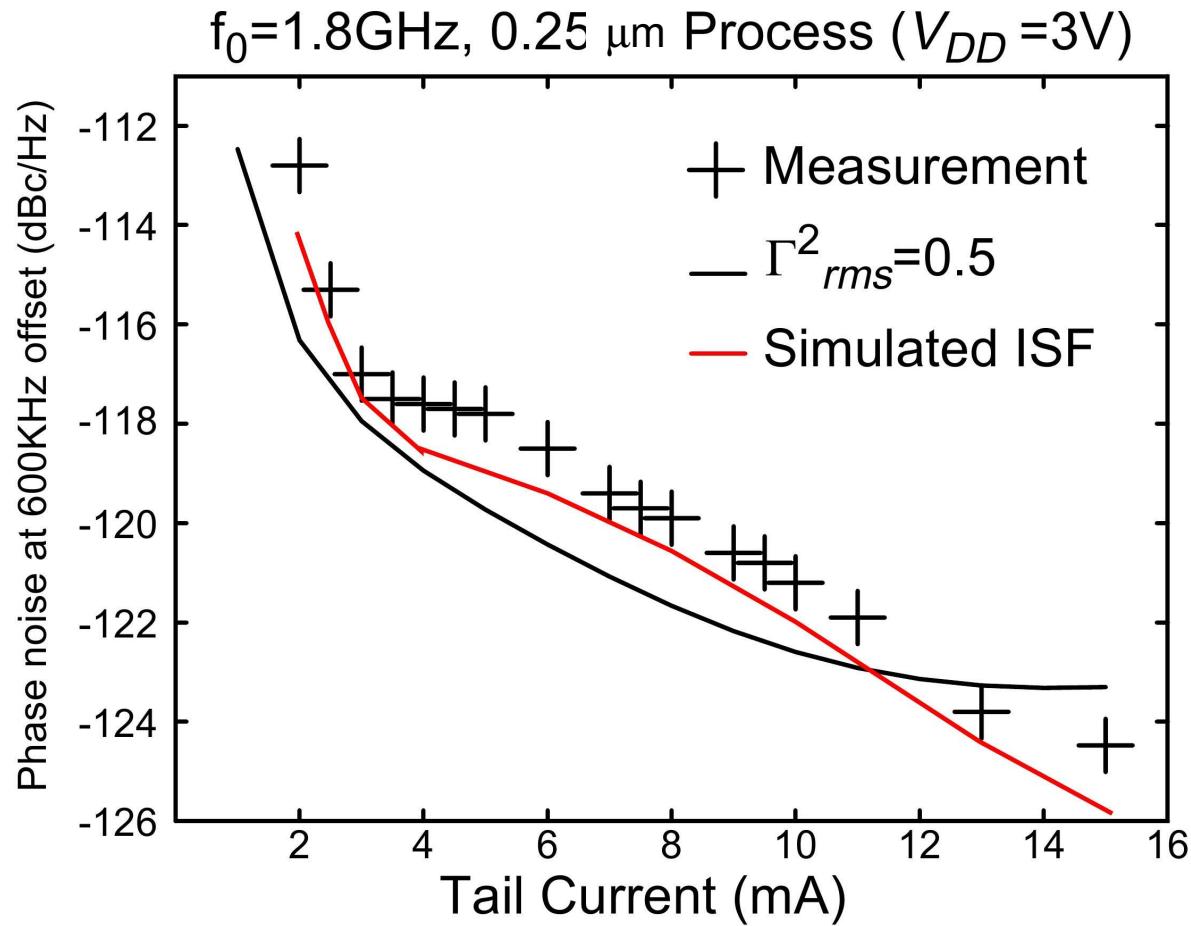


# Complementary cross-coupled VCO

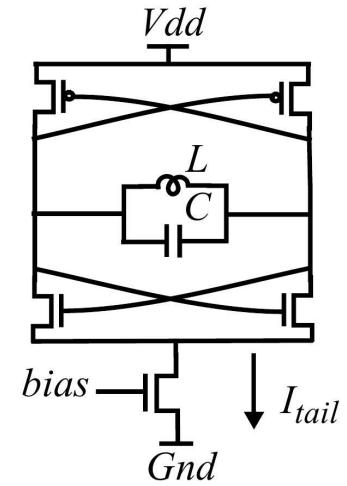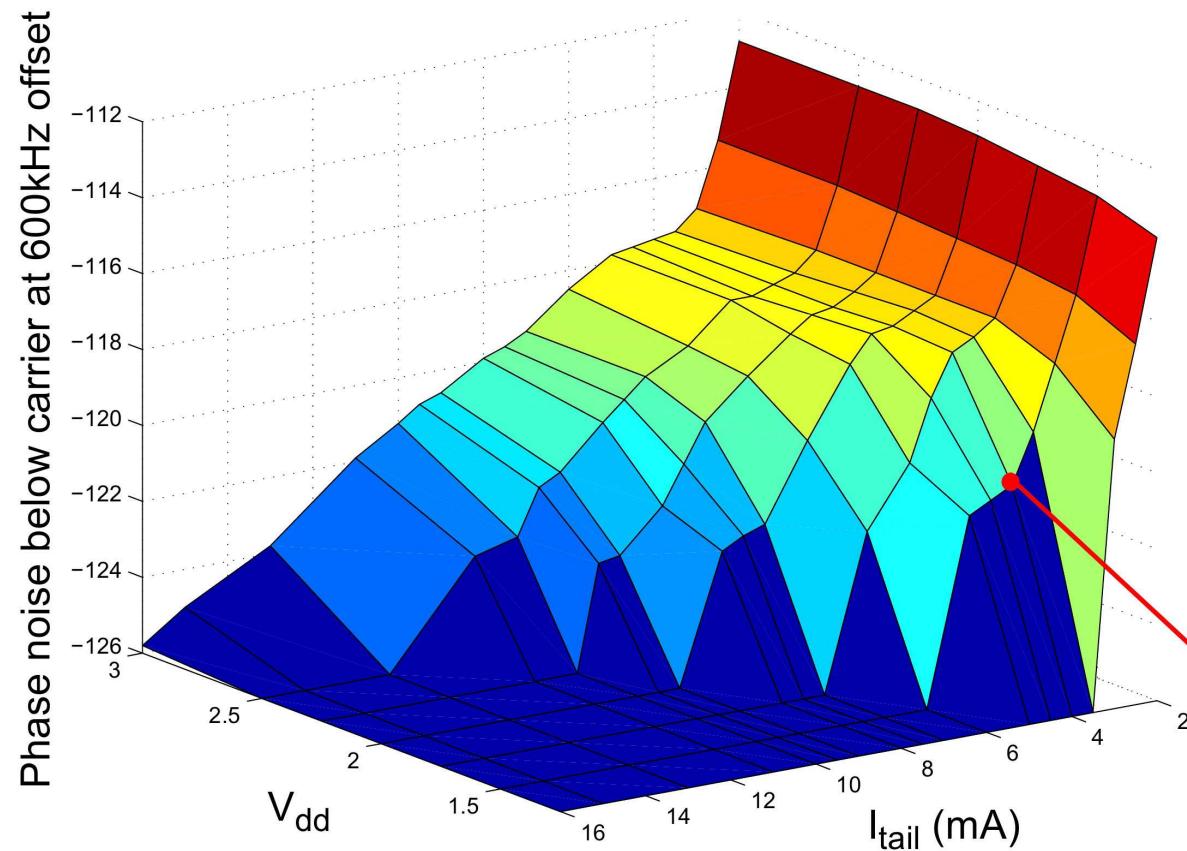


$f_0 = 1.8\text{GHz}$   
 $P = 6\text{mW}$   
 $-121\text{dBc/Hz@600kHz}$

# Complementary vs. all-NMOS VCO

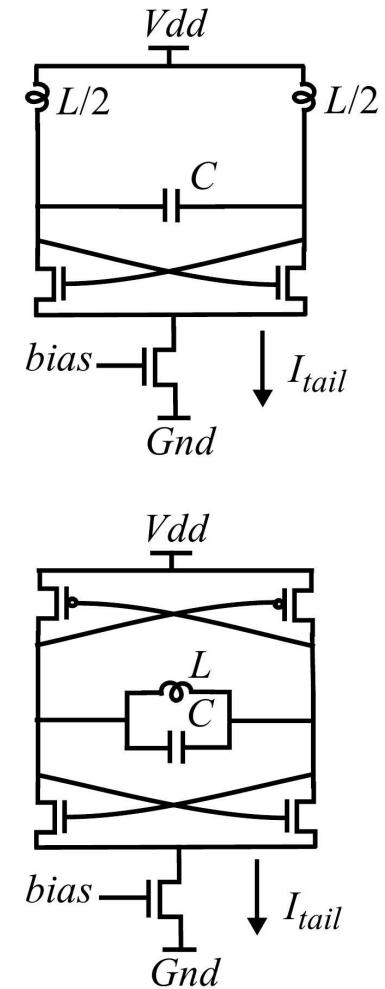
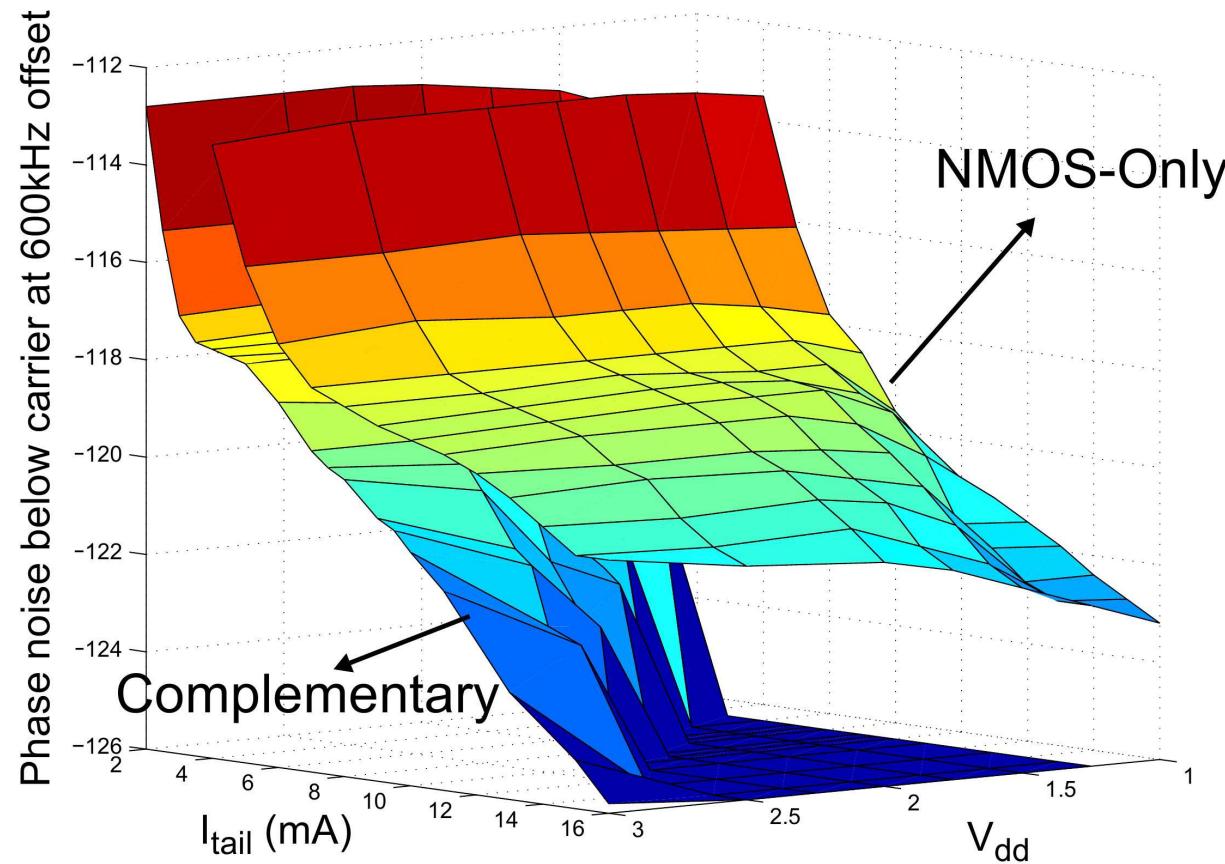


# A non-Stanford, non-CMOS example

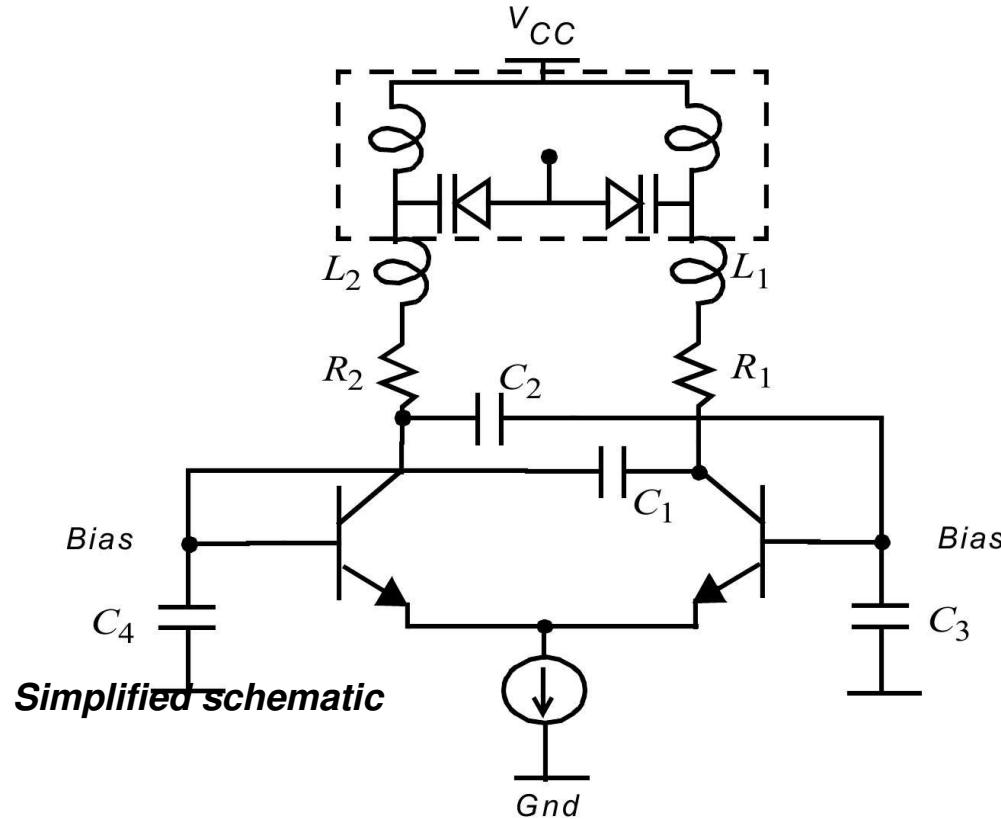


*Ref: M.A. Margarit, Joo Leong Tham, R.G. Meyer, M.J. Deen, “A low-noise, low-power VCO with automatic amplitude control for wireless applications,” IEEE JSSC, June 1999, pp.761-771.*


# $I_C$ and ISFs for core transistors

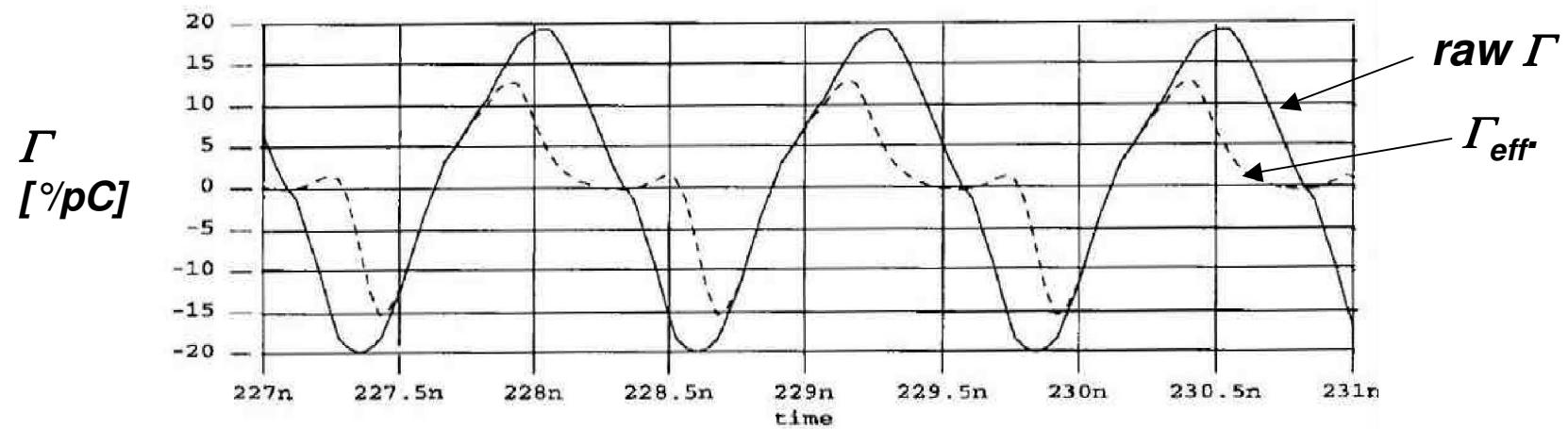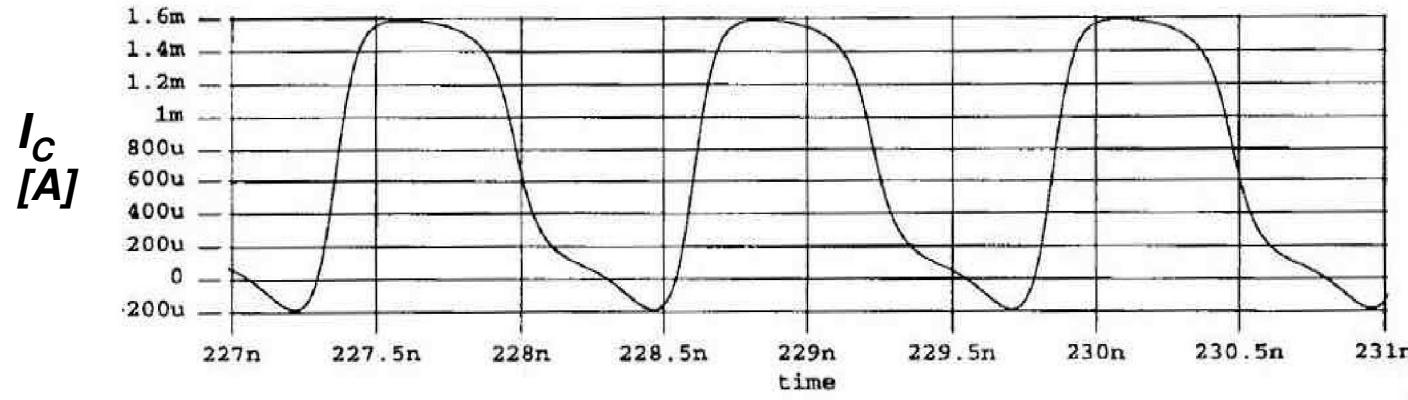


# $V_{out}$ and ISF for tail source

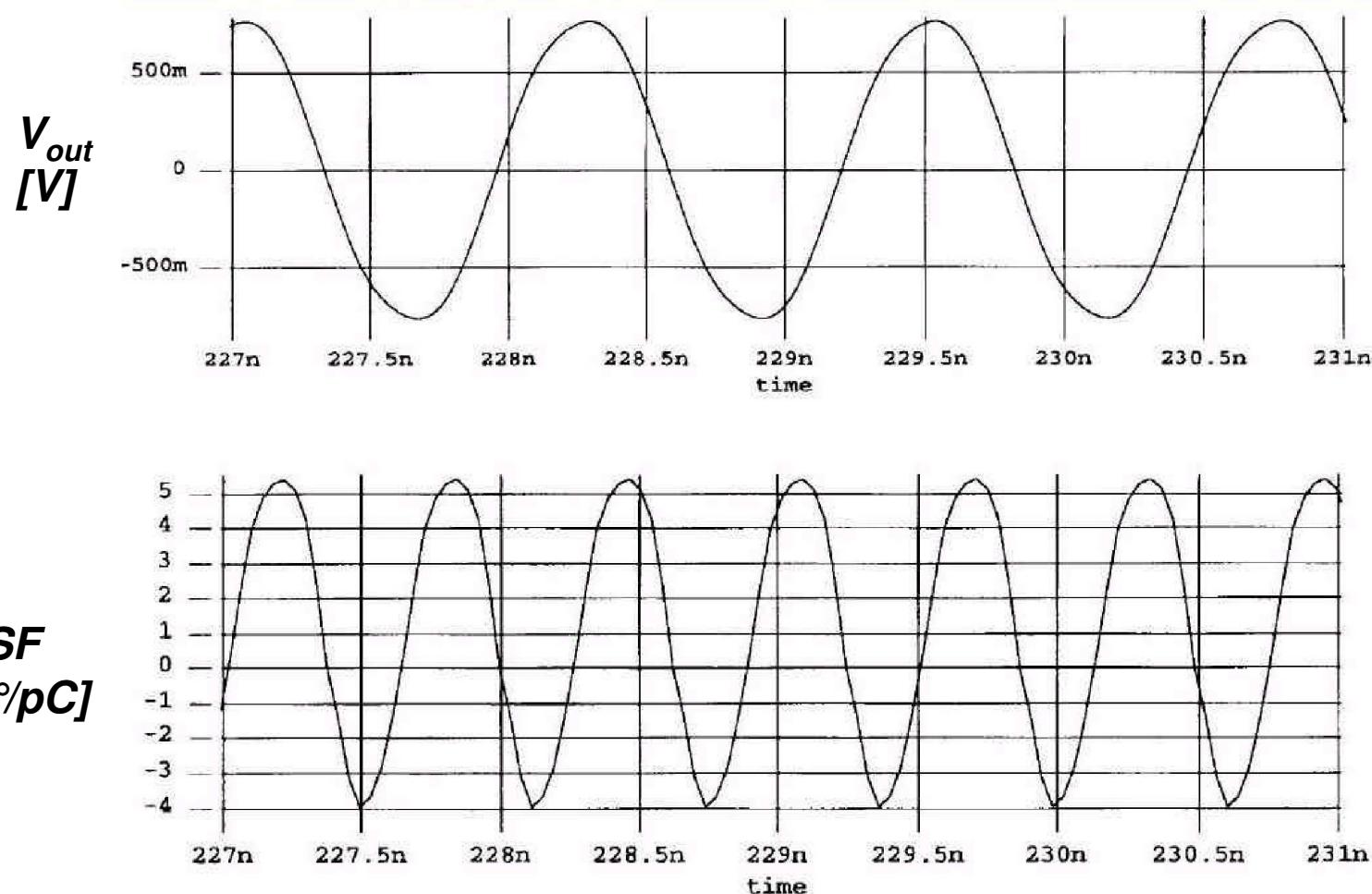

# Theory vs. measurement

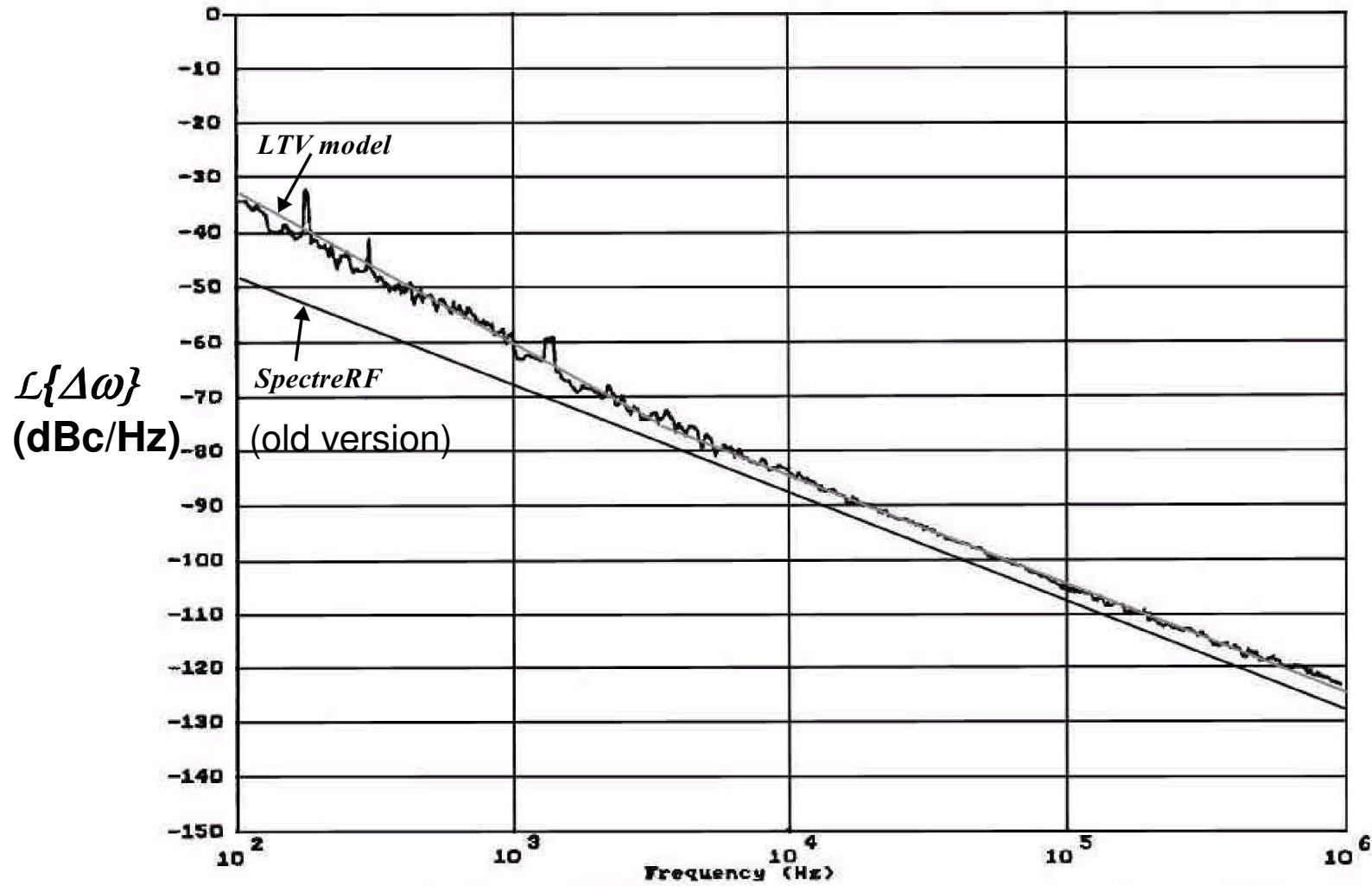
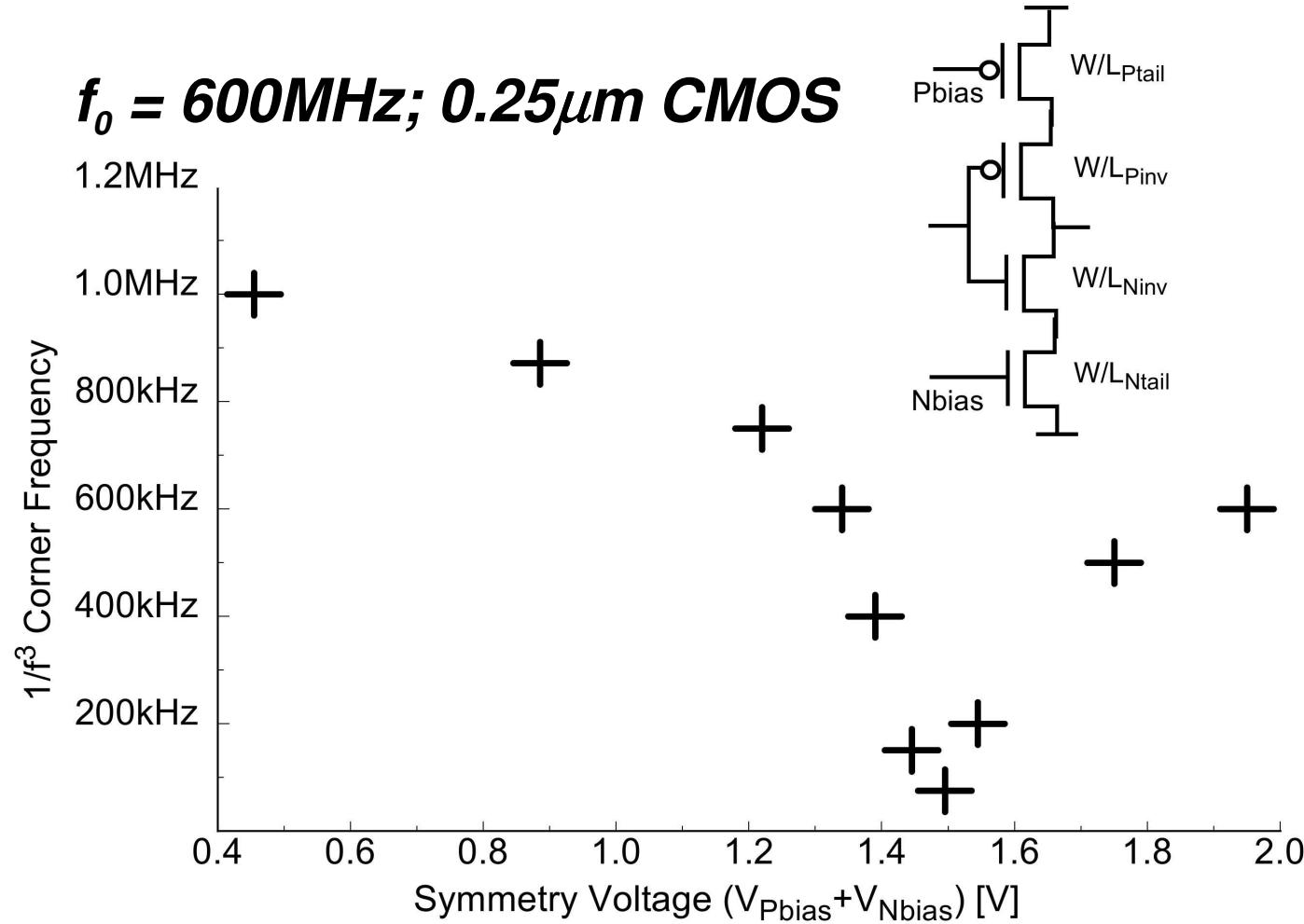
# 9-stage current-starved single-ended VCO




# Amplitude noise

- Phase noise generally dominates close-in spectrum.  
Amplitude noise generally dominates far-out spectrum.
- Amplitude noise can be accommodated with the same impulse-response method.
  - Amplitude control dynamics are frequently approximately single-pole.
    - For an isolated LC tank, the bandwidth is simply  $\omega_0/Q$ .
    - Contribution to output noise spectrum is flat up to an offset equal to the amplitude-control bandwidth, then rolls off.
    - Superposition with phase noise contribution leads to a characteristic pedestal in the oscillator spectrum.
  - If dynamics are second-order, there can be peaking in the oscillator spectrum.
- Sideband asymmetry can also result from superposition.
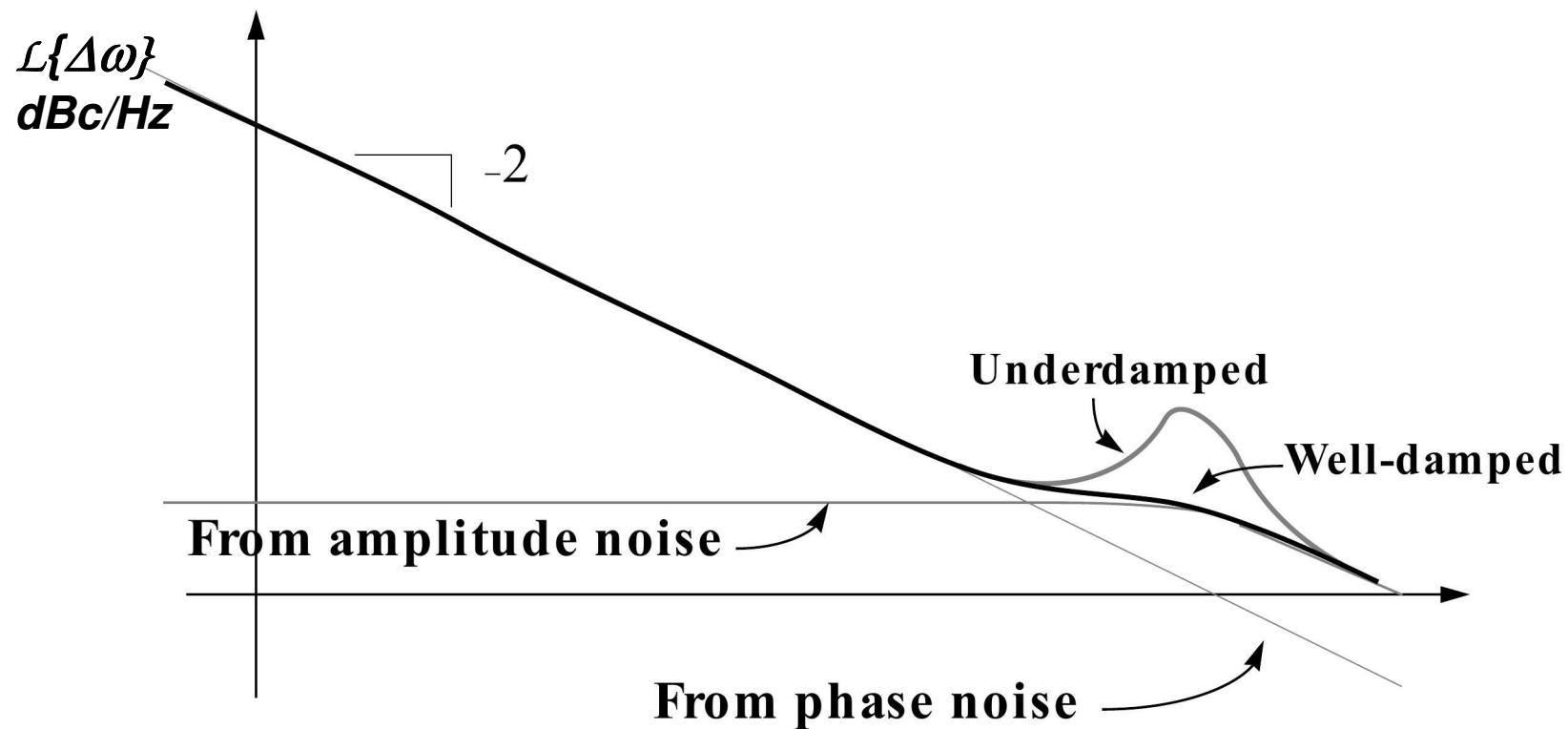
# Amplitude response

- Possible spectra resulting from different amplitude control dynamics are as follows:



# Summary and conclusions

- LTI theories say:
  - Maximize signal power and  $Q$ , operate at incipient voltage-limiting, with minimum  $L/R$ .
  - One cannot do anything about  $1/f$  noise upconversion.
    - $1/f^3$  corner is purely a function of technology and bias.
- LTV theory says:
  - LTI is generally right in the first bullet above.
  - LTI is wrong about the second bullet: Exploiting topological symmetry to minimize the ISF dc value can suppress  $1/f$  noise upconversion.


# Nonlinearity and Distortion

# Linear circuits

- In a linear system the output is always a linear function of the input:

$$v_o = c_1 v_i$$

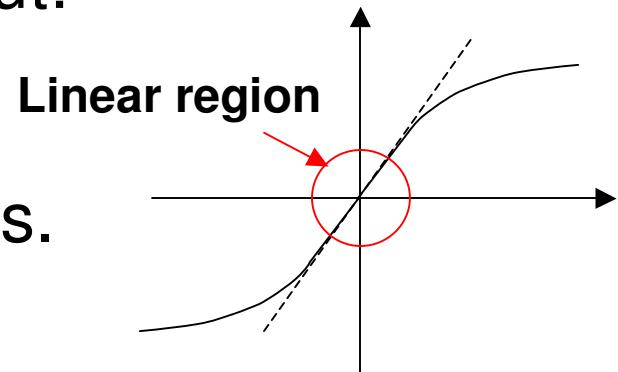- In real circuits, this relationship is typically valid only for small signals.



- The output of a nonlinear and memoryless circuit can be approximated with a polynomial:

$$v_o = f(v_{in}) \approx c_0 + c_1 v_i + c_2 v_i^2 + c_3 v_i^3 + \dots$$

# First: *Harmonic distortion*

- Assume the input is a single sinusoid:

$$v_i = V_i \cos(\omega t)$$

- A linear amplifier would only produce:

$$v_o = c_1 V_i \cos(\omega t + \phi) \quad \text{ignore phase today}$$


- But the output of a memoryless nonlinear system is:

$$v_o = c_0 + c_1 V_i \cos(\omega t) + c_2 V_i^2 \cos^2(\omega t) + c_3 V_i^3 \cos^3(\omega t) + \dots$$

$$v_o = c_0 + c_1 V_i \cos(\omega t) + \frac{c_2 V_i^2}{2} [1 + \cos(2\omega t)] + \frac{c_3 V_i^3}{4} [3 \cos(\omega t) + \cos(3\omega t)] + \dots$$
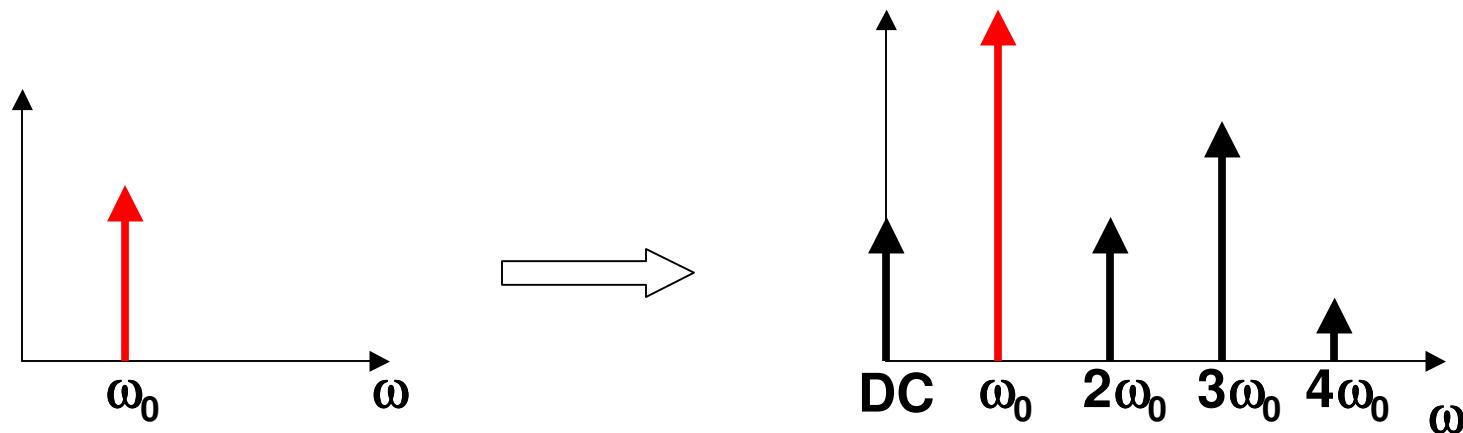
# Harmonic distortion (cont)

$$v_o = c_0 + c_1 V_i \cos(\omega t) + \frac{c_2 V_i^2}{2} [1 + \cos(2\omega t)] + \frac{c_3 V_i^3}{4} [3\cos(\omega t) + \cos(3\omega t)] + \dots$$



- As a result of nonlinearity not only do we get signals at the fundamental frequency ( $\omega$ ), we also get signals at multiples of the input frequency ( $2\omega$ ,  $3\omega$ , ...).
- Even-order nonlinearities produce even-order harmonics ( $2\omega$ ,  $4\omega$ , ...), which include DC.
- Odd-order nonlinearities produce odd-order harmonics ( $3\omega$ ,  $5\omega$ , ...), which include the fundamental frequency ( $\omega$ ).

# Fractional harmonic distortion

- Fractional second-harmonic distortion is a normalized measure:

$$HD2 = \frac{\text{amplitude of the second harmonic}}{\text{amplitude of the fundamental}}$$

- If we assume the squared term dominates the second harmonic

$$HD2 = \frac{\frac{1}{2}c_2V_i^2}{c_1V_i} = \frac{1}{2} \frac{c_2}{c_1} V_i$$

- HD2 is proportional to input amplitude.
- Similarly HD3 is defined as

$$HD3 = \frac{\text{amplitude of the third harmonic}}{\text{amplitude of the fundamental}} = \frac{\frac{1}{4}c_3V_i^3}{c_1V_i} = \frac{1}{4} \frac{c_3}{c_1} V_i^2$$

- HD3 is proportional to the input power.

# Total harmonic distortion

- Since the harmonics are orthogonal the total output power is the sum of the harmonic powers.
- Total harmonic distortion (THD) is defined as:

$$THD = \sqrt{\frac{\text{power in distortion}}{\text{power in fundamental}}}$$

- Therefore:

$$THD = \sqrt{HD2^2 + HD3^2 + \dots}$$

# ***Intermodulation distortion***

- So far we have characterized a nonlinear system using a single input tone. Now consider two tones:

$$v_i = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t$$

$$v_o = c_0 + c_1 v_i + c_2 v_i^2 + c_3 v_i^3 + \dots$$

- The squared term gives:

$$c_2 [V_1^2 \cos^2 \omega_1 t + V_2^2 \cos^2 \omega_2 t + 2V_1 V_2 \cos \omega_1 t \cos \omega_2 t]$$

$$= c_2 \frac{V_1^2}{2} (1 + \cos 2\omega_1 t) + c_2 \frac{V_2^2}{2} (1 + \cos 2\omega_2 t) +$$

$$c_2 V_1 V_2 [\cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t]$$

# Second-order intermodulation

- The last term,  $\cos(\omega_1 \pm \omega_2)t$ , is the second-order intermodulation (IM) product.
- The normalized second-order IM distortion is defined with two input tones of equal amplitude:

$$V_1 = V_2 = V_i$$


$$IM\ 2 = \frac{\text{amplitude of the intermod}}{\text{amplitude of the fundamental}} = \frac{c_2}{c_1} V_i$$

- Note that


$$IM\ 2 = 2HD2$$

$$IM\ 2|_{dB} = HD2|_{dB} + 6dB$$

# IM2 consequences

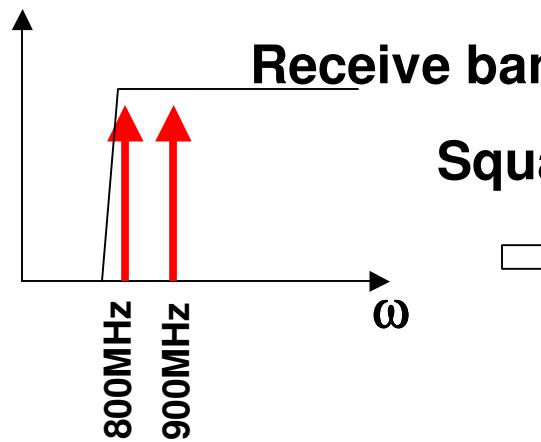


Squared term

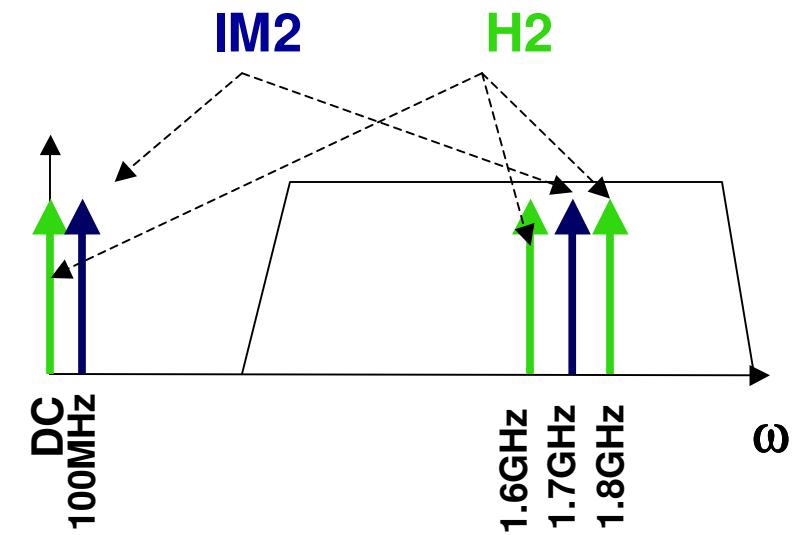

- IM2 produces both low frequency ( $\omega_1 - \omega_2$ ) and high frequency ( $\omega_1 + \omega_2$ ) components.
- The term at ( $\omega_1 + \omega_2$ ) can be a problem in wideband receivers (i.e., those with bandwidth larger than one octave).
- Example: Suppose the receiver covers 800MHz-2.4GHz and two interfering signals appear at 800MHz and 900MHz.
- The 2nd-order IM terms are at 100MHz and 1.7GHz; the second harmonics are at 1.6GHz and 1.8GHz. Thus IM2 and HD2 generate three components within the receive band.
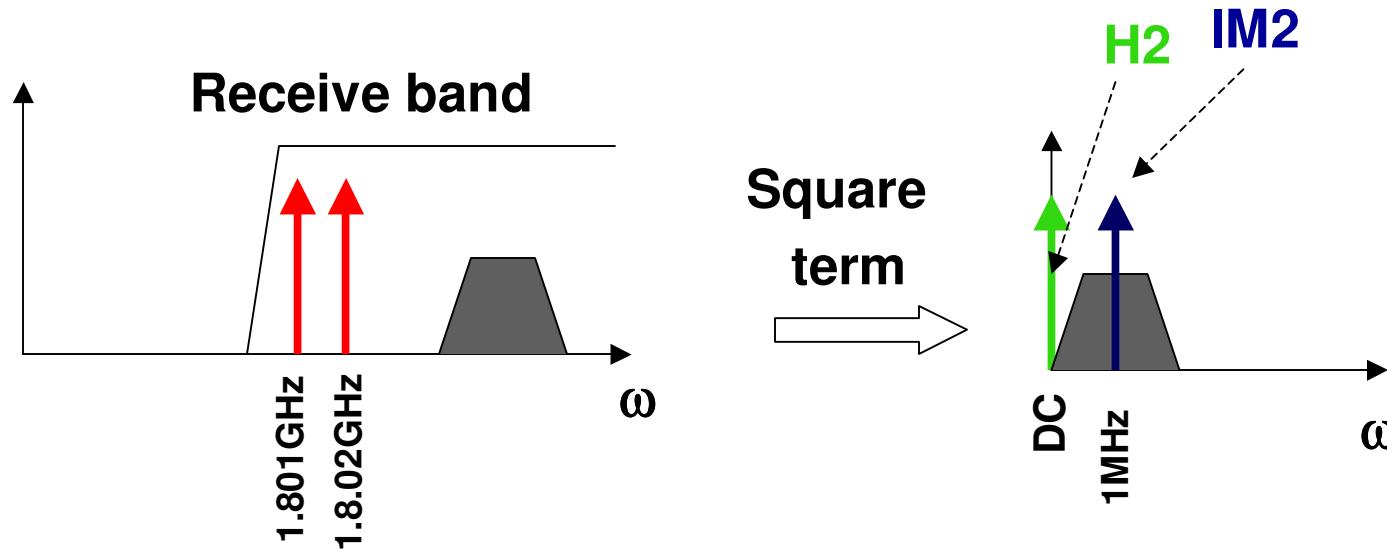
# IM2 issues for low-IF and zero-IF receivers



- The low frequency of the second-order IM term ( $\omega_1 - \omega_2$ ) can be a problem in low-IF or zero-IF receivers
- Example: Assume a receiver covers 1.8GHz-1.9GHz and has an IF=1MHz. Now assume two interfering signals at 1.801MHz and 1.802MHz.
- The second-order IM distortion product is at the IF frequency and therefore constitutes potentially serious interference.

# Third-order intermodulation

- Now if we consider the cubic term we get:

$$c_3 v_i^3 = c_3 [V_1 \cos \omega_1 t + V_2 \cos \omega_2 t]^3$$

- Expansion yields, in part, terms which are the same as the cubic distortion with a single input:

$$\frac{c_3 V_{1,2}^3}{4} [3 \cos \omega_{1,2} t + \cos 3\omega_{1,2} t]$$


- But we *also* get cross terms:

$$3c_3 [V_1 V_2^2 \underbrace{\cos \omega_1 t \cos^2 \omega_2 t}_{\frac{1}{2}[1+\cos 2\omega_2 t]} + V_1^2 V_2 \underbrace{\cos^2 \omega_1 t \cos \omega_2 t}_{\frac{1}{2}[1+\cos 2\omega_1 t]}]$$

$$= 3c_3 (V_1 V_2^2 [\frac{1}{2} \cos \omega_1 t + \frac{1}{4} \cos(2\omega_2 \pm \omega_1)t] + V_1^2 V_2 [\frac{1}{2} \cos \omega_2 t + \frac{1}{4} \cos(2\omega_1 \pm \omega_2)t])$$
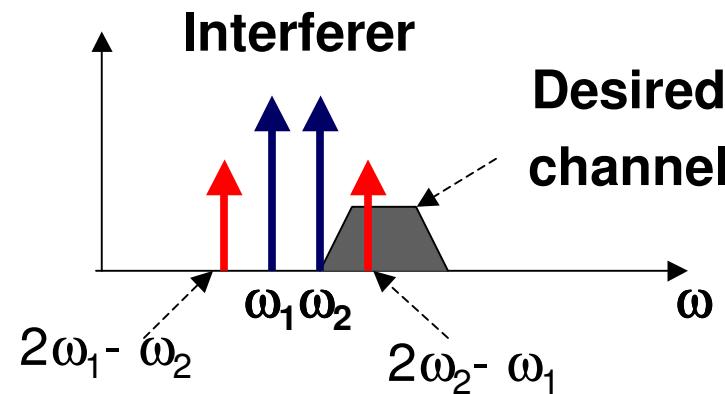
# Third-order intermodulation (cont.)

$$3c_3(V_1V_2^2[\frac{1}{2}\cos\omega_1t + \frac{1}{4}\cos(2\omega_2 \pm \omega_1)t] + V_1^2V_2[\frac{1}{2}\cos\omega_2t + \frac{1}{4}\cos(2\omega_1 \pm \omega_2)t])$$



- If  $\omega_1 \approx \omega_2$  then  $2\omega_1 - \omega_2 \approx 2\omega_2 - \omega_1 \approx \omega_1 \approx \omega_2$ .
- Unlike a 2<sup>nd</sup>-order nonlinearity, which creates in-band IM only if the system is wideband, a cubic nonlinearity can create in-band IM even in narrowband systems.

# IM3 definition

- The  $\cos(2\omega_1 \pm \omega_2)t$  and  $\cos(2\omega_2 \pm \omega_1)t$  terms are third-order intermodulation distortion terms.
- The normalized third-order IM is defined with two input tones of equal amplitude:

$$V_1 = V_2 = V_i$$

$$IM3 = \frac{\text{amplitude of the intermod}}{\text{amplitude of the fundamental}} = \frac{3}{4} \frac{c_3}{c_1} V_i^2$$

- The following relationships hold:

$$IM3 = 3HD3; \quad IM3|_{dB} = HD3|_{dB} + 9.5dB$$

# IP2

- The fundamental term increases linearly with the input signal:

$$V_o = c_1 V_i$$


- On a log scale the input-output curve has unit slope.

- The second-order IM term is proportional to the square of the input signal

$$V_o = c_2 V_i^2$$

- On a log scale the input-intermod curve thus has a slope of 2.
- IP2 is the **extrapolated** intercept point between the fundamental term and the second-order IM term.
  - At IP2 we have IM2=0dBc
  - When IP2 is known we can back-calculate IM2 at any other power.
    - For each dB input power drop, IM2 drops a dB:

$$IM2(dB) = P_{in}(dB) - IIP2(dB)$$

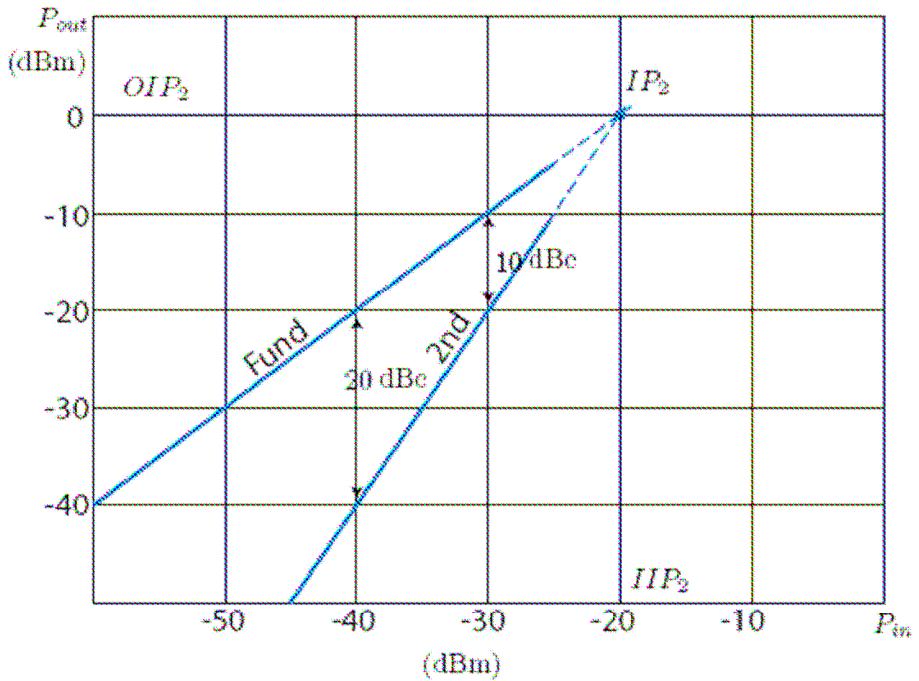


# IP3

- The fundamental term (still) increases linearly with input signal.
- The third-order IM term is proportional to the cube of the input signal:

$$V_o = \frac{3}{4} c_3 V_i^3$$

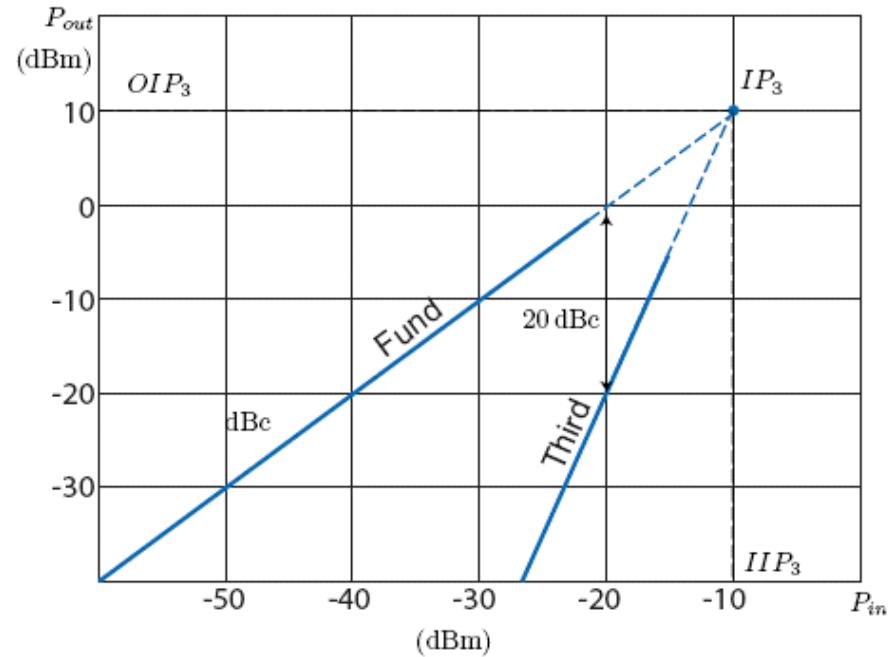- On a log scale the input-intermod curve thus has a slope of 3.
- IP3 is the **extrapolated** intercept point between the fundamental term and the third-order IM term.
  - At IP3 we have IM3=0dBc
  - When IP3 is known we can back-calculate IM3 at any other power.
    - For each dB input power drop, IM3 drops by 2dB:



$$IM3(dB) = 2[P_{in}(dB) - IIP3(dB)]$$

# IP3 (cont.)

- We can calculate the IP3 from the cubic non-linearity coefficient:

$$V_o|_{IP3} = \left| \frac{3}{4} c_3 V_i^3 \right| = |c_1 V_i| \Rightarrow V_{i,ip3} = \sqrt{\frac{4}{3} \left| \frac{c_1}{c_3} \right|}$$

- Notice that this calculation is correct even if other higher-order nonlinearities exist.
  - Remember IP3 is by definition an *extrapolation*. If we look at small enough signal levels, the cubic term would dominate the odd-order nonlinearity.

# Example 1

- Suppose an amplifier has a small-signal power gain of 12dB, OIP3=13dBm and OIP2=30dBm. What are IM2 and IM3 at Pin=-10dBm and Pin=-100dBm?

$$IIP2 = OIP2 - G = 30 - 12 = 18 \text{ dBm}$$

$$IIP3 = OIP3 - G = 13 - 12 = 1 \text{ dBm}$$

$$IM2 \Big|_{-10 \text{ dBm}} = -10 - IIP2 = -28 \text{ dBc}$$

$$IM3 \Big|_{-10 \text{ dBm}} = 2 * (-10 - IIP3) = -22 \text{ dBc}$$

$$IM2 \Big|_{-100 \text{ dBm}} = -100 - IIP2 = -118 \text{ dBc}$$

$$IM3 \Big|_{-100 \text{ dBm}} = 2 * (-100 - IIP3) = -202 \text{ dBc}$$

## Example 2

- In the previous example what is THD at Pin=-10dBm?  
Assume the amplifier has only square and cubic nonlinearities.


$$IM\ 2 = HD2 + 6 \Rightarrow HD2|_{-10\text{dBm}} = -28 - 6 = -34\text{dB} = 10^{-34/20} = 0.02$$

$$IM\ 3 = HD3 + 9.5 \Rightarrow HD3|_{-10\text{dBm}} = -22 - 9.5 = -31.5\text{dB} = 10^{-31.5/20} = 0.027$$


$$THD = \sqrt{HD2^2 + HD3^2} = \sqrt{0.02^2 + 0.027^2} = 0.034 = -29.4\text{dBc}$$
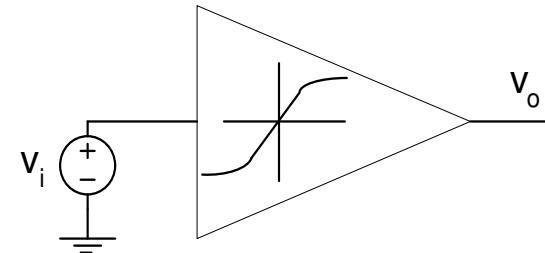
# IP3 measurement


- We can measure IP3 with a single two-tone test!
- Let  $v_i = V_1 \cos \omega_1 t + V_2 \cos \omega_2 t$   
 $V = V_1 = V_2$
- Choose  $\omega_1 \sim \omega_2$  in the middle of the operating frequency range.
- Now can run a transient simulation and take the FFT of the output to get:



# IP3 measurement (cont.)

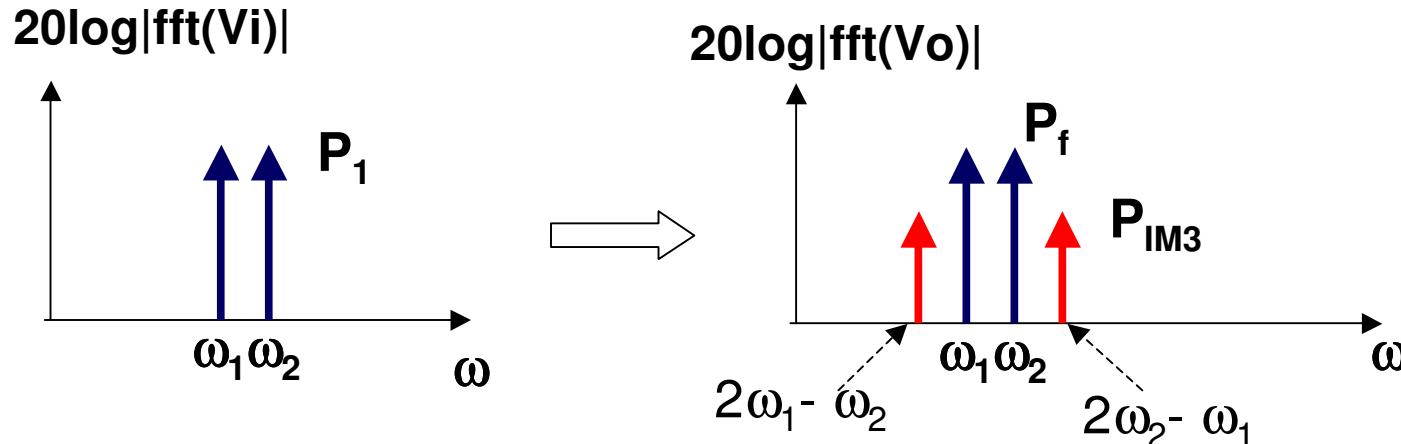

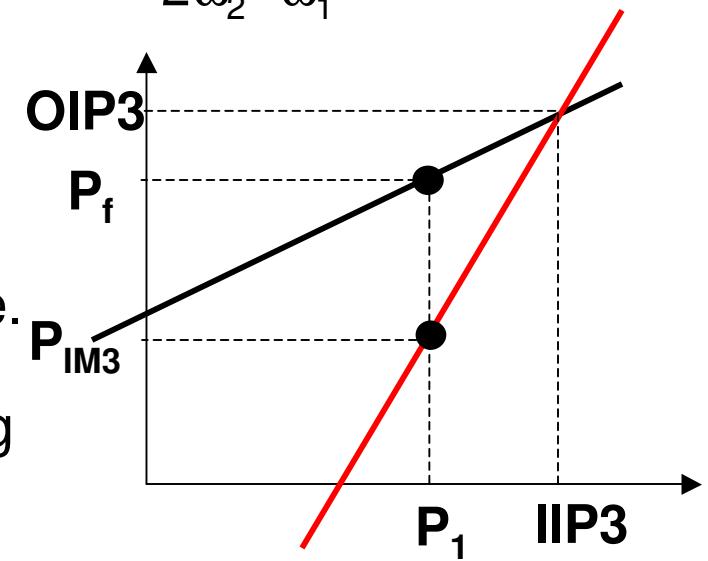- Now we can use  $P_1$ ,  $P_f$  and  $P_{\text{IM}3}$  to estimate IP3.
- Remember the fundamental output is linear in input power, so that the log Pout-Pin curve is a line with unit slope.
- The IM3 term is proportional to the cube of the input power so that the log PIM3-Pin curve is a line with slope of three.



# IP3 measurement (cont.)

- Now we can write the line equations for the fundamental and IM3 terms:

$$P_o = P_f + (P_i - P_1)$$

$$P_{o,IM3} = P_{IM3} + 3(P_i - P_1)$$

- IP3 is defined at  $P_o = P_{o,IM3}$ , therefore

$$OIP3 = P_f + (IIP3 - P_1) = P_{IM3} + 3(IIP3 - P_1)$$

$$IIP3 = \frac{P_f - P_{IM3} + 2P_1}{2}$$


$$OIP3 = \frac{3P_f - P_{IM3}}{2}$$

# IP3 estimation from harmonic measurement

- Remember from previous slides that:

$$V_{i,ip3} = \sqrt{\frac{4}{3} \left| \frac{c_1}{c_3} \right|}$$

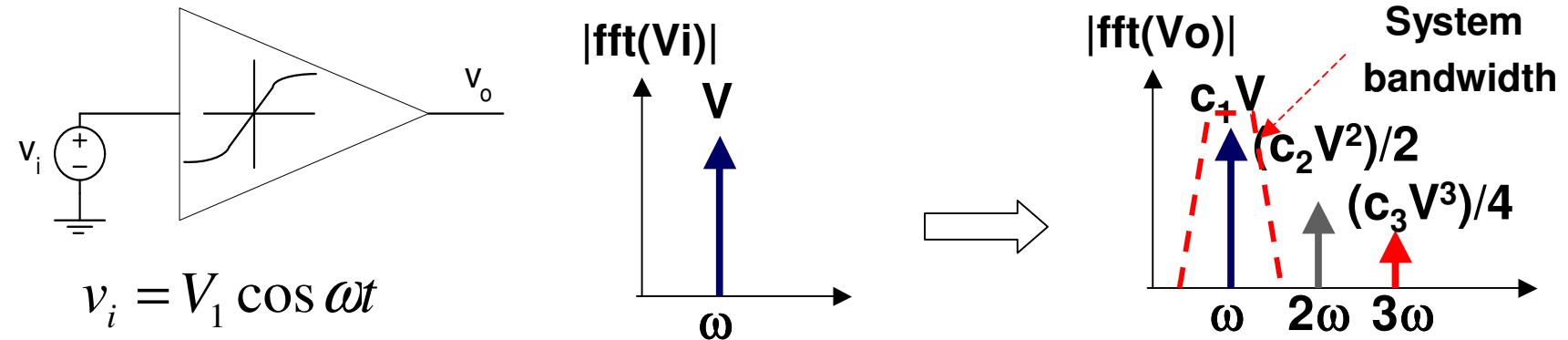- Then we should be able to use just a single tone and measure  $c_1$  and  $c_3$  by measuring the fundamental and 3<sup>rd</sup> harmonic:



- This technique works only for systems where the 3<sup>rd</sup> harmonic falls in band.

# Example 3

- You have designed an amplifier with 20dB power gain at 2GHz. The input impedance is  $50\Omega$  and the output impedance is  $200\Omega$ . Your test with 10mV tones at 1.99GHz and 2.01GHz results in an IM3 of  $100\mu V$  at the output. What are the IIP3 and OIP3 of this amplifier?
- We first need to calculate the amplitude of the fundamental signal at the output:

$$G_p = \frac{P_o}{P_i} = \frac{V_o^2 / 2R_o}{V_i^2 / 2R_i} = \frac{V_o^2}{V_i^2} \frac{R_i}{R_o} = G_v^2 \frac{R_i}{R_o} \Rightarrow G_v = \sqrt{G_p \frac{R_o}{R_i}} = \sqrt{100 \frac{200}{50}} = 20$$

$$V_{o,f} = G_v V_i = 20 * 10mV = 200mV$$

- Then IIP3 is:

$$IIP3 = \frac{P_f - P_{IM3} + 2P_i}{2} = \frac{20 \log(\frac{200mV}{100\mu V} (10mV)^2)}{2} = -6.9dBv = 0.45V$$

$$OIP3 = IIP3 * G_v = 0.45 * 20 = 9V$$

## Example 3 (cont)

- If the amplifier's 3dB bandwidth is 200MHz, then what would be HD3 for a 10mV single tone input?
- Let's first ignore the amplifier bandwidth:

$$IM3(dB) = 2[P_{in}(dB) - IIP3(dB)] = 2 * 20 \log(10mV / 0.45) = -66dBc$$

$$HD3 = IM3 - 9.5dB = -75.5dBc$$

- If we assume an *RLC* tank at the output,

$$BW = \frac{\omega_0}{Q} \Rightarrow Q = \frac{2GHz}{200MHz} = 10$$

## Example 3 (cont.)

- Now we can estimate HD3 after filtering

$$HD3 = HD3|_{\text{w/o filter}} + 10 \log \left( \frac{1}{1 + [Q(\frac{3\omega}{\omega} - \frac{\omega}{3\omega})]^2} \right)$$
$$= -75.5 - 28.5 = -104 dBc$$

# Gain at fundamental frequency

- Let's revisit the single-tone excitation case:

$$v_o = c_0 + c_1 V_i \cos(\omega t) + c_2 V_i^2 \cos^2(\omega t) + c_3 V_i^3 \cos^3(\omega t) + \dots$$

$$v_o = c_0 + c_1 V_i \cos(\omega t) + \frac{c_2 V_i^2}{2} [1 + \cos(2\omega t)] + \frac{c_3 V_i^3}{4} [3 \cos(\omega t) + \cos(3\omega t)] + \dots$$


$$v_o = \underbrace{\left[ c_0 + \frac{c_2 V_i^2}{2} \right]}_{\text{gain at } \omega} + \underbrace{\left[ c_1 + \frac{c_3 V_i^2}{4} \right]}_{\text{gain at } \omega} V_i \cos(\omega t) + \frac{c_2 V_i^2}{2} \cos(2\omega t) + \frac{c_3 V_i^3}{4} \cos(3\omega t) + \dots$$

- It appears that gain at the fundamental frequency is now a function of the signal level!
- Depending upon the polarity of  $c_3$  we can get gain *compression* or gain *expansion* (peaking) at the fundamental frequency.

$$\left. \frac{v_o}{v_i} \right|_{\omega} = c_1 + \frac{3V_i^2}{4} c_3$$
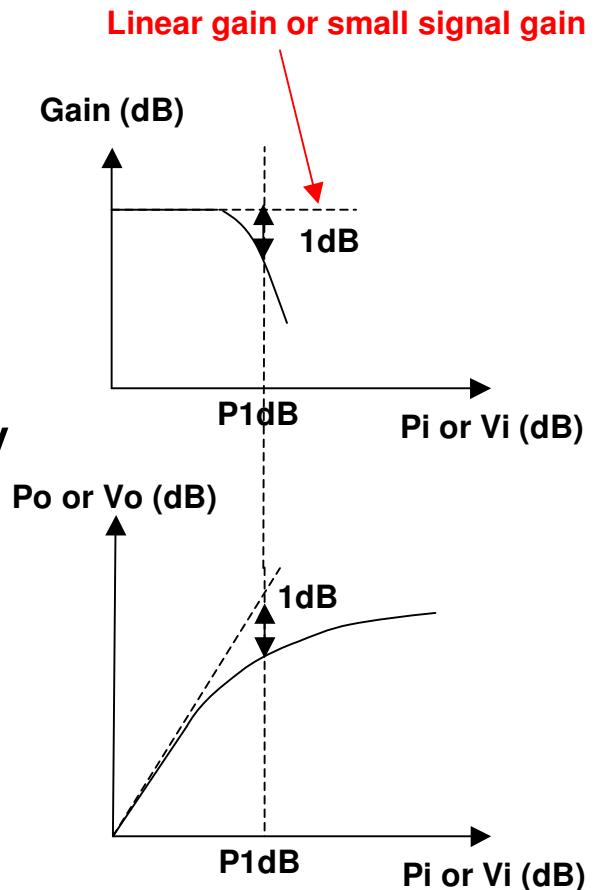
# 1dB compression point

- The 1dB compression point by definition is the power/signal level at which the large signal gain (i.e.,  $P_o/P_i$ ) at the fundamental frequency is reduced by 1dB.
- Remember that only odd-order distortions result in gain change at the fundamental frequency.



# 1dB compression point (cont.)

- If cubic nonlinearity is the only odd-order nonlinear term then we can calculate the 1dB compression point:

$$20\log(c_1V_i + \frac{3}{4}c_3V_i^3) = 20\log(c_1V_i) - 1dB$$


$$1 + \frac{3}{4} \frac{c_3}{c_1} V_i^2 = 0.89 \Rightarrow V_{i,1dB} = \sqrt{0.145 \left| \frac{c_1}{c_3} \right|}$$

$$P_{1dB} = 10\log\left(\left|\frac{c_1}{c_3}\right|\right) + 10\log(0.145) = IP3 + 10\log(0.145 * 3/4)$$

$$P_{1dB} = IP3 - 9.6dB$$

- This relationship is accurate when there is only cubic nonlinearity, as is perhaps explained best graphically!

# Distortion

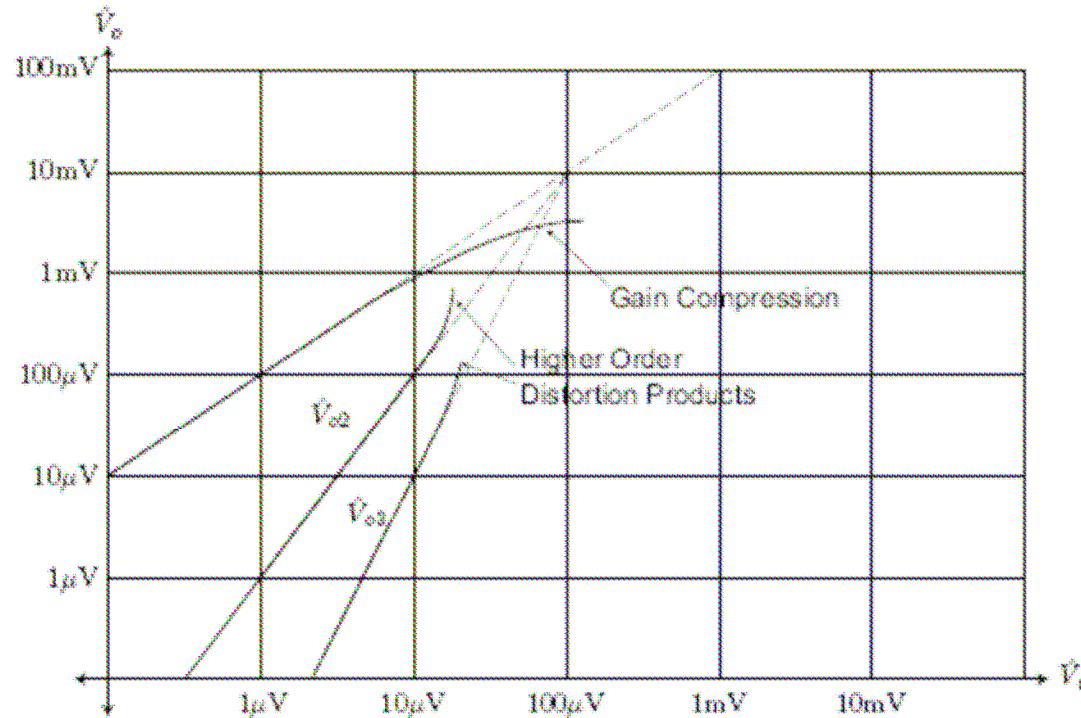


- The higher-order nonlinearities do not affect IP2 and IP3 points, but they control the 1dB compression point.

# Distortion in long-channel MOS devices

- If we ignore the output impedance:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{th})^2 = \frac{K}{2} (V_{GS} - V_{th})^2$$
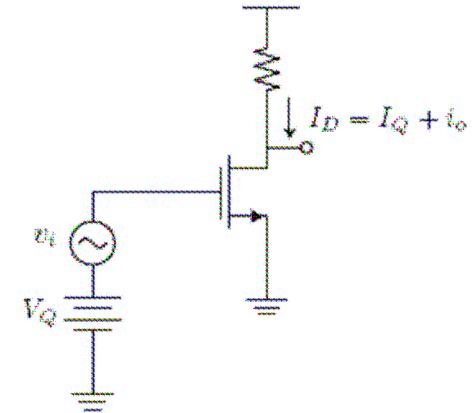
$$I_D = \frac{K}{2} (V_Q + v_i - V_{th})^2 = \underbrace{\frac{K}{2} (V_Q - V_{th})^2}_{c_0} + \underbrace{K(V_Q - V_{th})v_i}_{c_1} + \underbrace{\frac{K}{2} v_i^2}_{c_2}$$



- It seems that in long-channel devices  $IM3=0$ 
  - This cannot be true (because Murphy always wins); what are we missing?

# IM3 in “square-law” devices

- One factor we ignored is mobility degradation due to vertical field:

$$\mu_{eff} = \frac{\mu}{1 + \theta \cdot V_{OD}}$$

$$\theta \approx \frac{2 \times 10^{-9}}{t_{ox}} \text{ V}^{-1} : \text{fitting parameter}$$


$$\theta \approx 0.7 \text{ V}^{-1} \text{ for 90nm CMOS process}$$

$$V_{OD} = V_{GS} - V_{th}$$

$$I_D = \frac{1}{2} \mu_{eff} C_{ox} \frac{W}{L_{eff}} V_{OD}^2 = \frac{K}{2} \frac{V_{OD}^2}{1 + \theta \cdot V_{OD}}$$

$$\xrightarrow{\theta \cdot V_{OD} \ll 1} I_D \approx \frac{K}{2} (V_{OD}^2 - \theta \cdot V_{OD}^3) : \text{No longer a square-law device!}$$

# Blocker or jammer

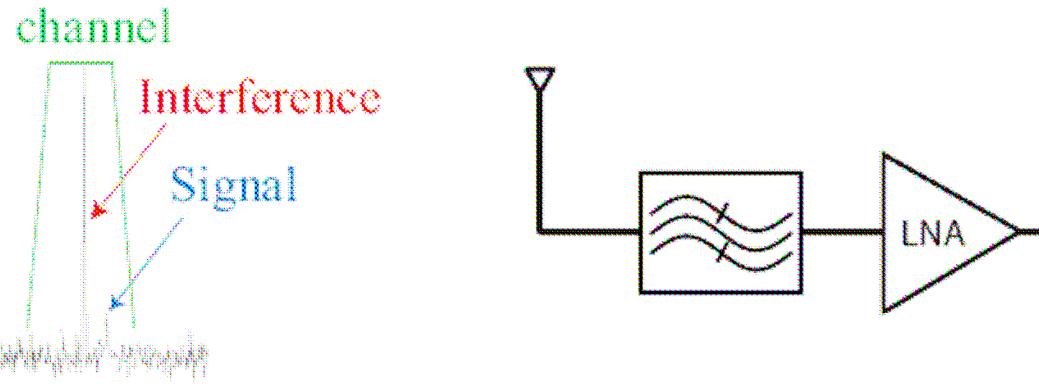

- Consider the input spectrum of a weak desired signal and a “blocker”

$$v_i = \underbrace{V_b \cos \omega_1 t}_{\text{Blocker}} + \underbrace{V_d \cos \omega_2 t}_{\text{desired}}$$

- A strong blocker reduces system gain. This “desensitization” can occur even if the interferer is at a very different frequency.
- This interfering signal is also often called a *jammer*.

# Blocking

- The linear terms do not induce any desensitization.
- Second-order terms only generate second harmonic, intermodulation, and DC terms, but no fundamental.
- A cubic nonlinearity ( $c_3 v_i^3$ ), on the other hand, *does* cause desensitization:

$$v_i^3 = V_b^3 \cos^3 \omega_1 t + V_d^3 \cos^3 \omega_2 t + 3V_d^2 V_b \underbrace{\cos^2 \omega_2 t}_{\frac{1}{2}(1+2\cos 2\omega_2 t)} \cos \omega_1 t + 3V_b^2 V_d \underbrace{\cos^2 \omega_1 t}_{\frac{1}{2}(1+2\cos 2\omega_1 t)} \cos \omega_2 t$$

- The first two terms are at the fundamental and third harmonic.
- The last two terms generate terms at  $\omega_1$  and  $\omega_2$ , as well as the intermodulation terms.
  - The third term is much smaller than the last ( $V_d \ll V_b$ ).

# Blocking (cont.)

- Blocker action, therefore, is explained by the last term:

$$\frac{3}{2} c_3 V_b^2 V_d \cos \omega_2 t$$

- In most systems  $c_3/c_1 < 0$  (compressive nonlinearity) and therefore the blocker term subtracts from the desired signal. Therefore:

$$\text{Apparent gain} = \frac{c_1 V_d + \frac{3}{2} c_3 V_b^2 V_d}{V_d} = c_1 \left( 1 + \frac{3}{2} \frac{c_3}{c_1} V_b^2 \right)$$

# Out-of-band 3dB desensitization

---

- Now we can find the blocker level that can desensitize, or simply *desense*, the amplifier by 3dB.

$$20 \log\left(1 + \frac{3}{2} \frac{c_3}{c_1} V_b^2\right) = -3 \text{dB}$$

- Therefore the power of a 3dB-desensing blocker is given by:

$$P_{OB} = P_{1\text{dB}} + 1.2 \text{dB}$$

# How can we improve linearity?


- The idea is to reduce the nonlinear coefficients compared to the linear term.
- For a long-channel MOS device we have

$$I_D = \underbrace{\frac{K}{2}(V_Q - V_{th})^2}_{c_0} + \underbrace{K(V_Q - V_{th})v_i}_{c_1} + \underbrace{\frac{K}{2}v_i^2}_{c_2}$$

- So all we need to do is to increase the overdrive voltage.
- We can also use feedback. How?

# Negative feedback review

- Negative feedback depends on large  $|af|$  (and a linear  $f$ ) to provide significant benefit.

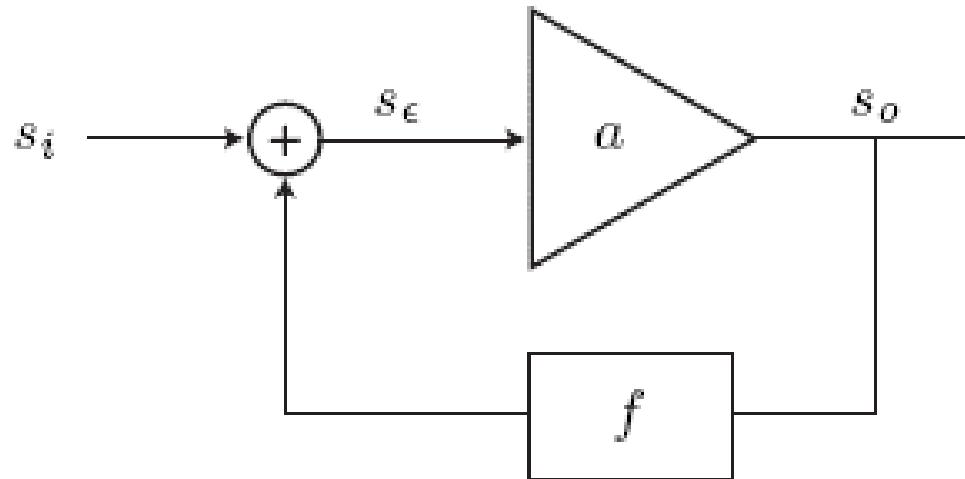

# Negative feedback review (cont.)

- If we express the output as:

$$s_o = b_1 s_i + b_2 s_i^2 + b_3 s_i^3 + \dots$$

- Then the first-order term is:

$$b_1 = \frac{a_1}{1 + a_1 f} = \frac{a_1}{1 + T}$$

## Negative feedback review (cont.)

- If we solve for the second-order term we get:

$$b_2 = \frac{a_2}{(1+a_1f)^3} = \frac{a_2}{(1+T)^3}$$

- And solving for the third-order term yields:

$$b_3 = \frac{a_3(1+T) - 2a_2^2 f}{(1+T)^5}$$

- Recall that  $b_3$  can be made zero if  $a_3(1+T) = 2a_2^2 f$

# How feedback changes HD2 and HD3

- From our previous derivation we have

$$HD2 = \frac{1}{2} \frac{b_2}{b_1} V_i = \xrightarrow{V_o = \frac{a_1}{1+T} V_i} \underbrace{\frac{1}{2} \frac{a_2}{a_1^2} V_o}_{\text{w/o feedback}} \frac{1}{(1+T)}$$

- For a given output level**  $HD2$  thus improves by  $(1+T)$ .

$$HD3 = \frac{b_3}{4b_1} V_i^2 = \underbrace{\frac{a_3}{4a_1^2} V_o^2}_{\text{w/o feedback}} \frac{1}{(1+T)} \left[ 1 - \frac{2a_2^2 f}{a_3(1+T)} \right]$$

- Note that  $HD3$  can be forced to zero and also scales by  $(1+T)$ , again **for a given output power**.

# Loop transmission effects


- These derivations show that – for equal output levels – the fractional harmonic distortion is inversely proportional to the loop transmission magnitude.
  - The larger the loop transmission, the better.
- Achieving large loop gains may be difficult at high frequencies or over large bandwidths.
- Maintaining closed-loop stability may be difficult with large loop transmissions over a large bandwidth.

# Evading limits: Feedforward

- The need for large loop gains with simple dynamics is not readily satisfied over large bandwidths or at high frequencies.
  - Negative feedback may be impractical in many cases of interest.
- An alternative to negative feedback is *feedforward*.
  - In some sense it involves “less than no feedback.”
  - No loop, so bandwidth not constrained by instability.
  - Achievable distortion reduction limited by matching.
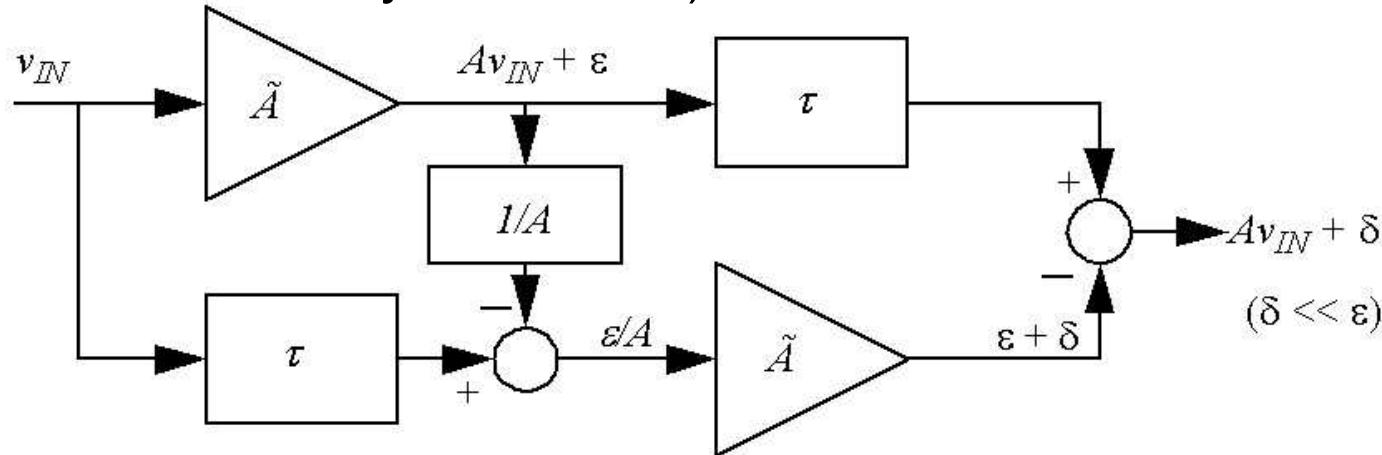
# Evading limits: Feedforward

- Invented by Harold Black in 1923 (four years before inventing electronic negative feedback).
  - Great idea, but ahead of its time (“matched vacuum tubes” is unintentionally humorous).



- Depends on two identical distorting amplifiers, plus linear attenuator and summing blocks.
  - Also need time delay elements that match amplifier delay for best broadband performance.

# Evading limits: Feedforward

- Describe each amplifier by a power series:

$$v_{out} = Av_{in} + \sum_{n=2}^{\infty} c_n v_{in}^n = Av_{in} + \varepsilon$$

- The total “error” (distortion) at the output of the first amplifier is then

$$\varepsilon = \sum_{n=2}^{\infty} c_n v_{in}^n$$


- The total error at the output of the complete amplifier is

$$\delta = \sum_{n=2}^{\infty} \frac{c_n}{A^n} \left[ \sum_{n=2}^{\infty} c_n v_{in}^n \right]^n$$

# Evading limits: Feedforward

- Note the attenuation by  $A^n$  in the error terms of the final output.
  - High-order terms quickly die off as  $n$  increases.
  - Large  $A$  helps, too.
- There is no need to satisfy a phase margin constraint, because there is no feedback loop.
  - Distortion reduction can be effective over a broad band.
  - Useful bandwidth depends on how well the delay elements track amplifier delay.

# Classic feedforward example: Cascomp

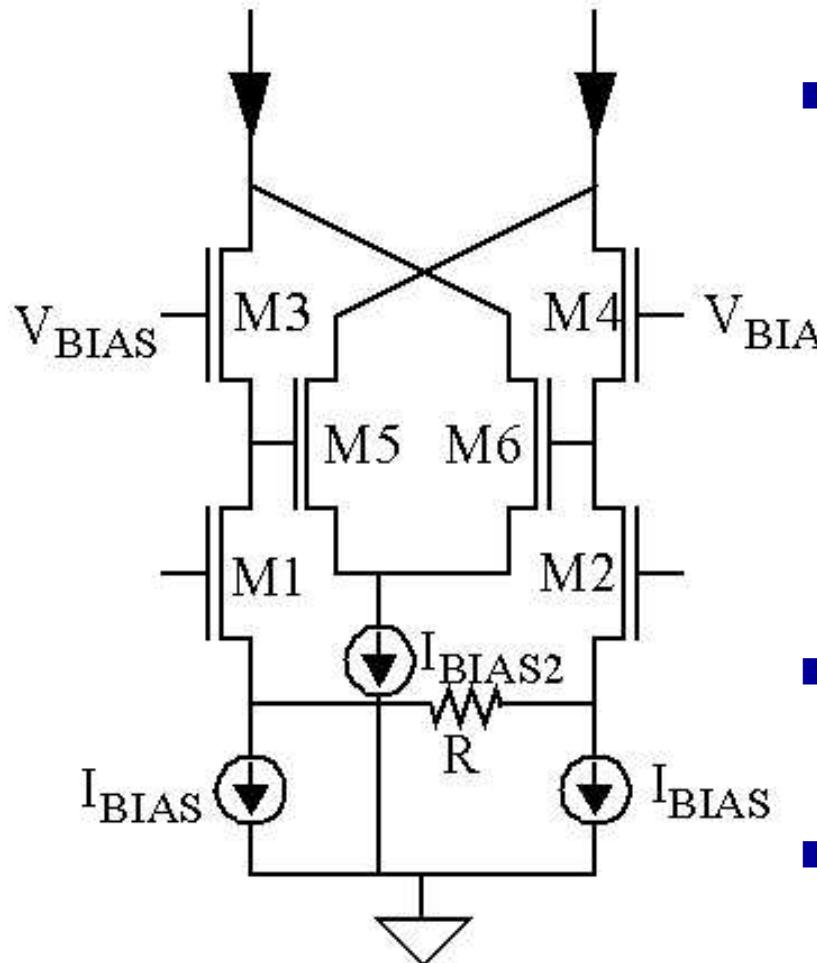

- M1-M4 are a differential cascode with emitter degeneration.
  - Perfect transconductance would put all of  $v_{in}$  across resistor.
  - Error is due to change in  $v_{gs1}$ ,  $v_{gs2}$  ( $= v_{gs3}, v_{gs4}$ ).
- M5-M6 measure the error, invert it, and feed it forward.
- Invented by Pat Quinn, used in Tektronix 2465 'scope.


# “Weak” or “soft” feedforward

---

- Many variations on the feedforward idea.
- Black’s architecture aims to reduce all distortion terms.
  - *Strong feedforward* sometimes used to describe it.
- *Weak* or *soft* feedforward targets a finite subset of distortion terms.
  - Common choice is to suppress second- or third-order distortion product.
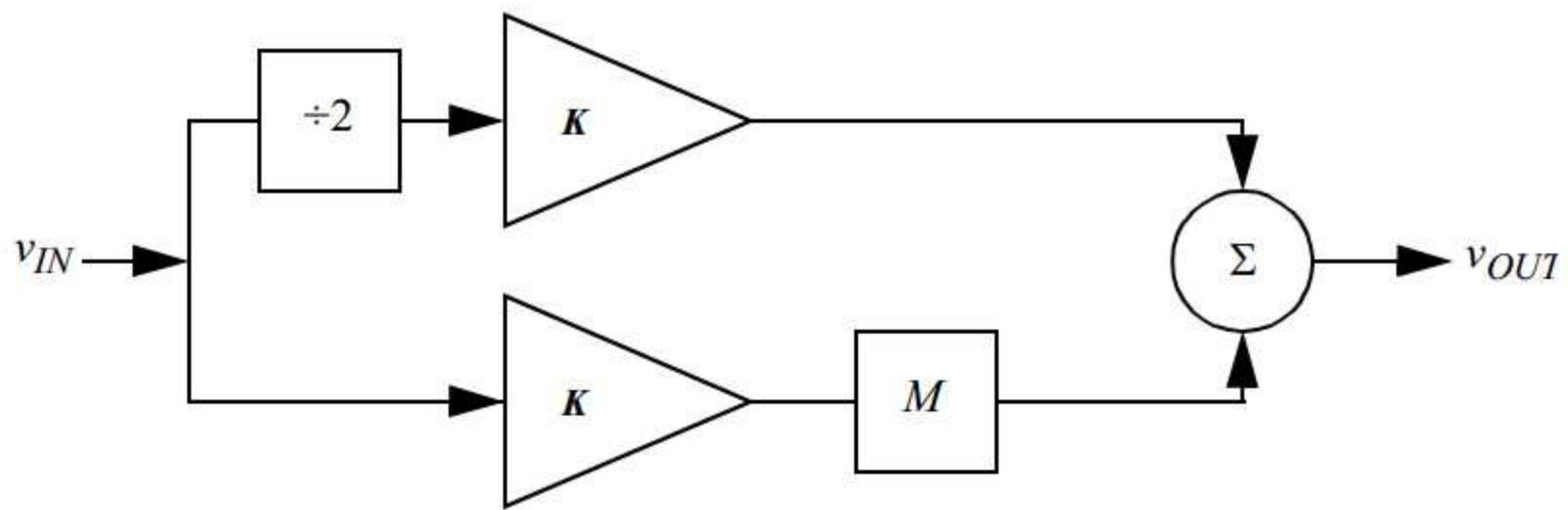
# “Weak” or “soft” feedforward

- Here's a block-diagram representation of a weak feedforward system:



- What value of  $M$  (if any) cancels out the third-order distortion term?

# When good circuits go bad

# Why RF design is hard

---

- Can't ignore parasitics:
    - $100\text{fF}$  is  $320\Omega$ @5GHz;  $1.6\Omega$ @1THz
  - Can't squander device power gain.
  - Can't tolerate much noise or nonlinearity.
    - $1\mu\text{V}$  amplitude =  $10\text{fW}$ @ $50\Omega$
  - Can't expect accurate models, but you still have to ship anyway.
-

# Traditional RF design flow

H7N9



- Wear pointy wizard hat.
- Obtain chicken.
- Design first-pass circuit.
- Utter magical Latin incantations (“*semper ubi sub ubi...omnia pizza in octo partes divisa est...e pluribus nihil*”).
- Test circuit. Weep.
- Adjust chicken. Iterate.



# Dark secrets: A partial list

---

- MOSFETs: Textbook lies
  - The two-port noise model: Why care?
    - Optimum noise figure vs. maximum gain
  - Secrets about impedance matching
  - Secrets about linearity and time invariance
  - Mixers: Deceptions, myths and confusion
  - Gain-bandwidth limits aren't
  - Strange impedance behaviors (SIBs)
-

---

# MOSFETs: What Your Textbooks May Not Have Told You

---

# The standard story

---

- “Gate-source impedance is that of a capacitor.”
  - A capacitor is lossless. A capacitive gate-source impedance therefore implies *infinite* power gain at all frequencies.
-


# Gate impedance has a real part

---

- Gate-source impedance *cannot be* purely capacitive.
    - True even if gate material is superconductive.
  - Phase shift associated with finite carrier transit speed means gate field does nonzero work on channel charge.
  - Therefore, power gain is not infinite.
  - *There is also noise associated with the dissipation.*
-
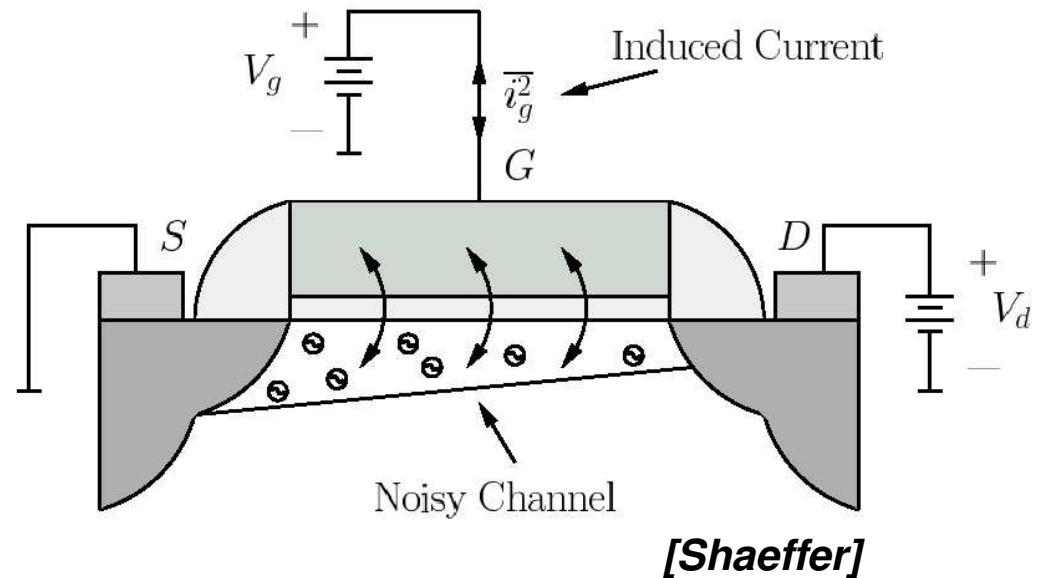
# Noisy channel charge

- Fluctuations couple capacitively to both top and bottom gates.
  - Induces noisy gate currents.
  - Bottom-gate term is ignored by most models and textbooks.



[Shaeffer]


- Gate noise current.  $\bar{i}_g^2 = 4kTB\delta \frac{(\omega C_{gs})^2}{5g_{d0}}$
- Real component of  $Y_g$ .  $\text{Re}[Y_g] = \frac{(\omega C_{gs})^2}{5g_{d0}}$

# Sources of noise in MOSFETs

---

- (Thermally-agitated) channel charge.
    - Produces current noise in both drain *and* gate.
  - Interconnect resistance.
    - Series gate resistance  $R_g$  is very important.
  - Substrate resistance.
    - Substrate thermal noise modulates back gate, augments drain current noise in some frequency range.
-

# (All) FETs and gate noise: Basic model

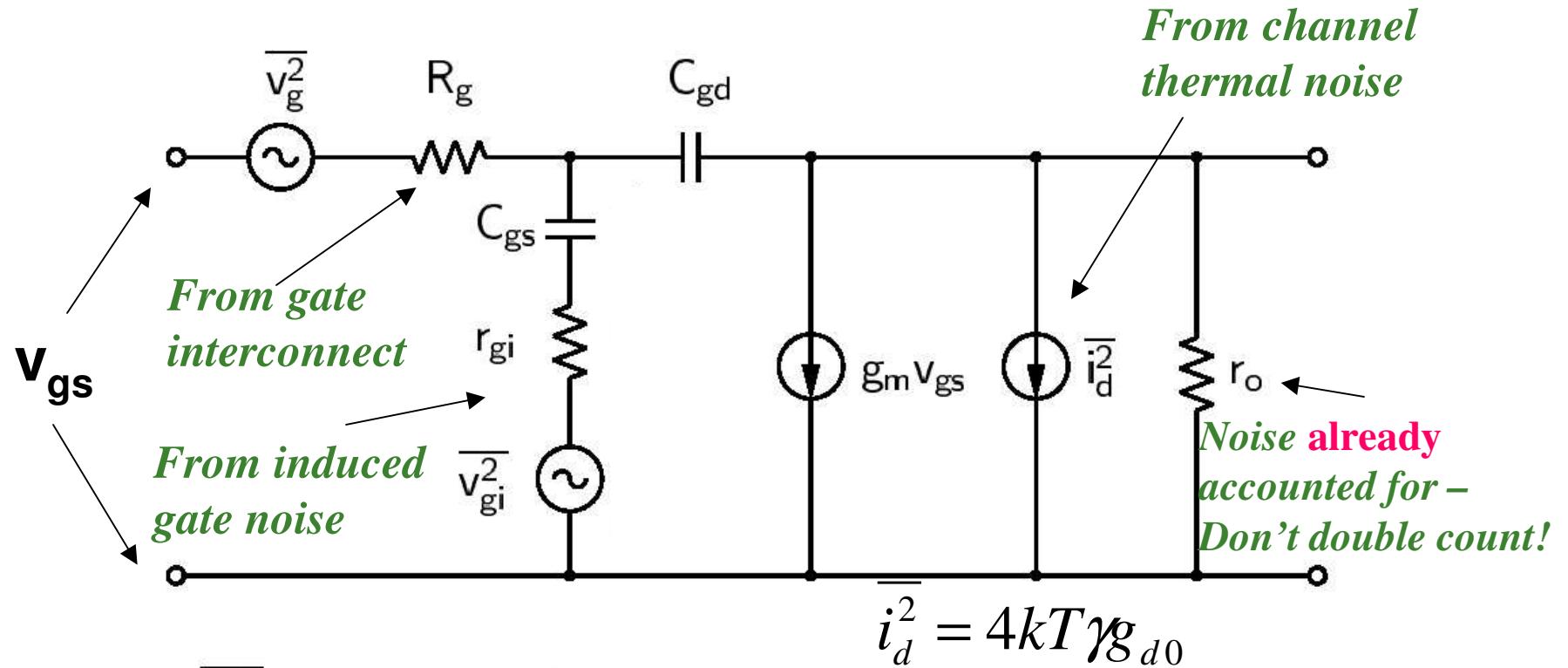

$$\overline{v_{gi}^2} = 4kTB\delta r_{gi}$$

$$r_{gi} = \frac{1}{5g_{d0}}$$

(Note the placement of  $v_{gs}$ .)



**Important: Common error is to define  $V_{GS}$  as across  $C_{GS}$  alone.**

# Dark secret: Confusing noise models

---

- Measuring drain noise at different frequencies has led to disagreement about  $\gamma$ .
  - Measurements made below  $\sim 1\text{GHz}$  may suggest both “excess” noise ( $\gamma$ ) and sensitivity to the number of substrate taps, depending on model used.
- Early fears that deep-submicron MOSFETs suffer from significant increase in  $\gamma$  not borne out.

# Substrate noise effects

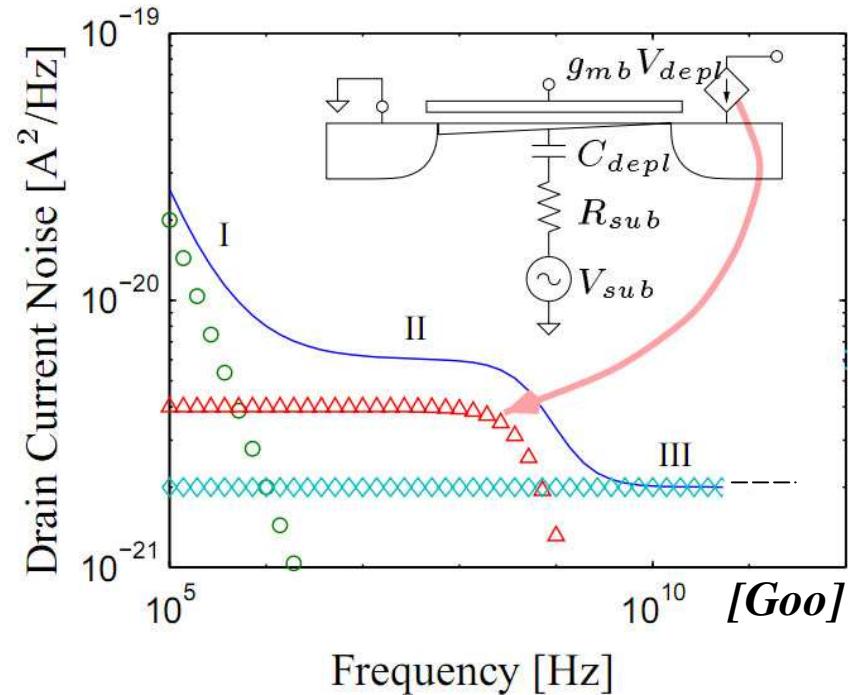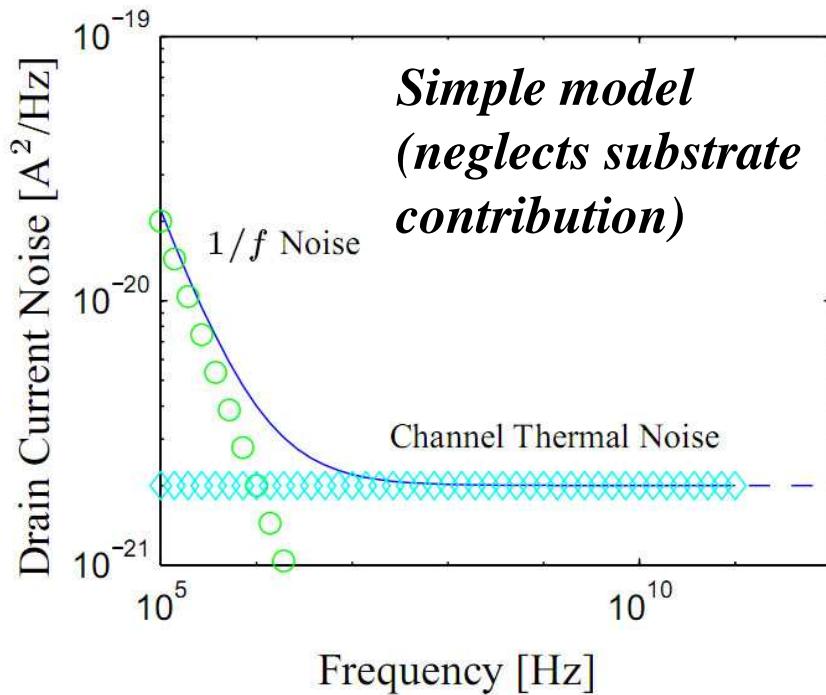


$$S_{i_d,sub} = \frac{4kT R_{sub} g_{mb}^2}{1 + (\omega R_{sub} C_{depl})^2}$$
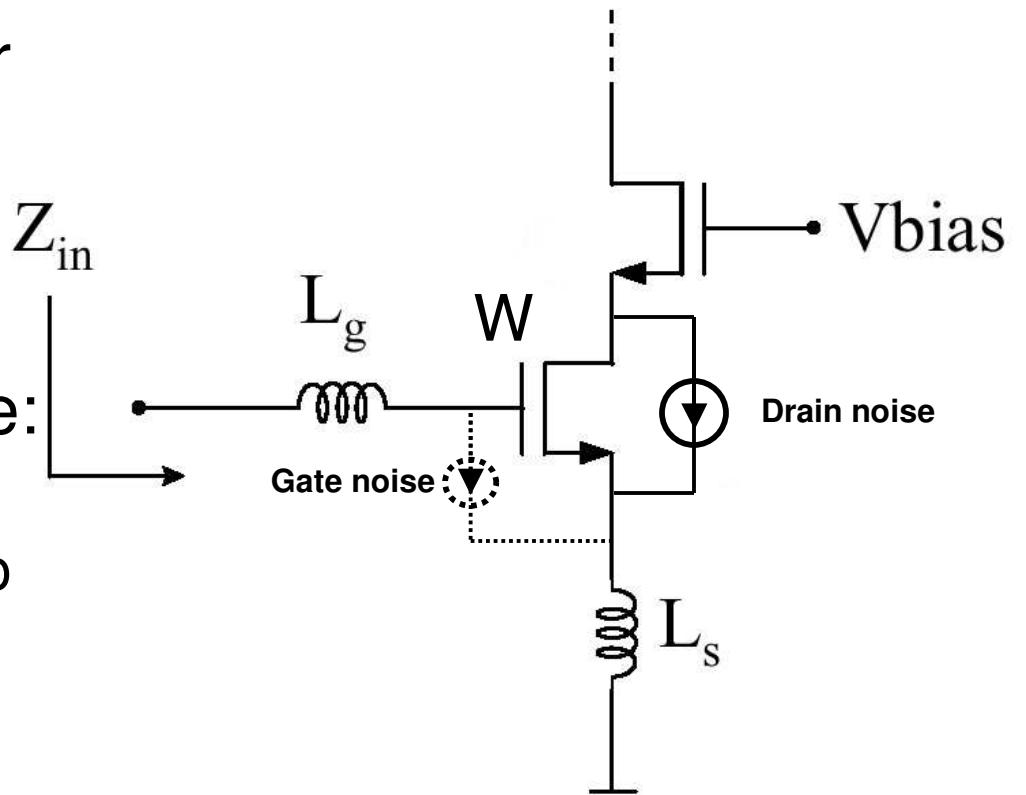
# Dark secret: Gate noise is real

- Let  $W \rightarrow 0$  while maintaining resonance and current density (for fixed  $f_T$ ).
  - Gain stays fixed.
  - $I_{bias} \rightarrow 0$ .

- If you ignore gate noise:
  - Output noise  $\rightarrow$  zero; absurd to consume zero power and provide noiseless gain.




---

# **The Two-Port Noise Model: Why?**

---

# Two-port noise model

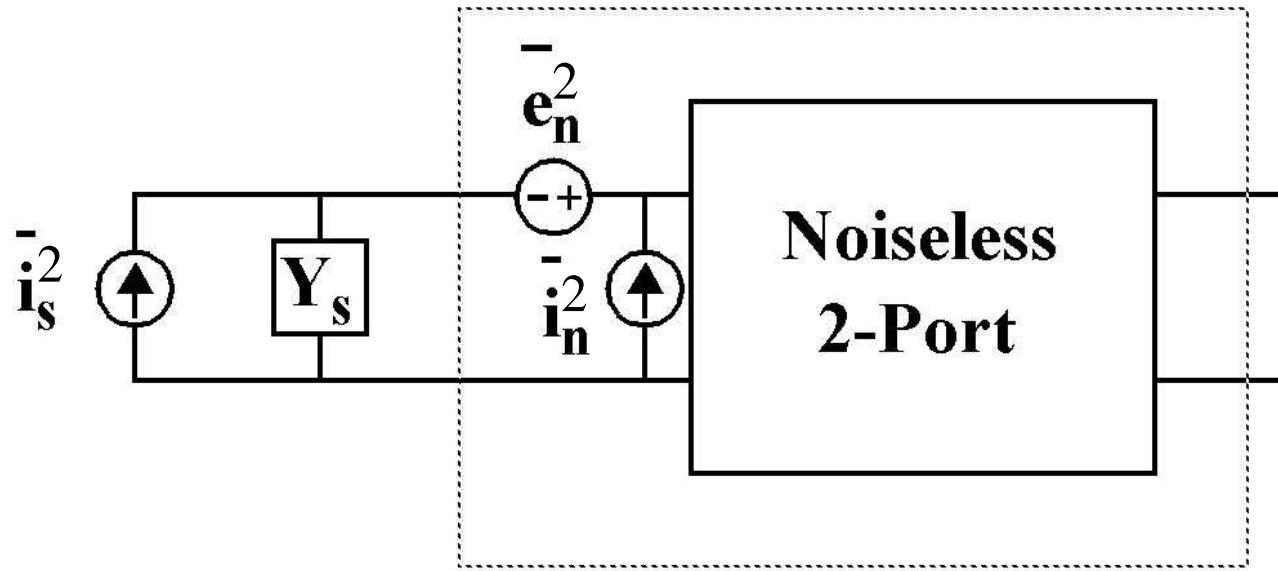

$$F = \frac{\bar{i}_s^2 + |\bar{i}_n + Y_s \bar{e}_n|^2}{\bar{i}_s^2} = 1 + \frac{\bar{i}_u^2 + |Y_c + Y_s|^2 \bar{e}_n^2}{\bar{i}_s^2}$$

- The *IRE* chose not to define  $F$  directly in terms of equivalent input noise sources. Instead:

# Two-port noise model

$$\text{Let } R_n \equiv \frac{\overline{e_n^2}}{4kT\Delta f}$$

$$G_u \equiv \frac{\overline{i_u^2}}{4kT\Delta f}$$

and

$$G_s \equiv \frac{\overline{i_s^2}}{4kT\Delta f}$$

# Conditions for minimum noise figure

$$B_s = -B_c = B_{opt}$$

$$G_s = \sqrt{\frac{G_u}{R_n} + G_c^2} = G_{opt}$$

$$F_{min} = 1 + 2R_n[G_{opt} + G_c] = 1 + 2R_n\left[\sqrt{\frac{G_u}{R_n} + G_c^2} + G_c\right].$$

$$F = F_{min} + \frac{R_n}{G_s} \left[ (G_s - G_{opt})^2 + (B_s - B_{opt})^2 \right]$$

# Dark secret: Murphy wants to hurt you

- Minimum NF and maximum power gain occur for the same source  $Z$  *only if three miracles occur simultaneously:*
  - $G_c = 0$  (noise current has no component in phase with noise voltage); *and*
  - $G_u = G_n$  (conductance representing uncorrelated current noise equals the fictitious conductance that produces noise voltage); *and*
  - $B_c = B_{in}$  (correlation susceptance happens to equal the actual input susceptance)

---

# **Dark secret: You don't always want to match impedances**

---

# Why match?

- Conjugate match maximizes power transfer.
- Terminating a  $T$ -line in its characteristic impedance makes the input impedance length-independent.
  - Also minimizes peak voltage and current along line.
- Choosing a standard impedance value (e.g.,  $50\Omega$ ) facilitates assembly, fixturing and instrumentation; it addresses *macroscopic* concerns.

# Why not match?

---

- Amplifiers generally exhibit best noise figure with a non-optimal gain match.
  - Many amplifiers are more stable or robust (in the PVT sense) when appropriately mismatched.
  - If power gain is abundant (and stability and noise are not a problem), can afford mismatch, resulting in a simpler circuit.
-

---

# **Dark secret: Circuits are neither linear nor time-invariant**

---

# LTI, LTV and all that

- A system is linear if superposition holds.
- A system is TI if an input timing shift only causes an equal output timing shift.
  - Shapes stay constant.
- If a system is LTI, it can only scale and phase-shift Fourier components.
  - Output and input frequencies are the same.
- If a system is LTV, input and output frequencies can be different, ***despite being linear***.
- If a system is nonlinear, input and output frequencies will generally differ.


# Mixers are supposed to be linear!

---

- But they are *time-varying* blocks.
    - Too many textbooks and papers say “mixers are nonlinear...” Mixers are nonlinear in the same way that amplifiers are nonlinear: *Undesirably*.
  - Mixers are noisier than LNAs for reasons that will be explained shortly. NF values of 10-15dB are not unusual.
  - Main function of an LNA is usually to provide enough gain to overcome mixer noise.
-
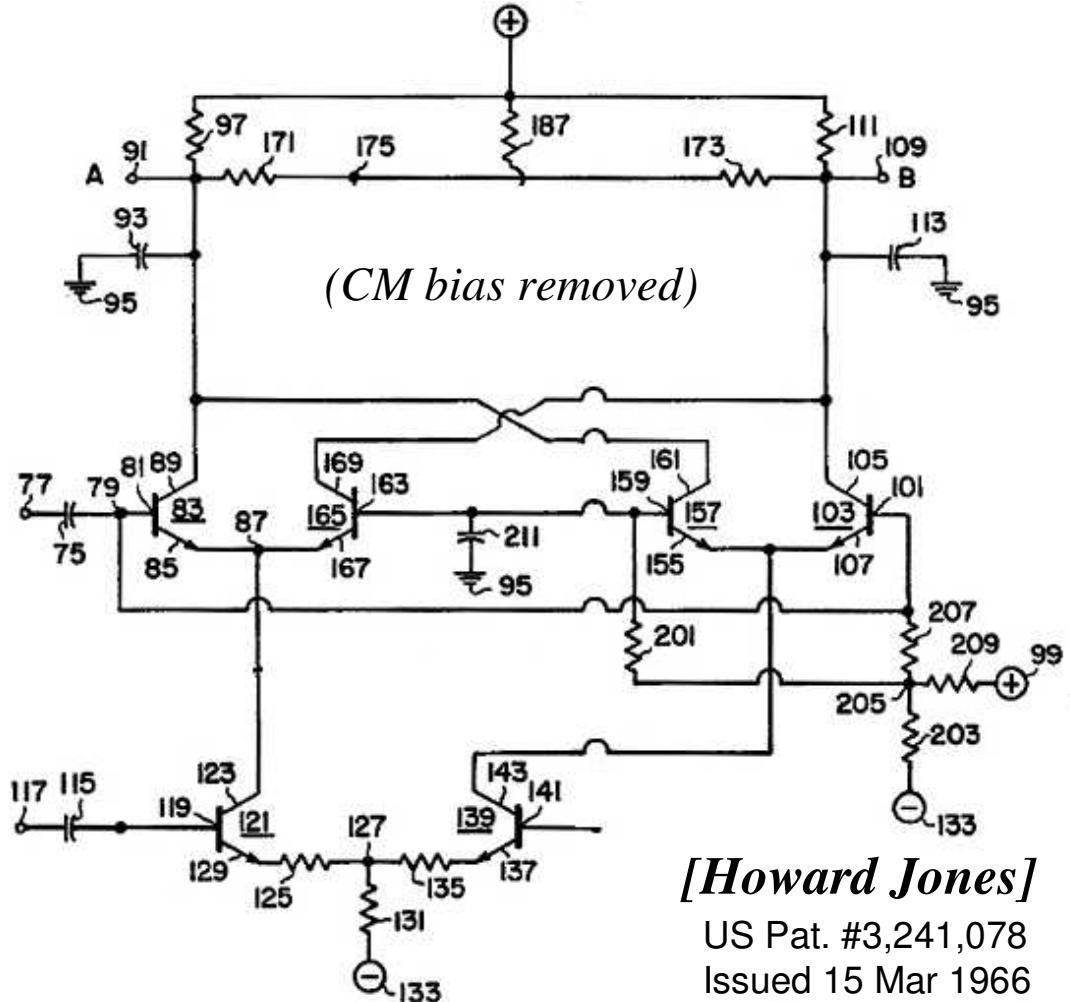
# Dark secret: Most “Gilbert” mixers aren’t

- This is a *Jones* mixer.
    - Most textbooks and papers (still) wrongly call it a Gilbert cell.
  - A true Gilbert cell is a *current-domain* circuit, and uses *predistortion* for linearity.



Thomas Lee, 17 August 2014

# The mixer: An LTV element

---

- Whether Gilbert, Jones or Smith, modern mixers depend on *commutation* of currents or voltages.
  - We idealize mixing as the equivalent of multiplying the RF signal by a square-wave LO.
    - Single-balanced mixer: RF signal is unipolar.
    - Double-balanced mixer: RF signal is DC-free.
  - Mixing is ideally *linear*: Doubling the input (RF) voltage should double the output (IF) voltage.
-


# A multiplier is an ideal mixer

- Key relationship is:

$$A \cos \omega_1 t \cos \omega_2 t = \frac{A}{2} [\cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t]$$

- Can be thought of as an amplifier with a time-varying amplification factor (e.g., term in blue box, above).

# Sources of noise in mixers

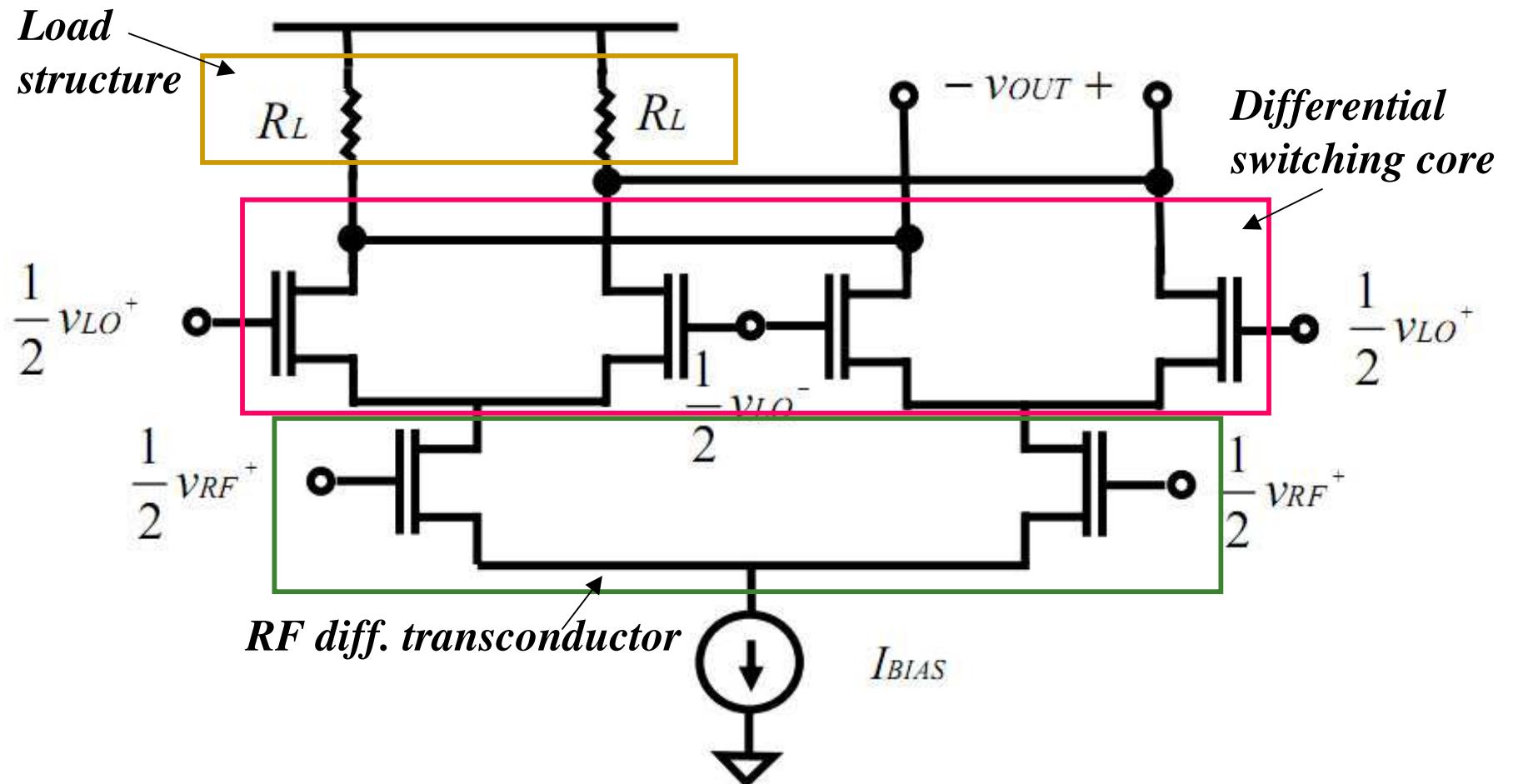

# Mixer noise

---

- Load structure is at the output, so its noise adds to the output directly; it undergoes no frequency translations.
    - If  $1/f$  noise is a concern, use PMOS transistors or poly resistor loads.
  - Transconductor noise appears at same port as input RF signal, so it translates in frequency the same way as the RF input.
-

# Dark secret: Switching noise can *dominate*

---

- Instantaneous switching not possible.
  - Noise from switching core passing through linear region can actually *dominate*.
  - Common-mode capacitance at tail nodes of core can reduce effectiveness of large LO amplitudes.
- Periodic core switching is equivalent to windowed sampling of core noise at (twice) the LO rate.
  - Frequency translations occur due to this self-mixing.


# Noise contribution of switching core

---

- As switching transistors are driven through the switching instant, they act as a differential pair for a brief window of time  $t_s$ .
  - During this interval, the switching transistors transfer their drain noise to the output.
  - Changing drain current implies a changing PSD for the noise; it is cyclostationary.
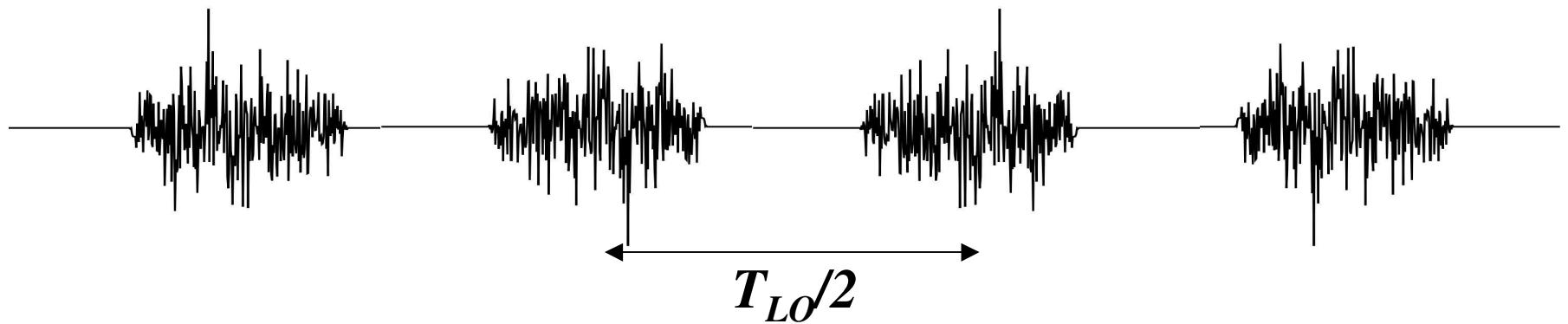
# Noise contribution of switching core


- The noise contributed by the switching core appears roughly as follows:



- Mathematically equivalent to multiplying stationary noise by a shaped pulse train of fundamental frequency  $2f_{LO}$ .
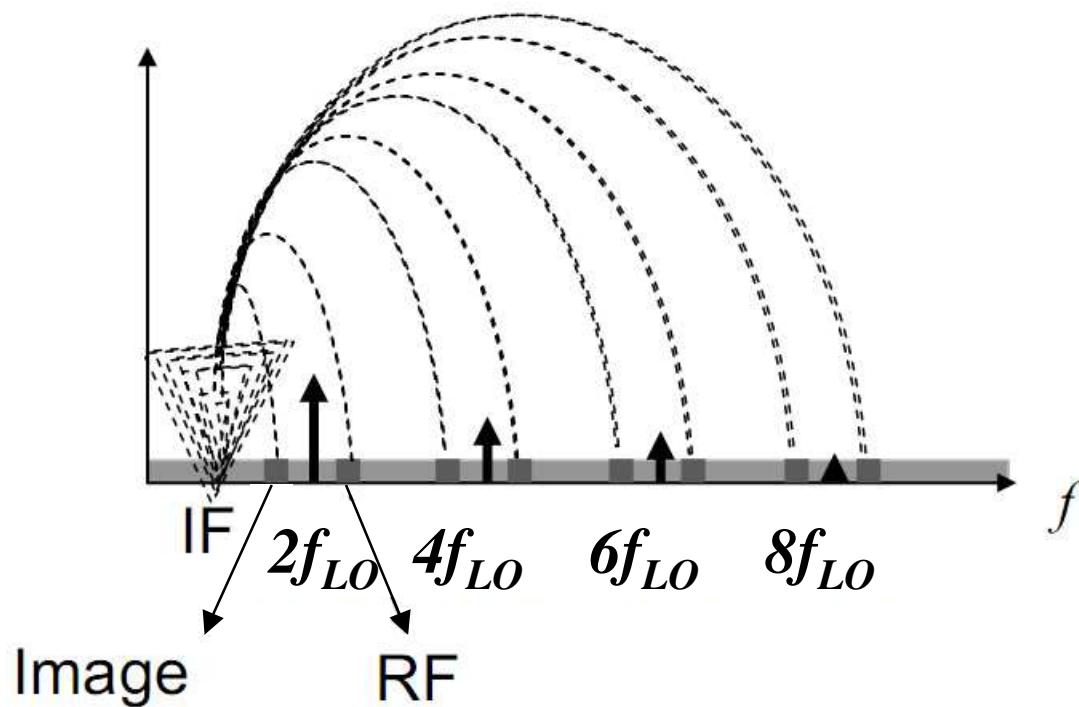
# Noise contribution of switching core

- Noise at  $2nf_{LO} +/- f_{IF}$  will therefore translate to the IF. This noise folding partly explains the relatively poor noise figure of mixers.



# Terrovitis mixer noise figure equation

- A simplified analytical approximation for the SSB noise figure of a Jones mixer is

$$F_{SSB} \approx \frac{\alpha}{c^2} + \frac{2\gamma g_m \alpha + 4\gamma \bar{G} - G_L}{c^2 g_m^2 R_S}$$

*important*

- Here,  $g_m$  is the transconductance of the bottom differential pair;  $G_L$  is the conductance of the load;  $R_S$  is the source resistance, and  $\gamma$  is the familiar drain noise parameter.
  - See [Terrovitis] for more complete version.

# Terrovitis mixer noise figure equation

- The parameter  $\bar{G}$  is the time-averaged transconductance of each pair of switching transistors. For a plain-vanilla Jones mixer,

$$\bar{G} \approx \frac{2I_{BIAS}}{\pi V_{LO}}$$

- The parameter  $\alpha$  is related to the sampling aperture, and has an approximate value

$$\alpha \approx 1 - \frac{4}{3} t_s f_{LO}$$

# Terrovitis mixer noise figure equation

- The parameter  $c$  is directly related to the effective aperture, and is given by

$$c \approx \frac{2}{\pi} \left[ \frac{\sin(\pi t_s f_{LO})}{\pi t_s f_{LO}} \right]$$

- This parameter asymptotically approaches  $2/\pi$  in the limit of infinitely fast switching.

---

# **Extreme Circuit Design:**

## ***Amplifier Tricks***

---

# The myth of G-BW limits

- Most circuit design textbooks convey the belief that there is a “gain-bandwidth limit.”
  - Given certain assumptions, yes, G-BW is limited, but that limit isn’t fixed...so it’s not quite as hard a limit.
- Let’s see what happens if we violate those “certain assumptions.”


# Single-pole common-source

---

- *Everyone* knows that the gain is  $g_m R_L$ , -3dB bandwidth is  $1/R_L C_L$ , so GBW is just  $g_m / C_L$ .
  - Single-pole systems trade gain for bandwidth directly.
- But what about higher-order systems? Can we use the additional degrees of freedom to do better?
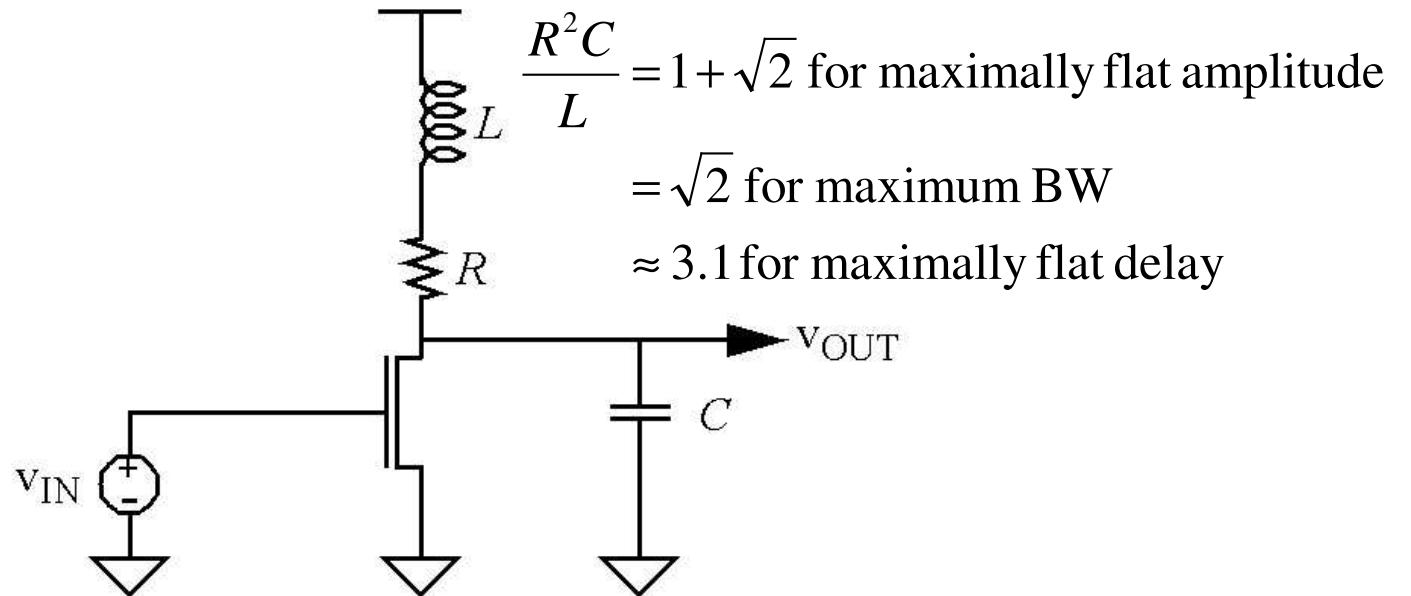
# Shunt peaking

- Ancient idea – dates back to the 1930s.




- Adding one low- $Q$  inductor nearly doubles BW.
  - 1.85x max. boost; 1.72x boost @ max. flat amplitude,  
1.6 boost for max. flat delay.
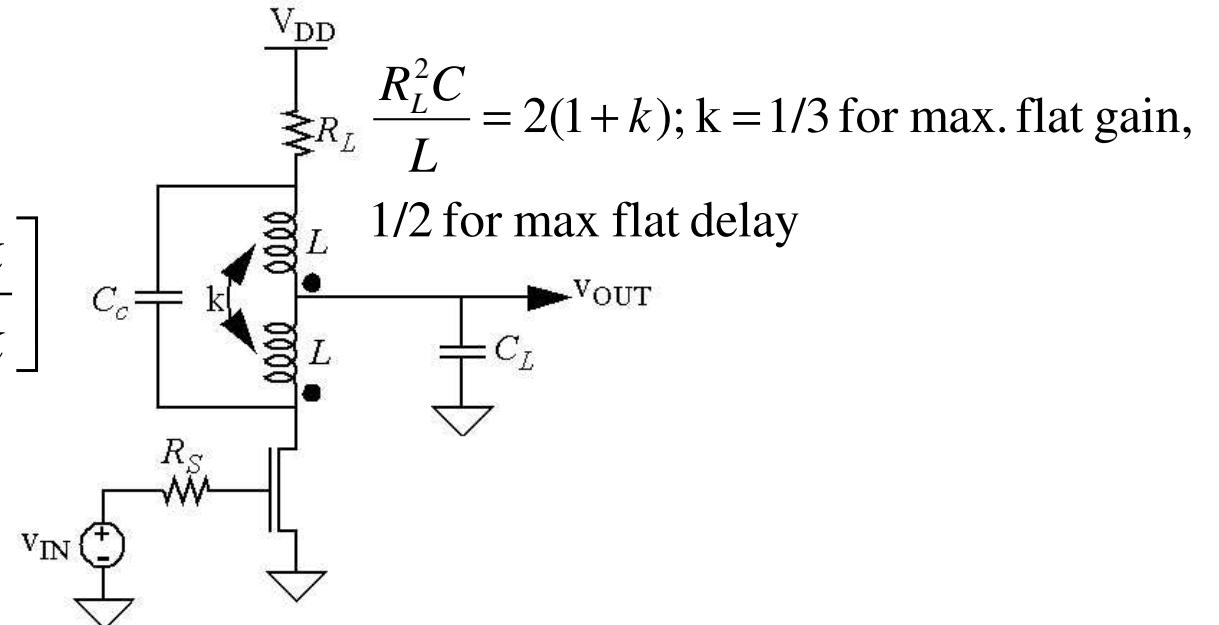
# Bridged T-coil


- Used extensively in Tektronix ‘scopes.

$$C_C = \frac{C_L}{4} \left[ \frac{1-k}{1+k} \right]$$




- A small capacitor and low- $Q$  transformer nearly triples BW.
  - ~3x max boost; 2.83x boost @ max. flat delay.

# Bridged T-coils in Tek 454

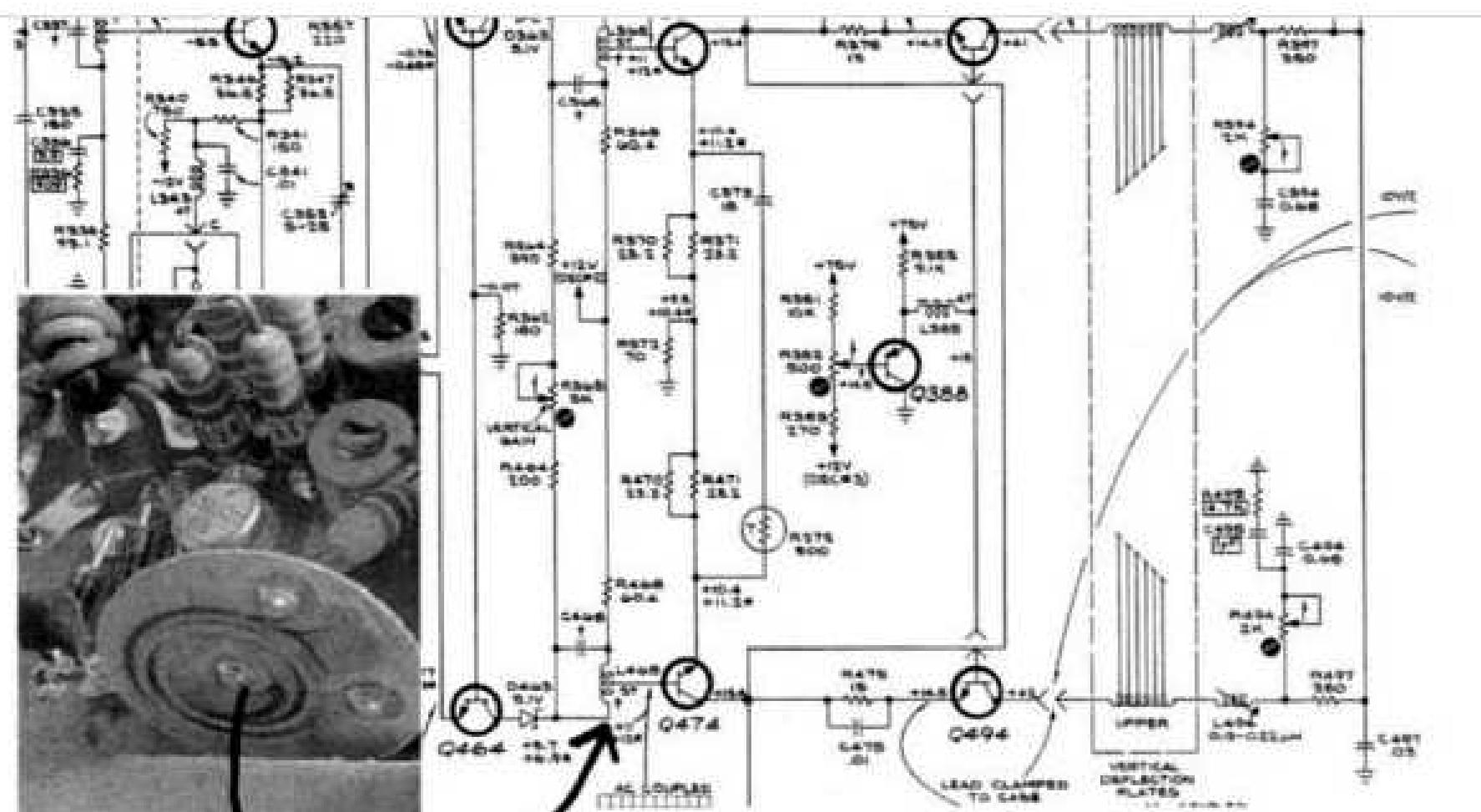

## **1967; last, fastest (150MHz) Tek scope using all discretes**


# $f_T$ isn't a process limit

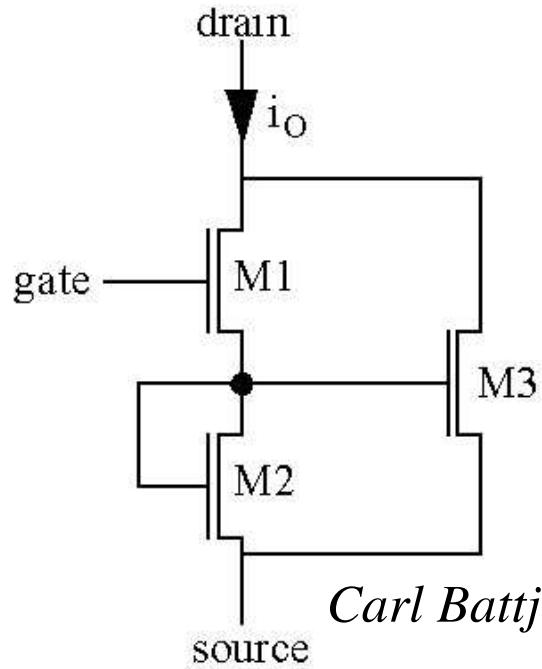

Carl Battjes, Tektronix, US Pat. 4236119


- $\omega_T = g_m/C_{in}$ , to an approximation. The Battjes doubler reduces  $C_{in}$  to provide a 1.5x boost in  $f_T$ . Used with T-coils in Tek 7904 scope to get 500MHz system BW using 3GHz transistors.

# Differential, cascaded $f_T$ doubler

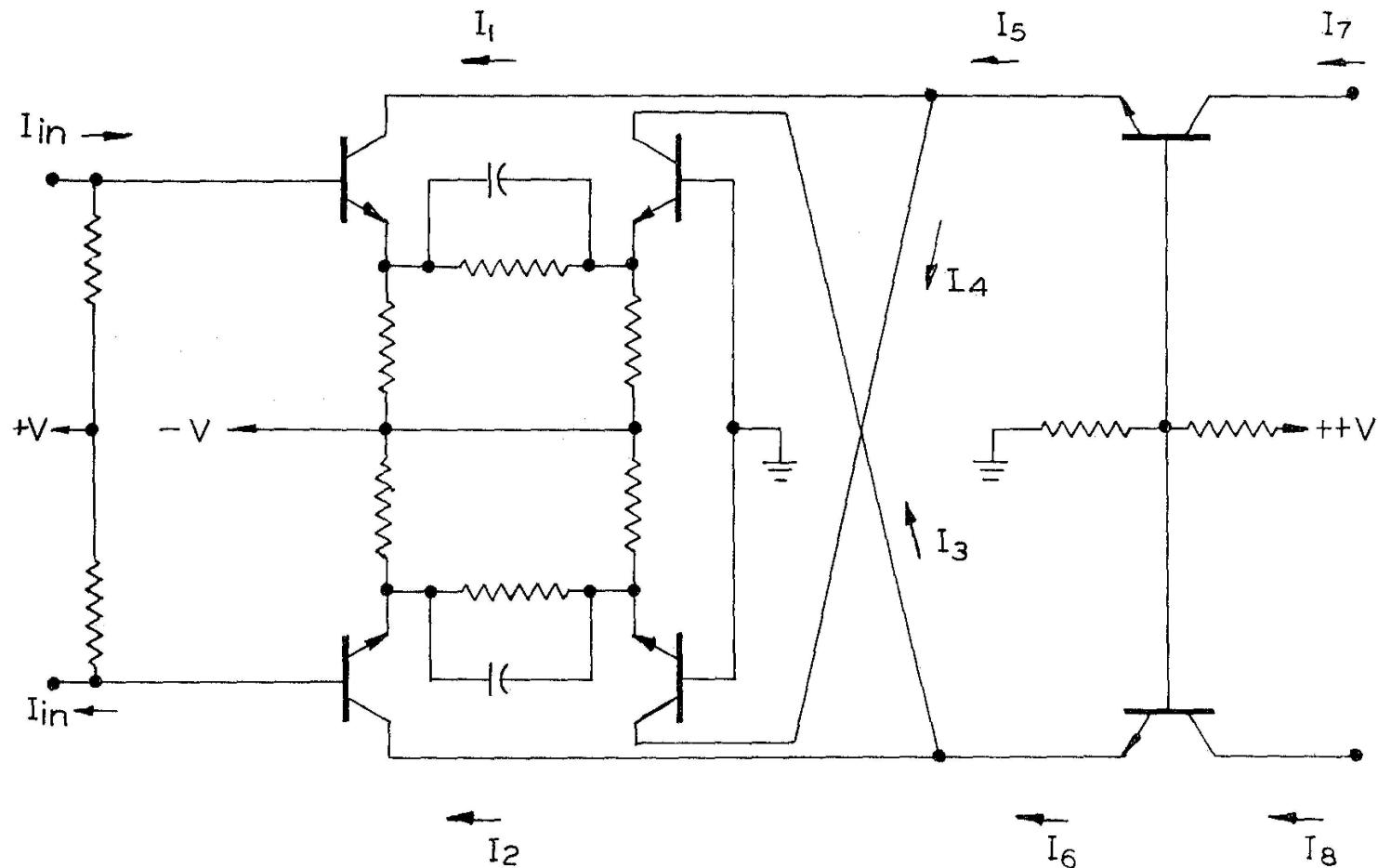

*Carl Battjes, Tektronix, US Pat. 3633120*

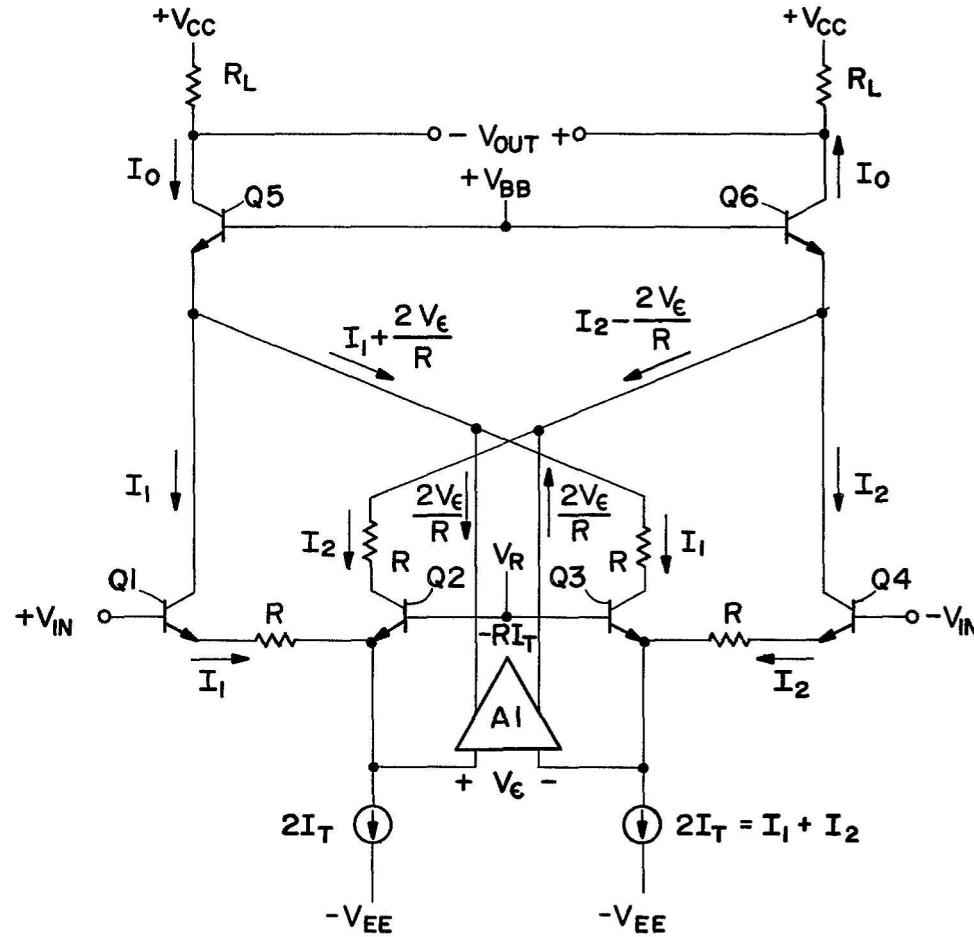
# Diff., cascoded doubler w/thermal comp.



*Einar Traa, Tektronix, US Pat. 4267516*

# The distributed amplifier

- Used extensively in Tektronix ‘scopes.

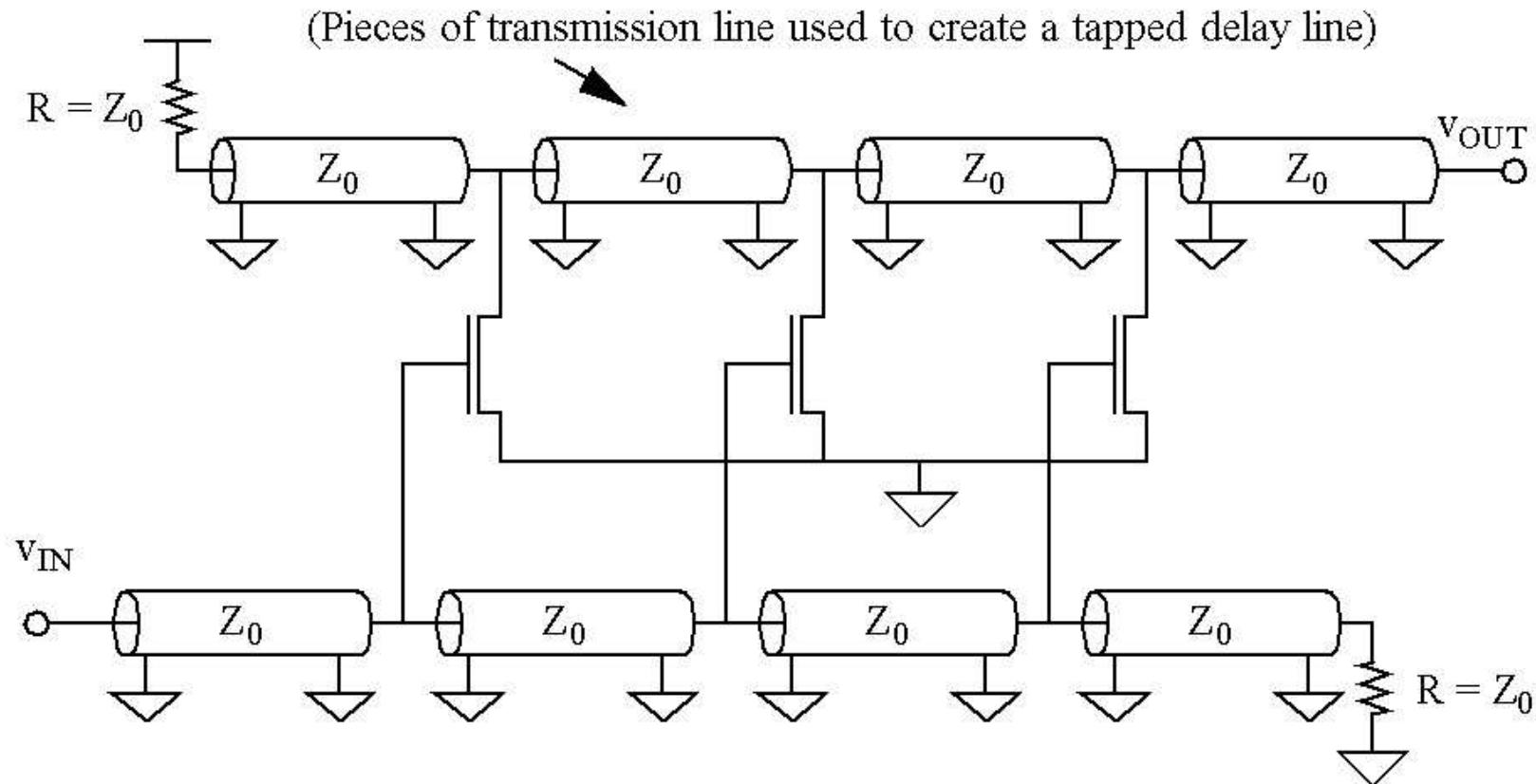

# The message?

- More poles = more degrees of freedom = greater ability to effect desirable tradeoffs.
- Extend gain-bandwidth tradeoff to gain-bandwidth-*delay* tradeoff.
  - Delay is frequently unimportant, so trading it for GBW is possible in many practical cases.
  - $G\text{-}BW\text{-}T_D$  tradeoff possible *only* if you can create excess delay – you can't trade what you don't have. In turn, creating delay over large BW implies many poles.

---



# **Extreme Circuit Design:**

## ***Strange Impedance Behaviors***

## **(SIBs)**
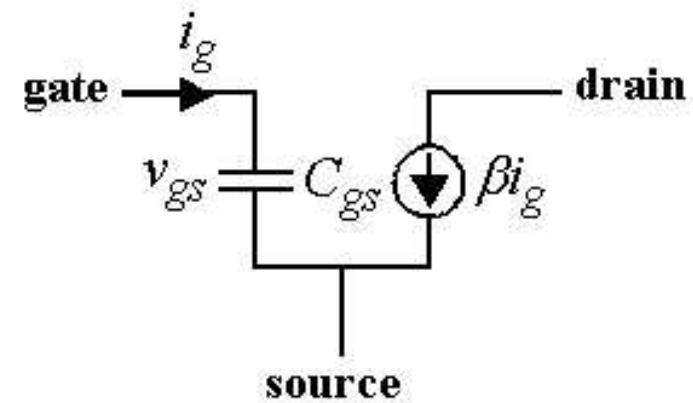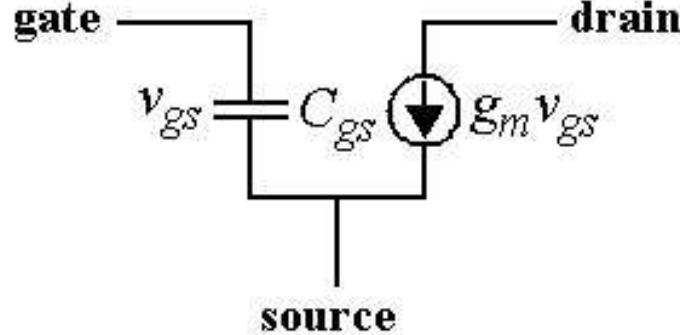
# First: Some simple transistor models

- Can use *either* gate-source voltage *or* gate current as independent control variable




- Models are fully equivalent as long as we choose

$$\beta = \frac{g_m v_{gs}}{i_g} = \frac{g_m}{sC_{gs}} = \frac{\omega_T}{j\omega} = -j \frac{\omega_T}{\omega}$$
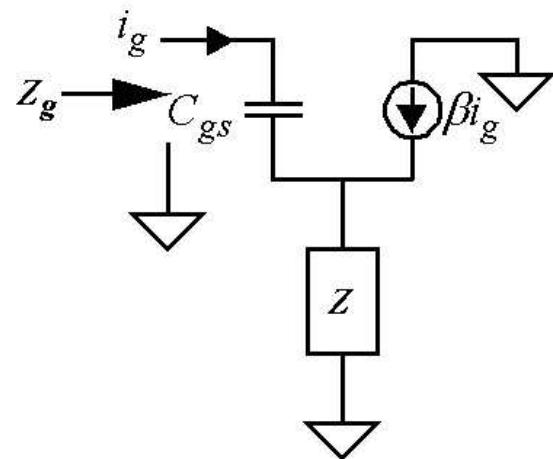
# View from the gate: Load in source

- Consider input impedance of the following at  $\omega \ll \omega_T$ :



$$Z_g = \frac{1}{j\omega C_{gs}} + (\beta + 1)Z \approx \frac{1}{j\omega C_{gs}} + \left(-j \frac{\omega_T}{\omega}\right)Z$$


- The non-intuitive behavior comes from the second term: The impedance  $Z$  gets multiplied by a (negative) imaginary constant.

# What does multiplication by $-j\omega_T/\omega$ do?

- Turns  $R$  into capacitance =  $1/\omega_T R$ .
- Turns  $L$  into resistance =  $\omega_T L = g_m(L/C_{gs})$ .
- Turns  $C$  into *negative* resistance =  $-\omega_T/\omega^2 C$ .
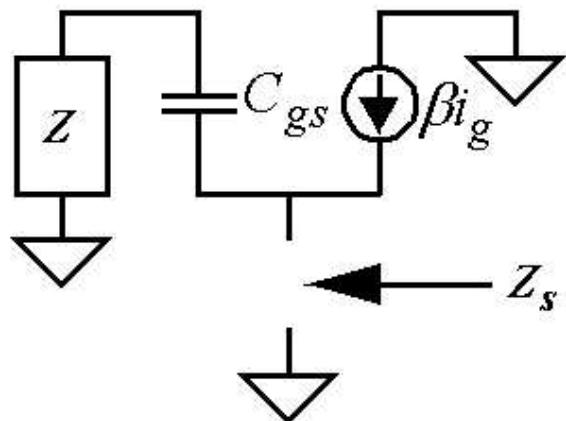
## View from the source: Load in gate

- Now consider input impedance of the following:



$$Z_s = \frac{\frac{1}{j\omega C_{gs}} + Z}{\beta + 1} \approx \frac{1}{g_m} + \left(j\frac{\omega}{\omega_T}\right)Z$$


- This time,  $Z$  gets multiplied by a  $+j$  factor.

# What does multiplication by $+j\omega/\omega_T$ do?

- Turns  $R$  into inductance =  $R/\omega_T$ .
- Turns  $C$  into resistance =  $1/\omega_T C = (C_{gs}/C) (1/g_m)$ .
- Turns  $L$  into negative resistance =  $-\omega^2 L/\omega_T$ .
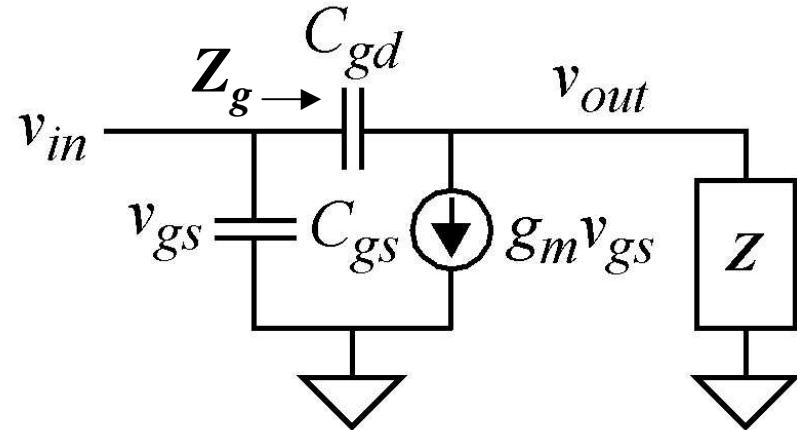
# View from the gate: Load in drain

- Consider (partial) input impedance of the following:



$$Z_g \approx \frac{1}{sC_{gd}(1 + g_m Z)}$$
$$Z_g \approx \frac{1}{sC_{gd} g_m Z} \text{ if } |g_m Z| \gg 1$$

- This is the generalized Miller effect:  $C_{gd}$  is multiplied by *complex* gain when viewed by gate.

# What does multiplication by $g_m Z$ do?

- Turns  $R$  into capacitance =  $C_{gd}(g_m R)$ ; this is just the classic Miller effect.
- Turns  $C$  into resistance =  $(C/C_{gd})(1/g_m)$ .
- Turns  $L$  into negative conductance =  $-\omega^2 g_m L C_{gd}$ .



# Why SIBs are strange

---

- Apparent weirdness arises because of feedback around complex gains.
  - Phase shift associated with complex gains causes impedances to change *character*, not just magnitude.
  - The strangeness evaporates once you spend a little time studying where it comes from.
-

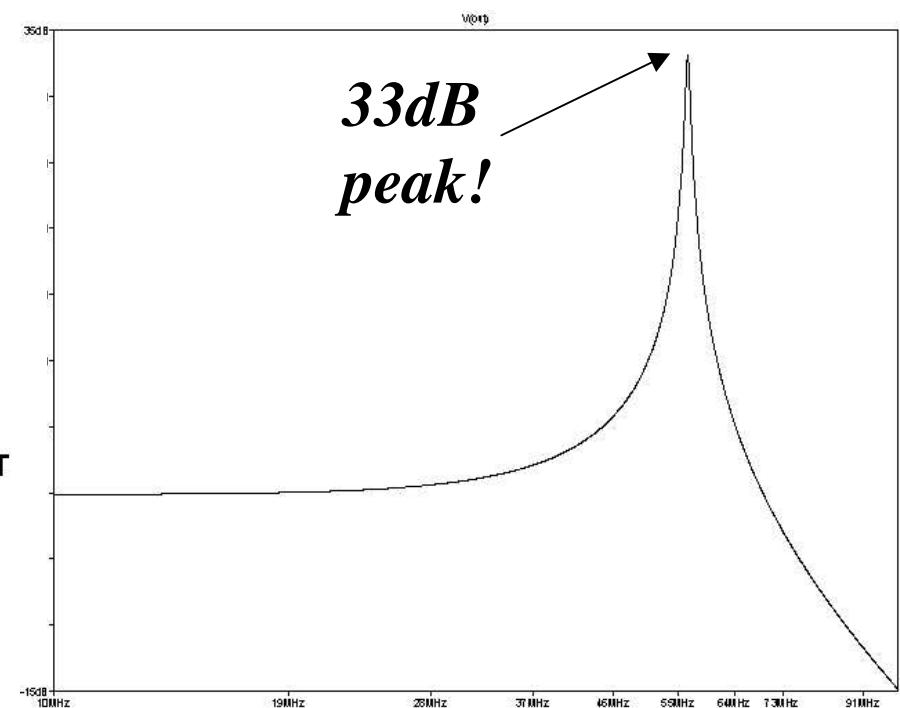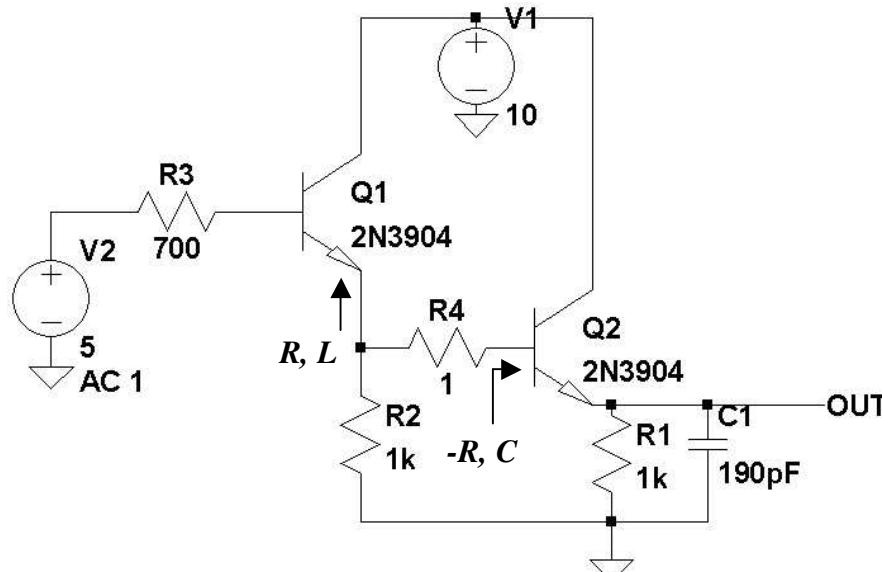
# SIBs example: Cascaded followers

- Familiar circuit has surprising, terrifying but *understandable* behavior:




# Cascaded followers: The fix

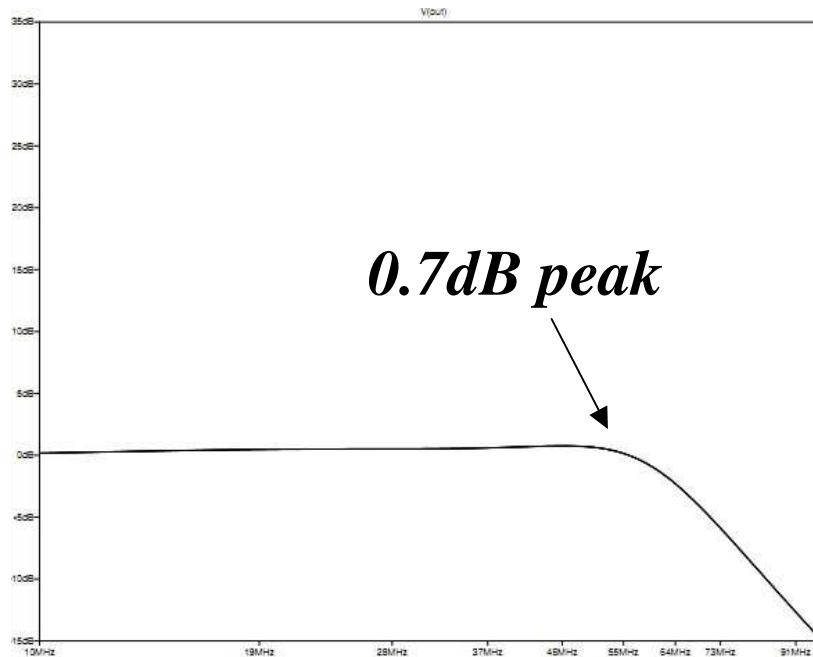- Problem is negative  $R$ , so add  $R4$  ( $220\Omega$ ) to cancel it:



- Shunt R4 with a capacitor to reduce BW loss.
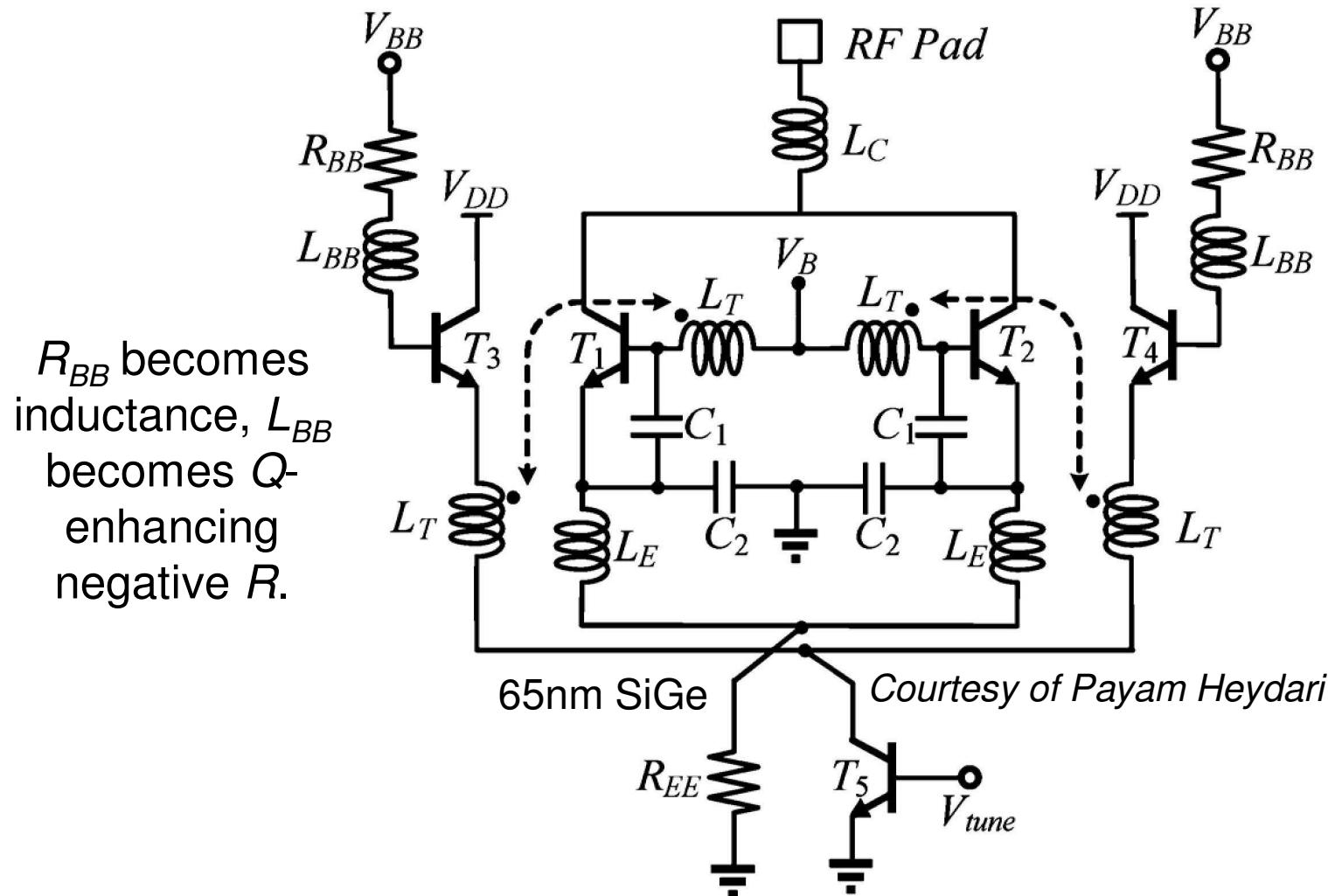
# *Exploiting SIBS: 200GHz push-push VCO*




---

# **Extreme Circuit Design:**


## *Oscillator Tricks*

---


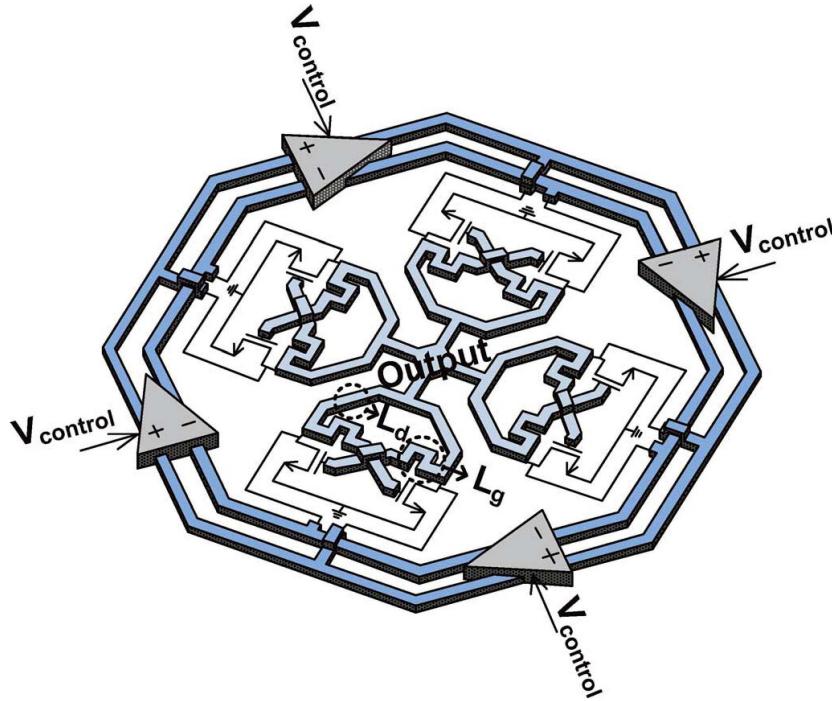
# 280GHz quad-push oscillator (65nm CMOS)



Courtesy of Ehsan Afshari



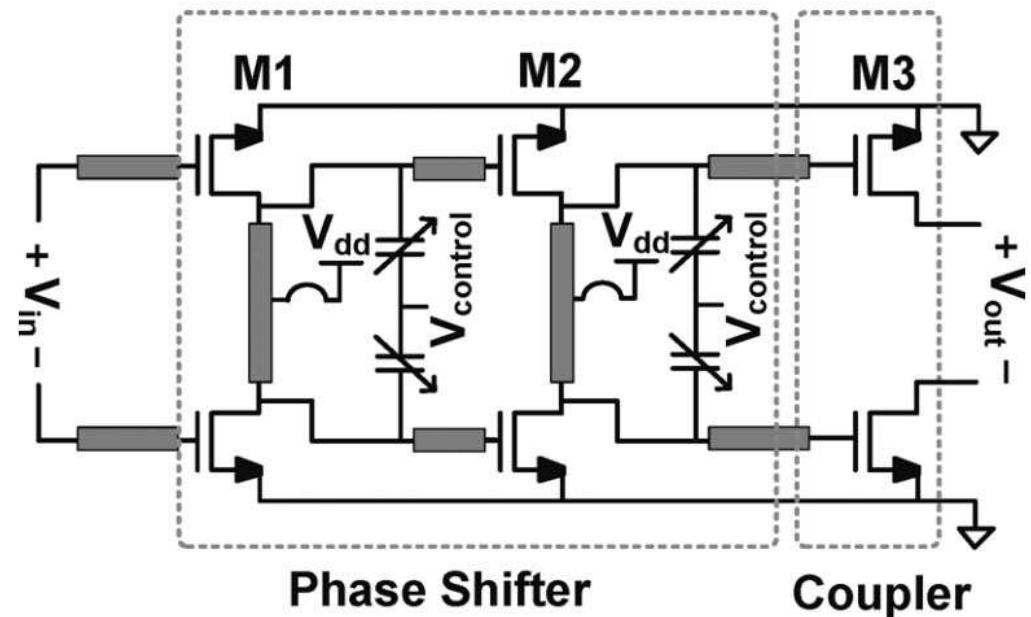

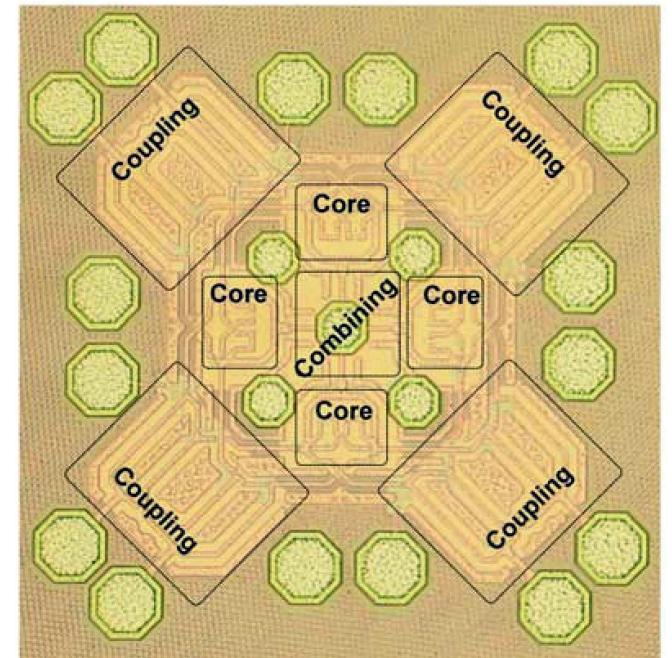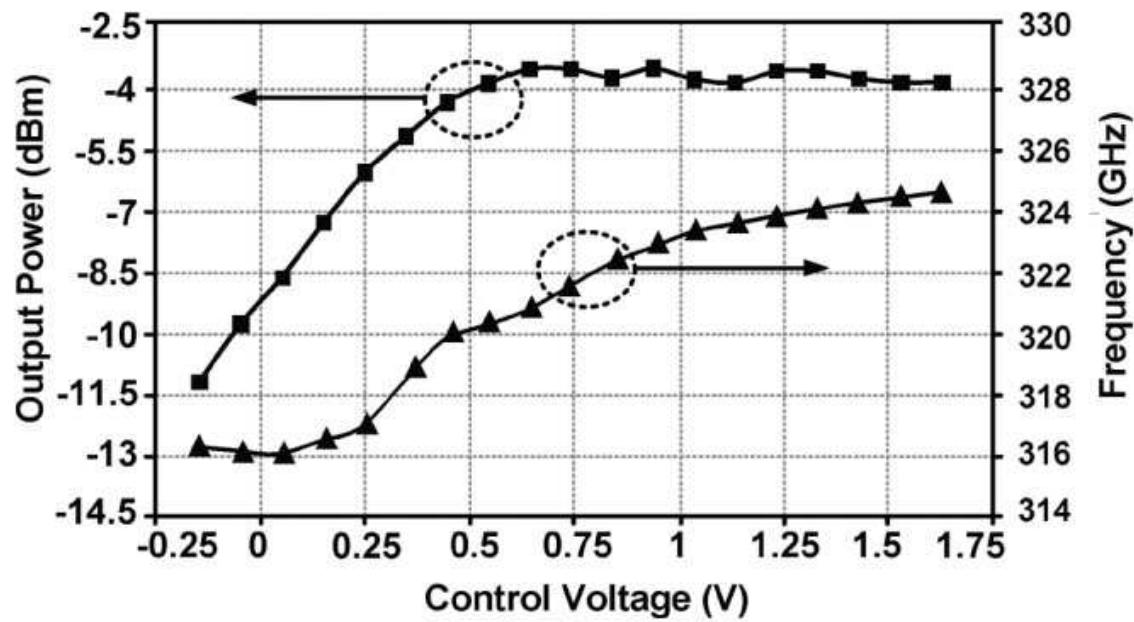
# Measured performance of 280GHz oscillator




Courtesy of Ehsan Afshari

# 300GHz triple-push SiGe synthesizer

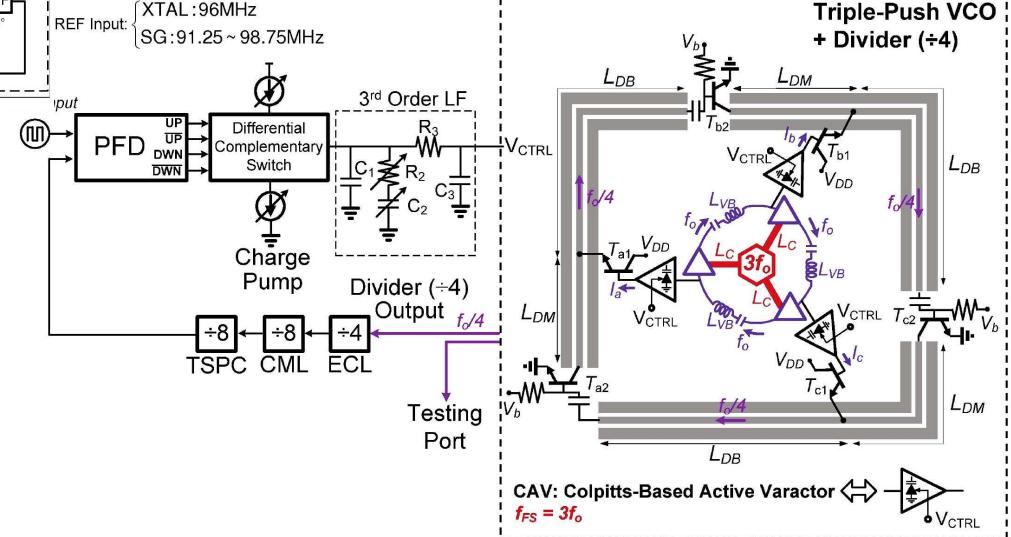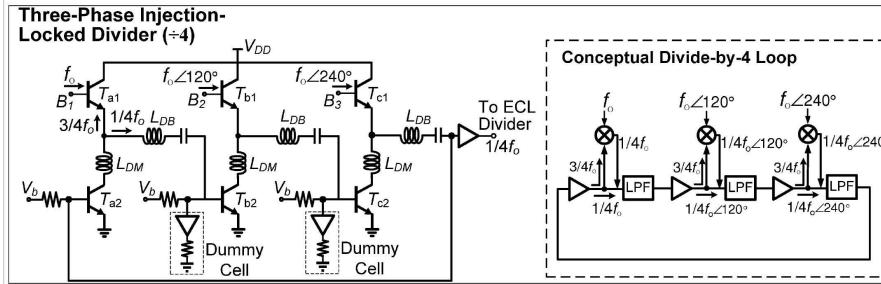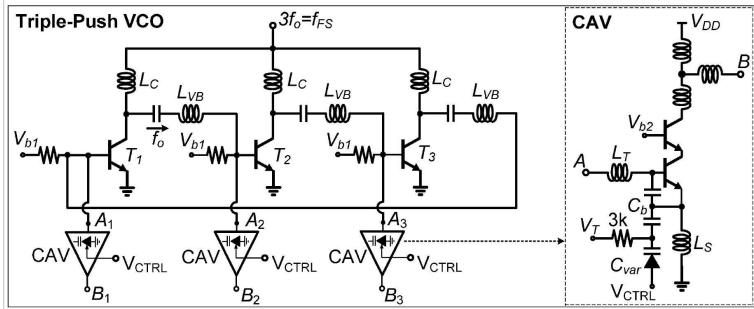


Courtesy of Payam Heydari

# Return of superregeneration

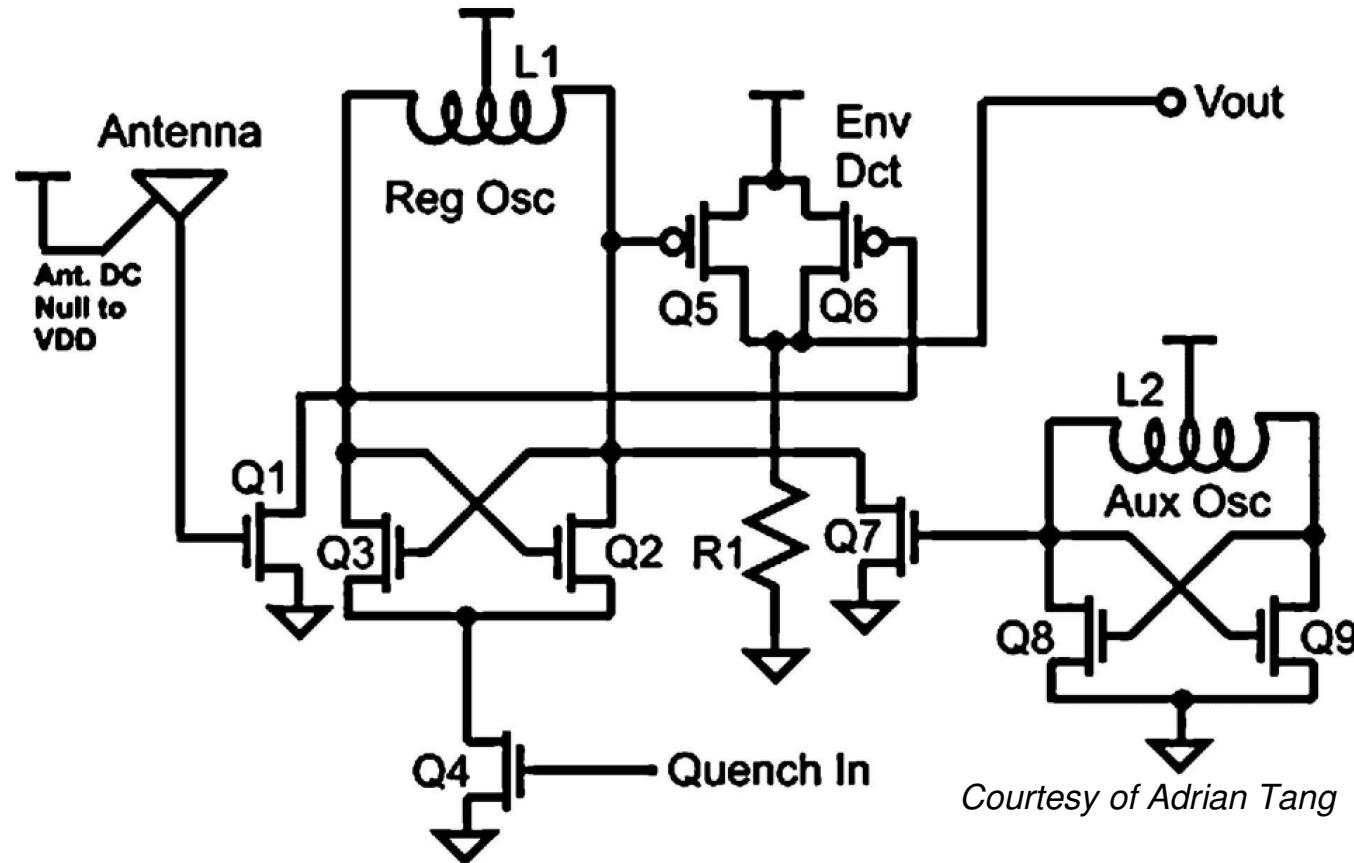


349GHz receiver in 65nm CMOS;  
495GHz in 40nm

# Tri-band imaging result

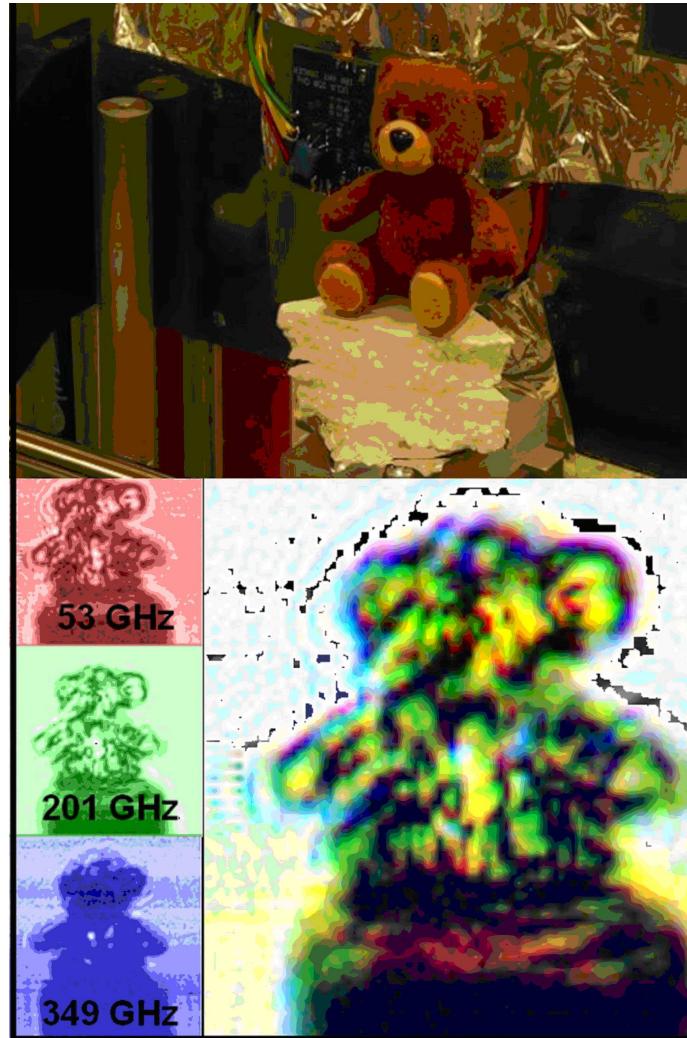

*Courtesy of Adrian Tang*


# PLL frequency synthesis challenges

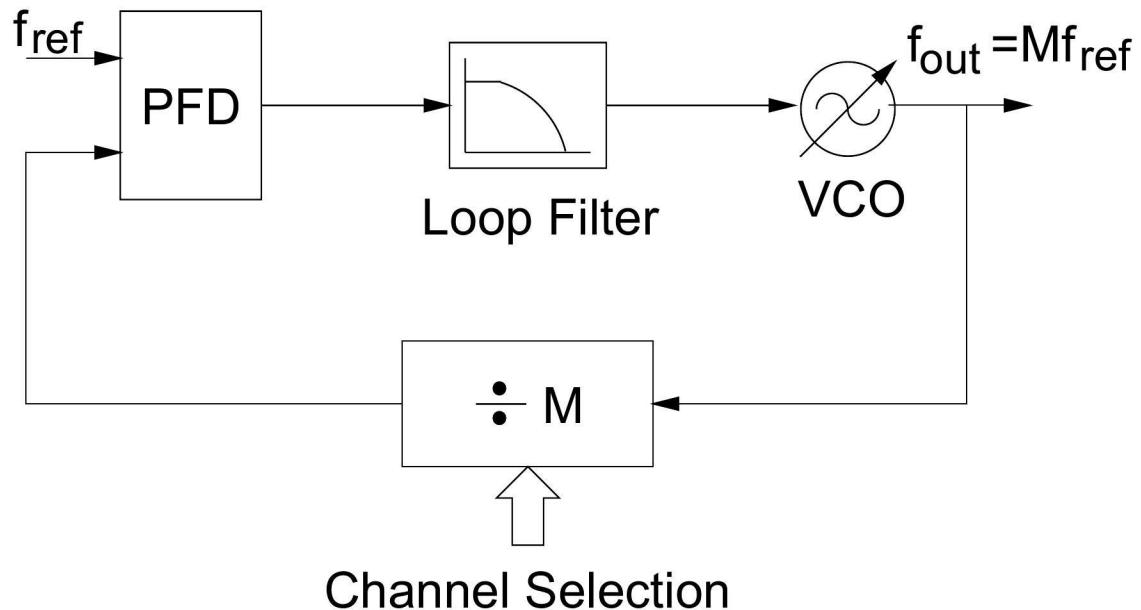


- Reference is a crystal oscillator.

- $f_{out} = M \times f_{ref}$
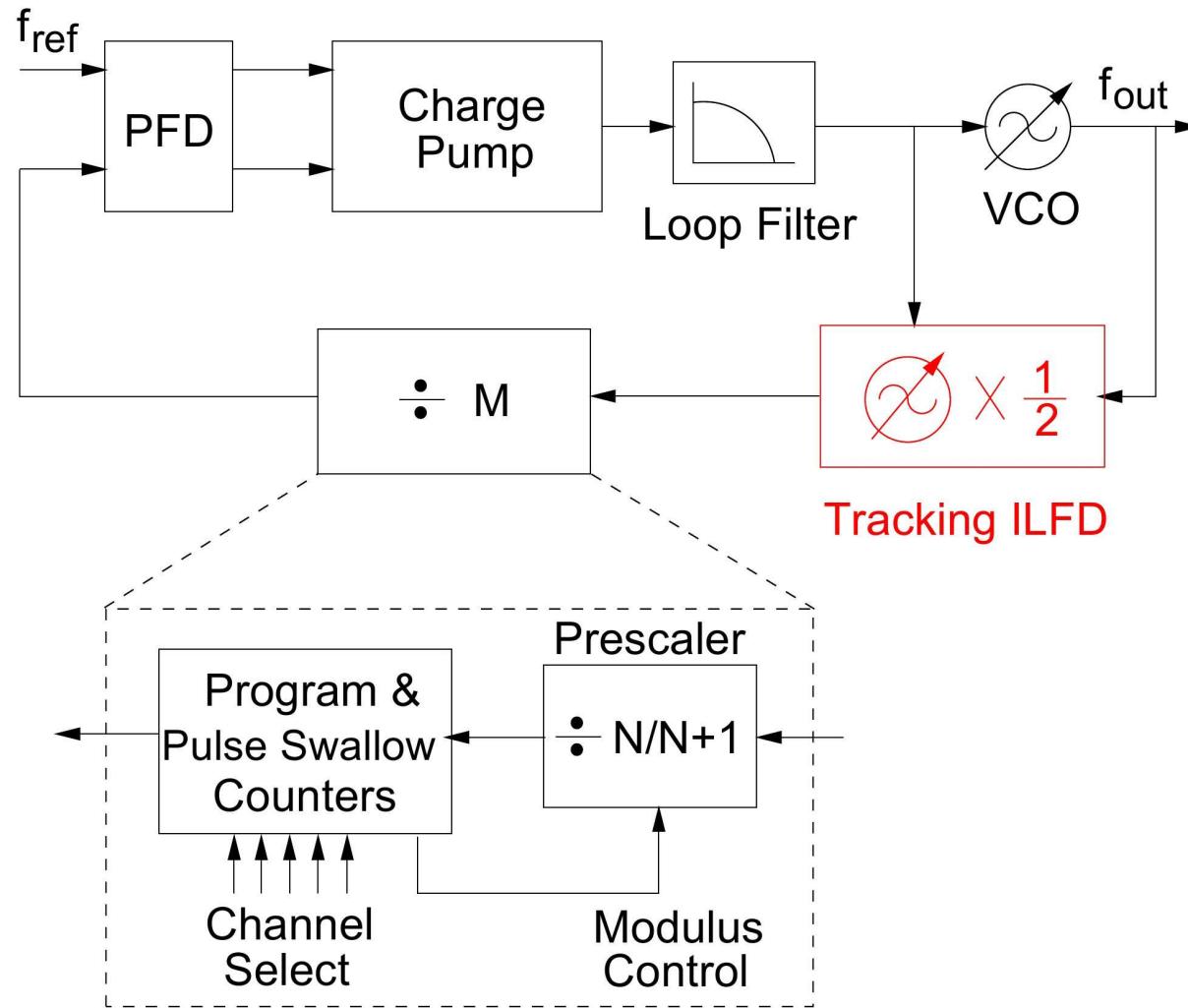
# Injection-locking eases prescaler design



# Injection-locking uses embedded mixing

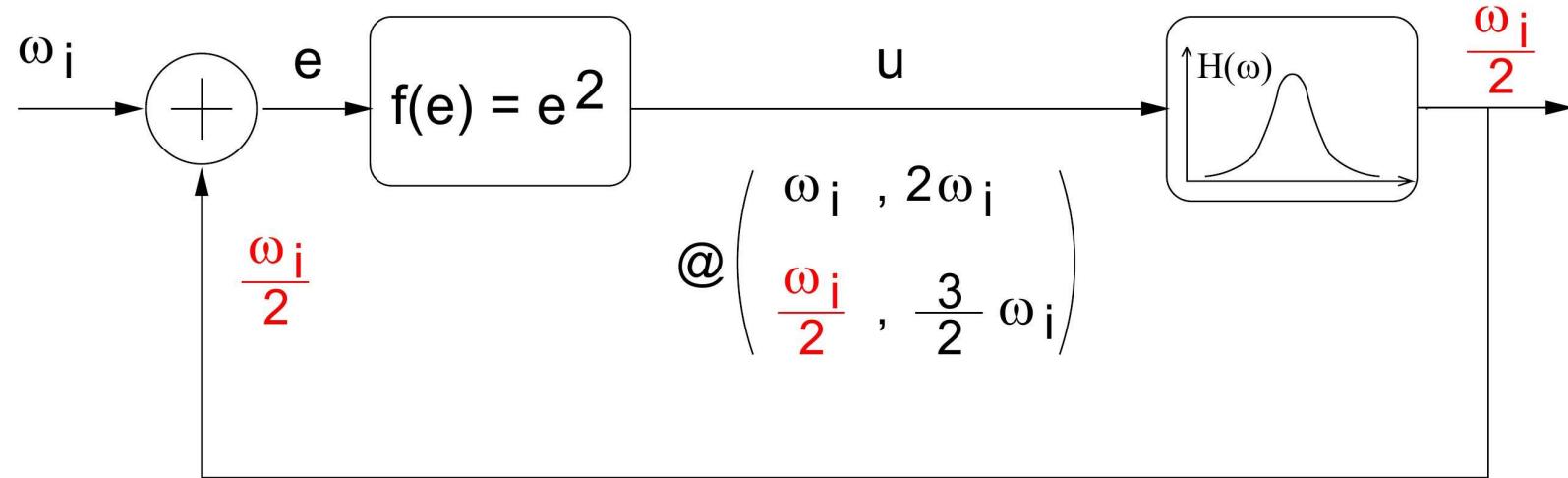


- Example above is a divide-by-2 prescaler.
  - Second-order nonlinearity creates mixing products.
  - Filter preserves only difference component ( $\omega_i/2$ ).

# Injection-locked dividers at freq. extremes


- Maximum input frequency of ILFD can (greatly) exceed device  $f_T$ .
  - Key elements are nonlinearity and filtering, neither of which is bounded directly by  $f_T$ .
  - Basic requirement is to support oscillation at desired *output* frequency, which is often a tiny fraction of the input frequency.
- Power consumption is also typically much lower than for conventional FF-based dividers.
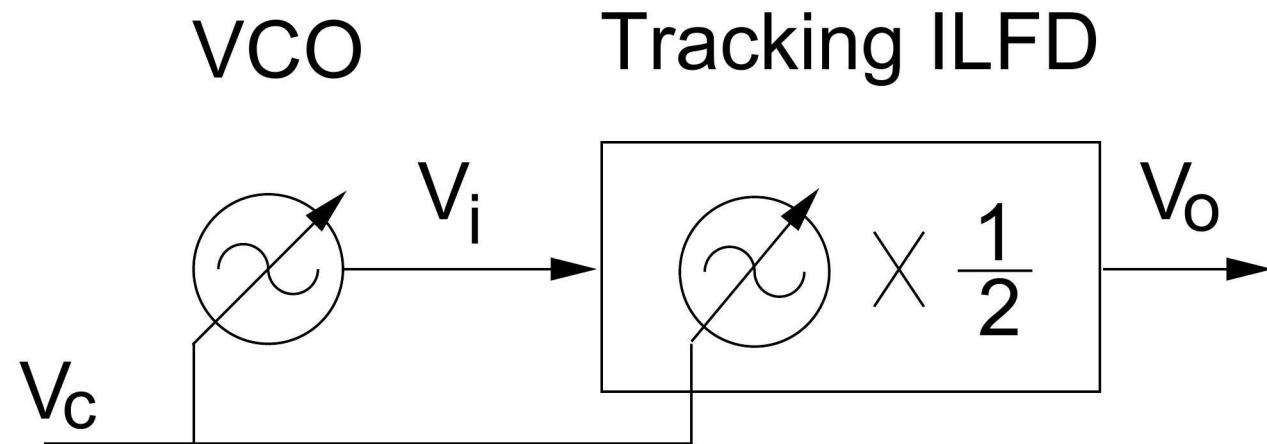
# Injection-locking for frequency synthesis



- Extended locking range provided by tuning ILFD filter to track VCO.

# Representative CMOS ILFD

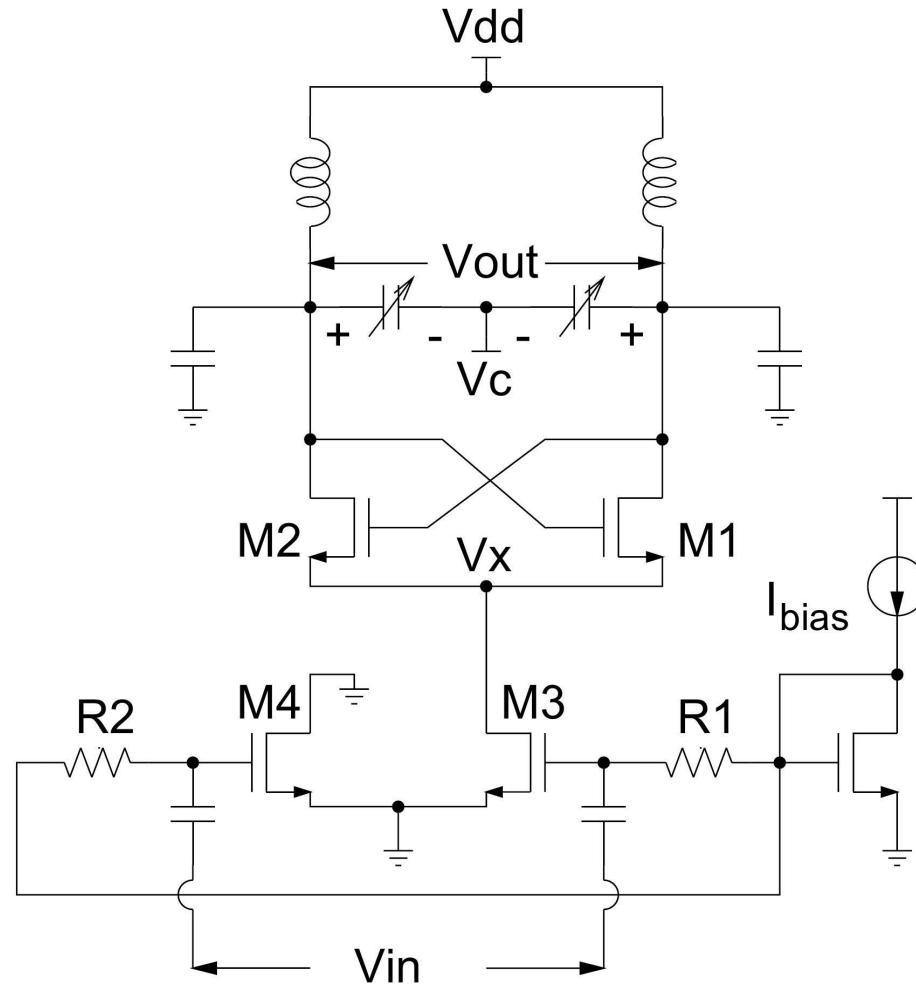


# Need interconnect, too

- Mode-free microstrip at 670 GHz and higher requires thin, fragile substrates.
- Primary conductor losses increase as the substrate is thinned according to

$$\alpha_{\text{skin}} \propto \epsilon_r^{1/2} T^{-1}$$

- A low- $\epsilon_r$  substrate such as BCB ( $\epsilon_r=2.5$ ) reduces attenuation compared to a Si substrate with  $\epsilon_r$  of ~11–13.
- $10\mu\text{m}$  BCB thickness represents good compromise between interconnect density and line attenuation.

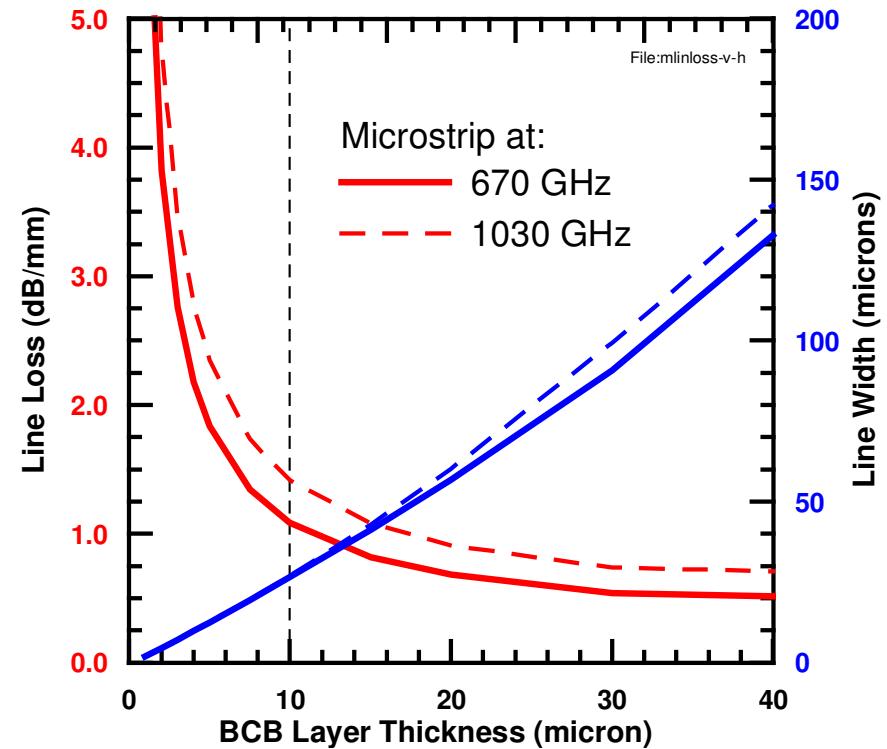- Loss of the order of  $1.5\text{dB/mm}$  at  $1\text{THz}$ .



# Fixturing interconnect matters, too

- HE11-mode THz waveguide now available.
- Attenuation below 3dB/m.



*Source: Swissto12*




---

# **Extreme Circuit Design:**


## *Frequency multiplication*

---


# NGC 670 GHz SSPA

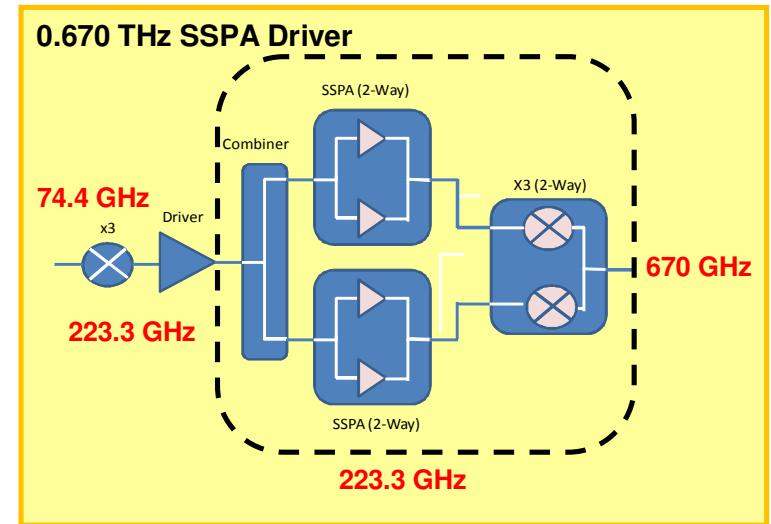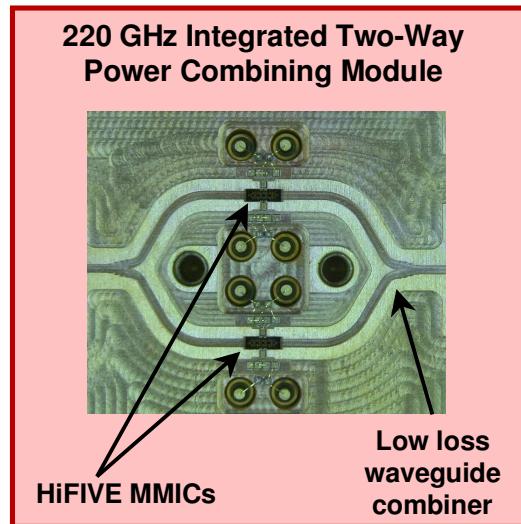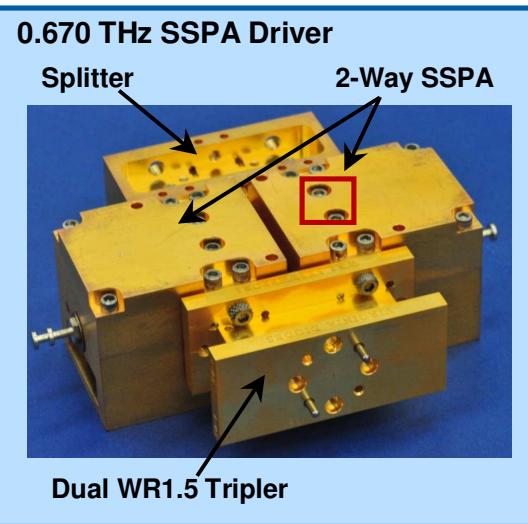

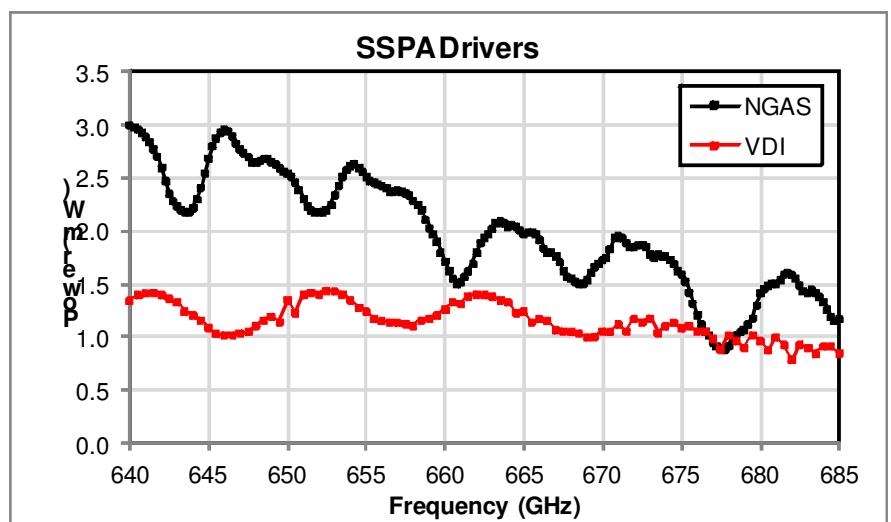- Power combining of 2 two-way SSPA modules (4-way combining of MMICs in total)
- MMIC housing and waveguide combiner integrated in single module to reduce interconnect losses
- Each SSPA module produces 110 mW @ 220 GHz with 9-13 dB gain
- Tripled, power-combined output is 1-3 mW from 0.640-0.685 THz




# Passive doubler for 480GHz output

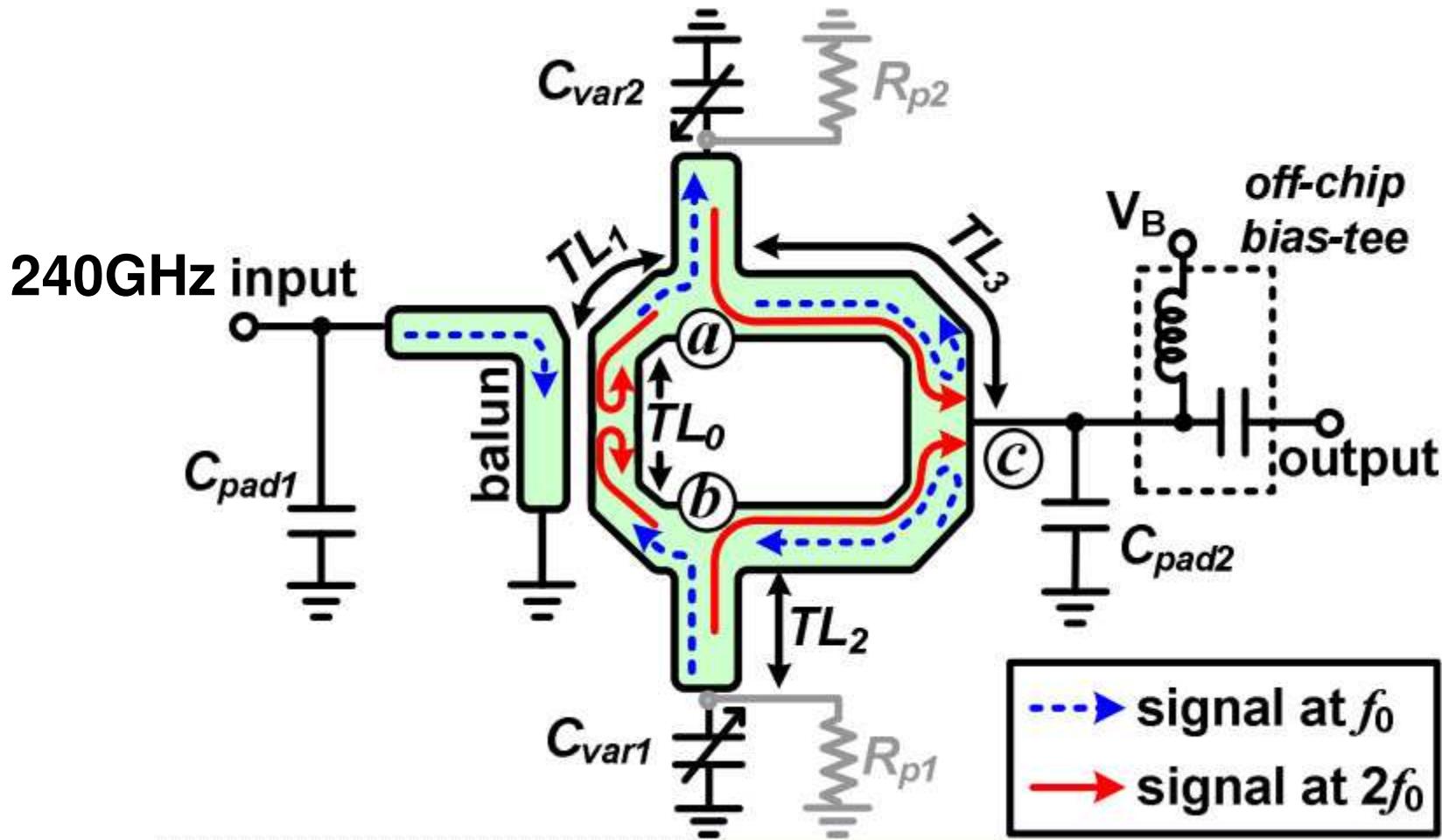


Courtesy of Ehsan Afshari
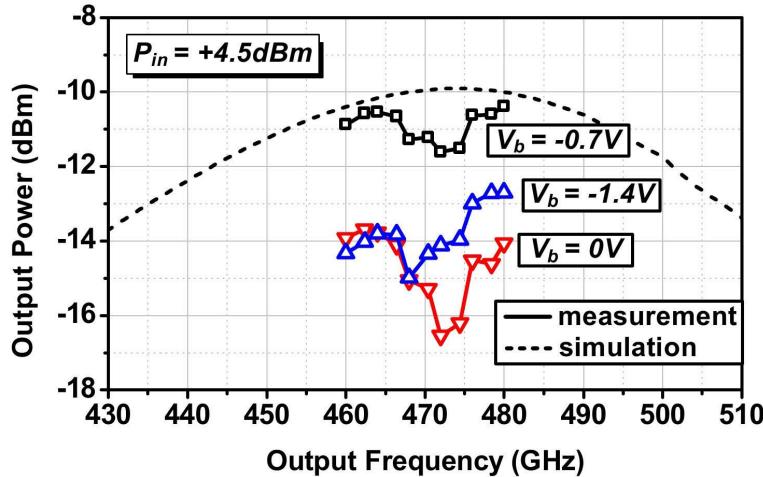
# Measured performance of passive doubler




(a)

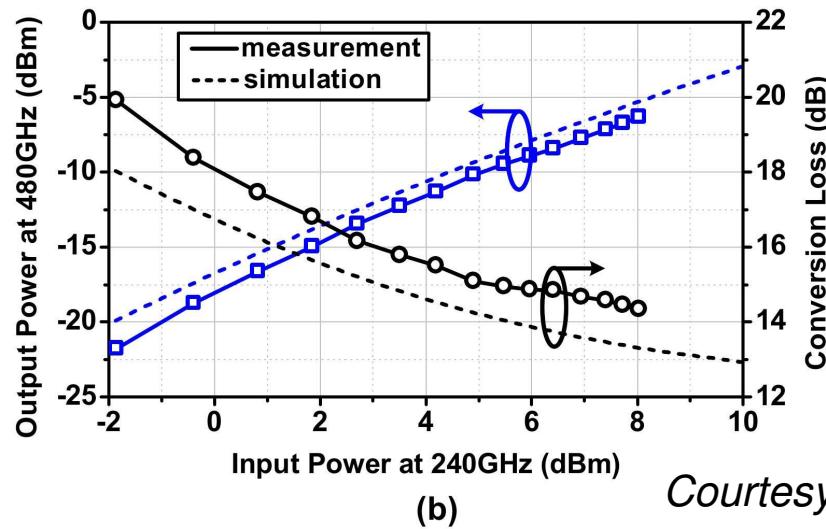


(b)

Courtesy of Ehsan Afshari

# 2D shockwave line for fast pulses

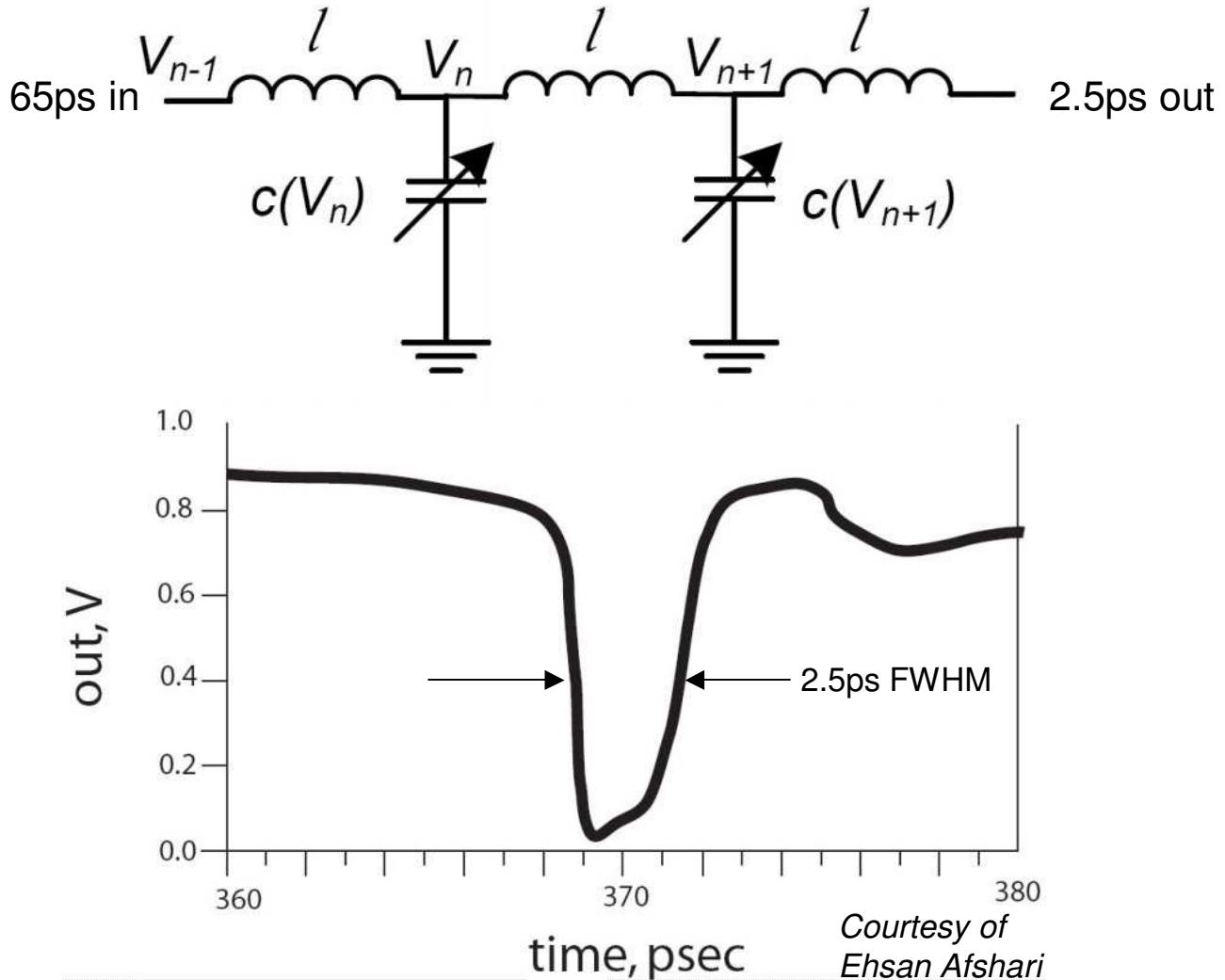

# 2D shockwave fabric for higher power

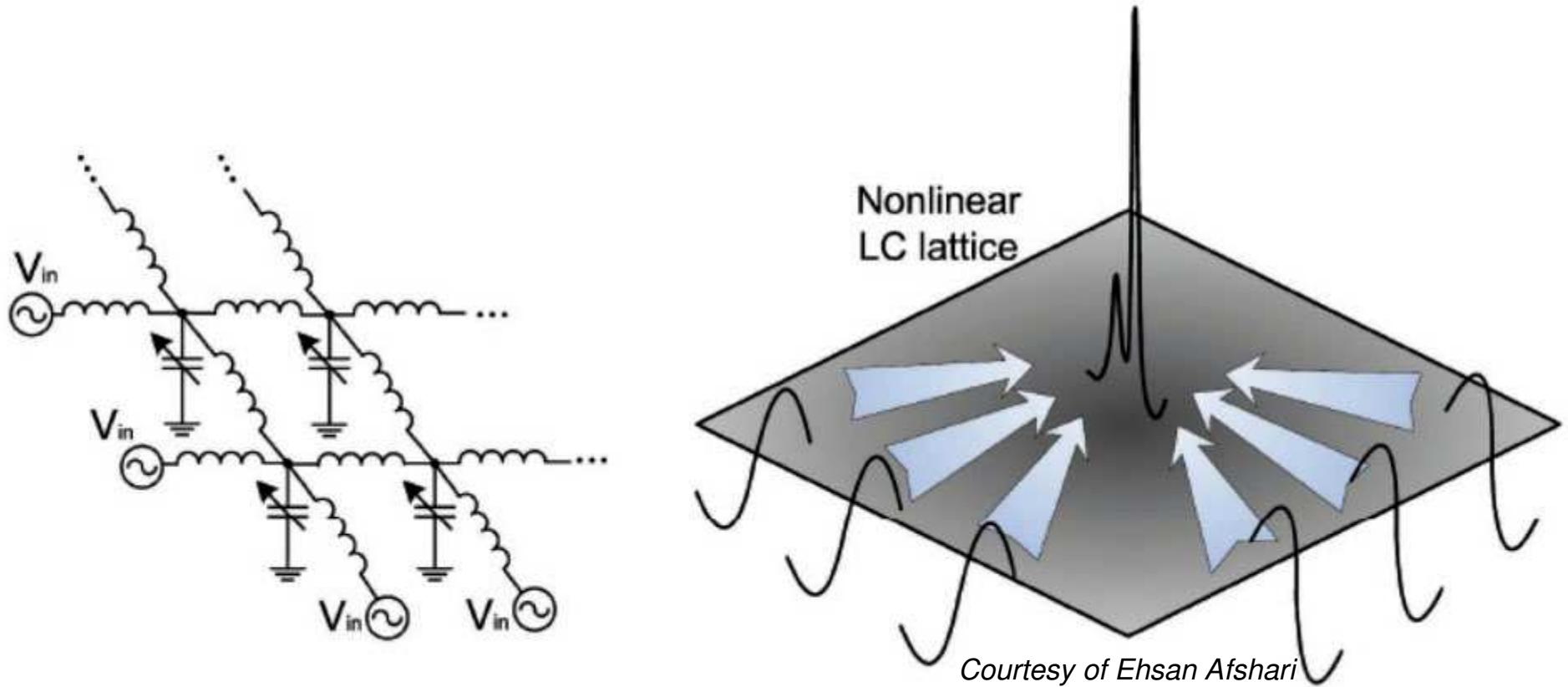

# Summary

- Moore's law continues to give us faster devices.
- Appropriate circuit techniques can allow operation at frequencies near device limits.
- Fuller exploitation of SIBs, nonlinearities and parametric (LTV) phenomena can push frequencies of operation *beyond*  $f_T$ .

# References

- [Goo] J.S. Goo, *High Frequency Noise in CMOS Low-Noise Amplifiers*, Doctoral Dissertation, Stanford University, August 2001.
- [Jones] H. E. Jones, US Pat. #3,241,078, "Dual Output Synchronous Detector Utilizing Transistorized Differential Amplifiers," issued March 1966.
- [Lee] *The Design of CMOS Radio-Frequency Integrated Circuits*, 2<sup>nd</sup> edition, Cambridge U. Press, 2004.
- [Shaeffer] D. Shaeffer and T. Lee, "A 1.5-V, 1.5-GHz CMOS Low Noise Amplifier," *IEEE J. Solid-State Circuits*, v.32, pp. 745-758, 1997.
- [Terrovitis] M. T. Terrovitis and R. G. Meyer, "Noise in Current-Commutating CMOS Mixers," *IEEE Journal of Solid-State Circuits*, vol. 34, No. 6, June 1999.